

# EECS 370 - Lecture 9

## Sequential Logic



# Announcements

- P1s & M due tonight!
- P2a due Thu 2/16
  - Walkthrough available on website
- HW 2 due Mon 2/6

# Next few lectures: Digital Logic


- Lectures 1-7:
  - LC2K and ARMv8/LEGV8 ISAs
  - Converting C to Assembly
  - Function Calls
  - Linking
- Lecture 8:
  - Finish up linking
  - Combinational Logic
- **Today:**
  - **Sequential Logic**



# Sequential Logic

- Can we build a processor out of these combinational elements?
- How to build something like a program counter (PC)?
  - Increment it for every instruction... fine, use an adder
  - But only increment it once ready to move on to next instruction
  - That takes a finite amount of time... until then we need to "remember" the current value
- Combinational logic's output is determined from current input
  - But computers have "state" – they remember previous inputs and behave differently based on its history
- Examples of state
  - Registers
  - Memory
  - PC
- Sequential logic's output depends not only on current input, but also the current state
- This lecture will show you how to build sequential logic from gates
  - Key is feedback




# Using feedback to "remember"

 

- This remembers its initial value!
- Very basic memory
- What's wrong with this, though?

   
# Let's look at the following circuit

Useful identify:  
 $\text{NOR}(0, X) = \text{NOT}(X)$




| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | $\bar{Q}$ |

 When  $R=S=0$ , turns  
into our memory  
element!




Let's look at the following circuit

 

| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | Q         |
| 0 | 1 | 0 | 1         |

What is the value of Q if R is 1 and S is 0?

Let's look at the following circuit

 

| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | Q         |
| 0 | 1 | 0 | 1         |
| 1 | 0 | 1 | 0         |


What is the value of Q if R is 0 and S is 1?

Poll


 
# SR Latch

- So this circuit (an SR latch):
  - "Sets" Q to 1 when  $S=1$   $R=0$
  - "Resets" Q to 0 when  $S=0$   $R=1$
  - "Latches" Q when  $S=0$   $R=0$
  - What about when  $S=1$   $R=1$  ?




| S | R | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | $\bar{Q}$ |
| 0 | 1 | 0 | 1         |
| 1 | 0 | 1 | 0         |
| 1 | 1 | 0 | 0         |

**BAD! Why?**
 
# SR Latch – Undefined behavior


- If  $S=1$ ,  $R=1$ , then  $Q$  and its inverse are both 0
- If inputs then change to  $S=0$ ,  $R=0$ , we get this circuit




- This is unstable! Output rapidly oscillates between 0 and 1
 
# Improving SR Latch

- SR Latch works great at saving a bit of data...
  - Unless  $S=R=1$ , even for a fraction of a second
- Idea: let's prevent that from happening by adding AND gates in front of each input
  - Impossible for R and S to both be 1




# Transparent D Latch

 

Next state is set

| D | G | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | $\bar{Q}$ |
| 0 | 1 | 0 | 1         |
| 1 | 0 | Q | $\bar{Q}$ |
| 1 | 1 | 1 | 0         |

 Set state  
is retained  
when gate  
is low



No invalid  
states 😊


# Transparent D Latch

- When G ("gate") is high,  $Q=D$  (the latch is "transparent")
- When G is low, Q "latches" to the value of D at that instant and remembers, even if D changes later


| D | G | Q | $\bar{Q}$ |
|---|---|---|-----------|
| 0 | 0 | Q | $\bar{Q}$ |
| 0 | 1 | 0 | 1         |
| 1 | 0 | Q | $\bar{Q}$ |
| 1 | 1 | 1 | 0         |

Next state is set


Set state is retained when gate is low

 

# D-Latch Timing Diagram

 


# D-Latch Timing Diagram

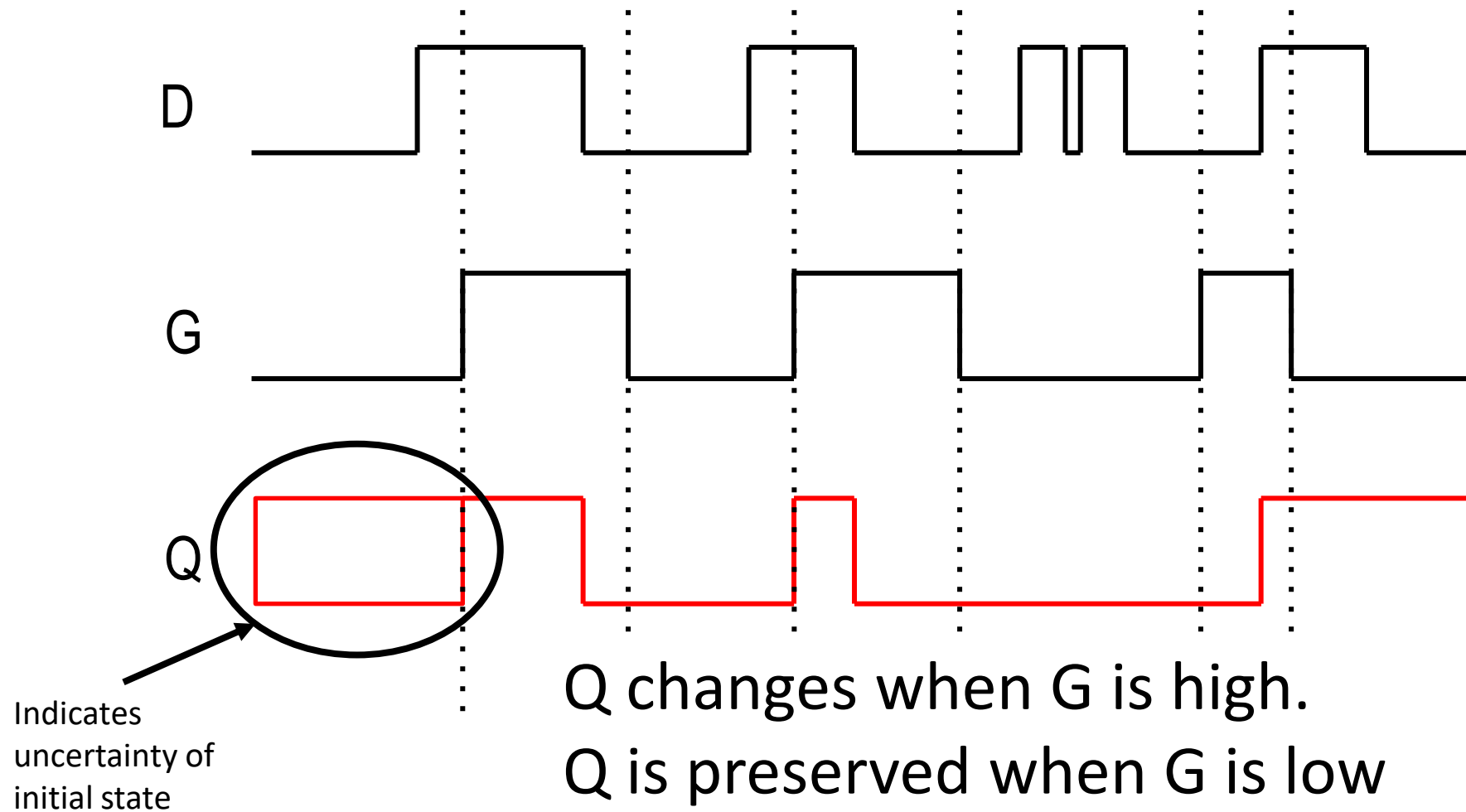
 
# Is D-Latch Sufficient?


- Can we use D-latches to build our PC logic?
- Idea:
  - Use 32 latches to hold current PC, send output Q to memory
  - Also pass output Q into 32-bit adder to increment by 1 (for word-addressable system)
  - Wrap sum around back into D as "next PC"
  - Once ready to execute next instruction, set G high to update





# Shortcoming of D-Latch

 
- Problem: G must be set very precisely
  - Set high for too short: latch doesn't have enough time for feedback to stabilize
  - Set high for too long: Signal may propagate round twice and increment PC by 2 (or more)
- Challenging to design circuits with exactly the right durations




Not just a problem  
for PC, much of our  
processor will  
involve logic like  
this
 
# Adding a Clock to the Mix

- We can solve this if we introduce a **clock**
  - Alternating signal that switches between 0 and 1 states at a fixed frequency (e.g., 1 GHz)
  - Only store the value the **instant** the clock changes (i.e. the **edge**)



# Adding a Clock to the Mix

 


We won't discuss it further here, but this circuit sets  $Q=D$  **ONLY** when clock transitions from 0 -> 1


Intuitively, the design works by inverting the Gate signals, so only one passes at a time (like a double set of sliding doors)



# D Flip-Flop Timing Diagram

 

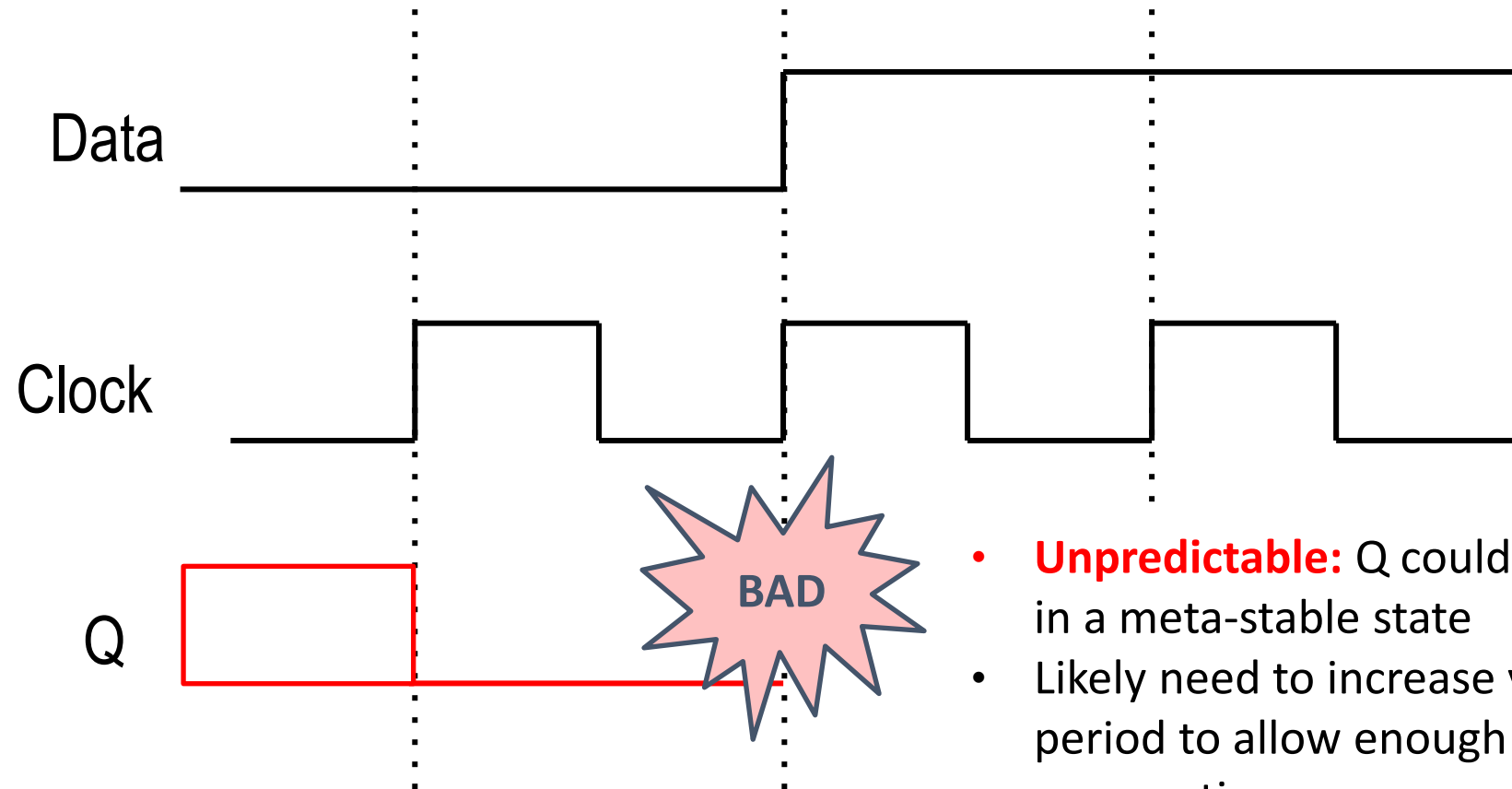
# What happens if Data changes on clock edge?




- **Unpredictable:** Q could be high, low or in a meta-stable state
- Likely need to increase your clock period to allow enough time for signal propagation


# Latches vs Flip-flops

 

D Latch

 

D Flip-flop

 


Enabled D Flip-flop  
(only updates on  
clock edge if 'en' is  
high)

# Finite State Machines

- So far we can do two things with gates:
  1. Combinational Logic: implement Boolean expressions
    - Adder, MUX, Decoder, logical operations etc
  2. Sequential Logic: store state
    - Latch, Flip-Flops
- How do we combine them to do something interesting?
  - Let's take a look at implementing the logic needed for a vending machine
  - Discrete states needed: remember how much money was input
    - Store sequentially
  - Transitions between states: money inserted, drink selected, etc
    - Calculate combinatorially or with a control ROM (*more on this later*)
 
# Input and Output

- Inputs:
  - Coin trigger
  - Refund button
  - 10 drink selectors
  - 10 pressure sensors
    - Detect if there are still drinks left
- Outputs:
  - 10 drink release latches
  - Coin refund latch





# Operation of Machine

- Accepts quarters only
- All drinks are \$0.75
- Once we get the money, a drink can be selected
- If they want a refund, release any coins inserted
- No free drinks!
- No stealing money.




# Building the controller




- Finite State Machine
  - An abstract model describing how the machine should be have under a fixed set of circumstances (i.e. finite states)
  - Remember how many coins have been put in the machine and what inputs are acceptable
- Read-Only Memory (ROM)
  - A cheaper way of implementing combinational logic
  - Define the outputs and state transitions
- Custom combinational circuits
  - Reduce the size (and therefore cost) of the controller

# Finite State Machines

- A Finite State Machine (FSM) consists of:
  - K states:  $S = \{s_1, s_2, \dots, s_k\}$ ,  $s_1$  is initial state
  - N inputs:  $I = \{i_1, i_2, \dots, i_n\}$
  - M outputs:  $O = \{o_1, o_2, \dots, o_m\}$
  - Transition function  $T(S, I)$  mapping each current state and input to next state
  - Output Function  $P(S)$  or  $P(S, I)$  specifies output
    - $P(S)$  is a Moore Machine
    - $P(S, I)$  is a Mealy Machine

 
# FSM for Vending Machine



-  Coin trigger
-  Refund button
-  Drink Select



# FSM for Vending Machine

 

## Is this a Mealy or Moore Machine?

This is Mealy: Mealy output is based on current state *AND* input


## Poll: Mealy or Moore?



**Poll: How many flip-flops would we need to remember which state we're in?**
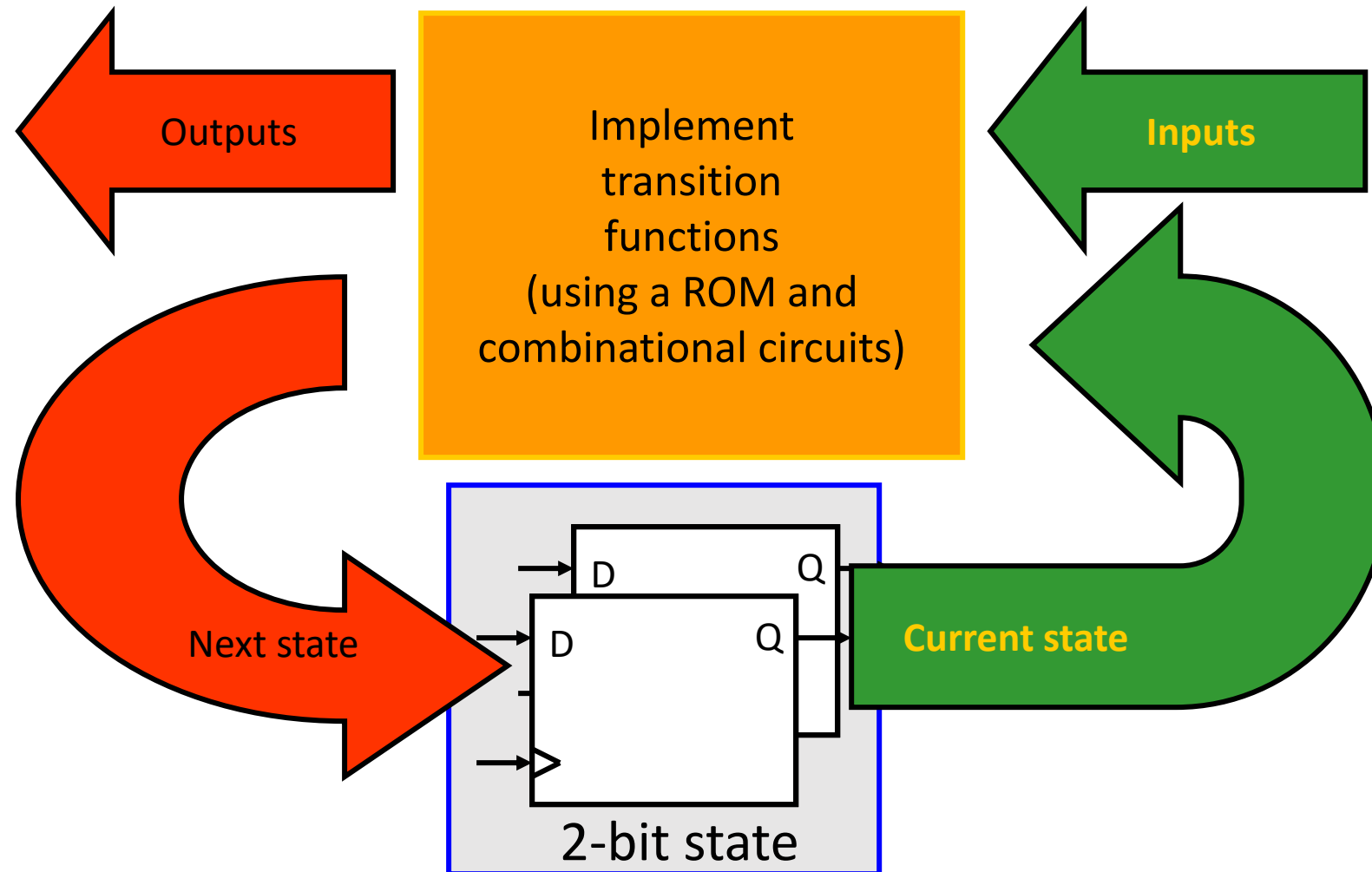
# Implementing an FSM

Poll: How cheaply do you think we can build one of these controllers?



# Implementing an FSM

- Let's see how cheap we can build this vending machine controller!
- [Jameco.com](http://Jameco.com) sells electronic chips we can use
  - D-Flip-flops: \$3, includes several in one package
- For custom combinational circuits, would need to design and send to a fabrication facility
  - Thousands or millions of dollars!!
  - Alternative?

**JAMECO ELECTRONICS** | Log In/Register | Track Orders | Cart 0  
Serving our customers since 1974  
Customer Care 1-800-831-4242

PRODUCTS ▾ MANUFACTURERS ▾ ORDERING ▾ QUOTE REQUEST ▾ WORKSHOP ▾

Product Search:  SEARCH

Home / ICs & Semiconductors / Logic, TTL / 74 Series

### IC 7474 DUAL D TYPE FLIP-FLOP

Jameco Part no.: 50551  
Manufacturer: Major Brands  
Manufacturer p/n: 7474  
HTS code: 8542310000  
Fairchild Semiconductors [59 KB]  
Data Sheet (current) [52 KB]  
Representative Datasheet, MFG may vary

**\$2.95** ea  
1,121 In Stock  
More Available - 7 weeks

Qty

Add to cart

+ Add to my favorites





| # of units | Price (USD) |
|------------|-------------|
| 1+         | \$2.95      |
| 10+        | \$2.59      |
| 100+       | \$2.39      |

Request a Large Quantity Quote

WARNING: Proposition 65

View larger image


You may also like:

|   |  |  |   |
|---|--|--|---|
| <br>74HCT74<br>Major Brands | <br>74HC74<br>Major Brands | <br>74LS74<br>Major Brands | <br>74189<br>Major Brands |
|---|--|--|---|
 
# Implementing Combinational Logic


If I have a truth table:

- Either implement this using combinational logic:



- ...or literally just store the entire truth table in a memory and "index" it by treating the input as a number!
  - Can be implemented cheaply using "Read Only Memories", or "ROMS"

| A | B | C | O |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 



# ROMs and PROMs

## IC 28C256-15 EEPROM 256K-Bit CMOS Parallel



[View larger image](#)

Jameco Part no.: 74843

Manufacturer: [Major Brands](#)

Manufacturer p/n: 28C256-15

HTS code: 8542320050

[Data Sheet \(current\)](#) [116 KB]

[Data Sheet \(current\)](#) [499 KB]

[ST MICRO](#) [62 KB]

[Atmel](#) [371 KB]

[Atmel](#) [67 KB]

Representative Datasheet, MFG may vary

**\$12.25** ea

36 In Stock

More Available - 7 weeks

Qty


1

[Add to cart](#)

[+ Add to my favorites](#)

- Read Only Memory (ROM)
  - Array of memory values that are constant
  - Non-volatile (doesn't need constant power to save values)
- Programmable Read Only Memory
  - Array of memory values that can be written exactly once
- Electronically Erasable PROM (EEPROM)
  - Can write to memory, deploy in field
  - Use special hardware to reset bits if need to update
- 256 KBs of EEPROM costs ~\$10 on Jameco
  - Much better then spending thousands on design costs unless we're gonna make **tons** of these


# 8-entry 4-bit ROM

 

# 8-entry 4-bit ROM

| Input | Output |
|-------|--------|
| 000   |        |
| 001   |        |
| 010   |        |
| 011   |        |
| 100   |        |
| 101   |        |
| 110   |        |
| 111   |        |

 This ROM  
corresponds to this  
truth table




# 8-entry 4-bit ROM

Poll: What's the formula for size of ROM needed?

| Input | Output |
|-------|--------|
| 000   | 1001   |
| 001   | 0100   |
| 010   | 0010   |
| 011   | 1001   |
| 100   | 0010   |
| 101   | 0001   |
| 110   | 1000   |
| 111   | 0000   |

This ROM corresponds to this truth table

 

# Aside: Other Memories


- Static RAM (random access memory)
  - Built from sequential circuits
    - Takes 4-6 transistors to store 1 bit
    - Fast access (< 1 ns access possible)
- Dynamic RAM
  - Built using a single transistor and a capacitor
    - 1's must be refreshed often to retain value
    - Slower access than static RAM
    - Much more dense layout than static RAM
- Both require constant power, or they will lose their data (i.e. are **volatile**)
- These will be used to build computer memory hierarchies (later in class)



# Implementing Combinational Logic

- Custom logic
  - Pros:
    - Can optimize the number of gates used
  - Cons:
    - Can be expensive / time consuming to make custom logic circuits
- Lookup table:
  - Pros:
    - Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly
  - Cons:
    - Size requirement grows exponentially with number of inputs (adding one just more bit **doubles** the storage requirements!)

# Controller Design So far

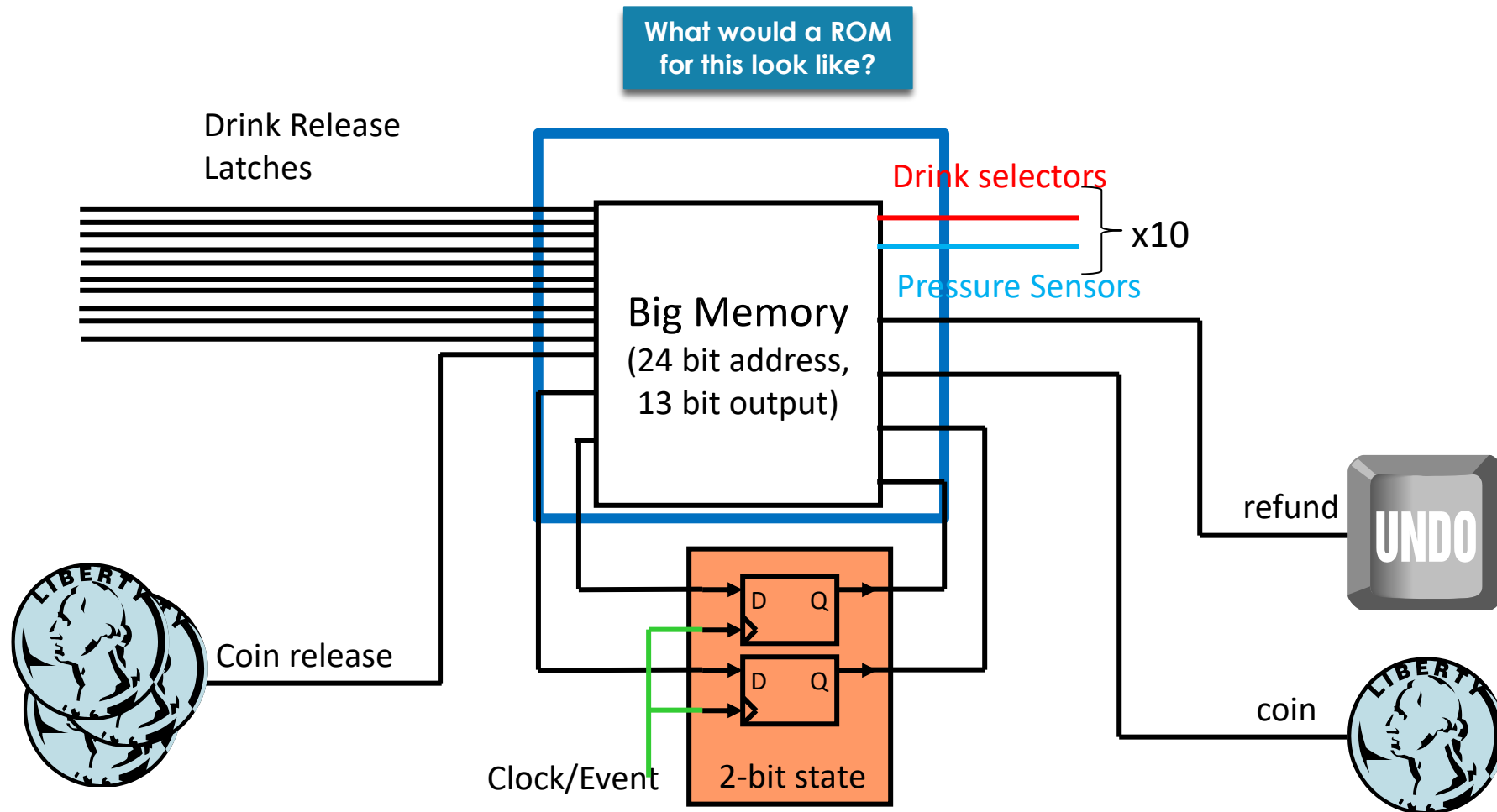

# ROM for Vending Machine

Size of ROM is (# of ROM entries \* size of each entry)

- # of ROM entries =  $2^{\text{input\_size}} = 2^{24}$
- Size of each entry = output size = 13 bits

We need  $2^{24}$  entry, 13 bit ROM memories


- **218,103,808 bits of ROM (26 MB)**
- Biggest ROM I could find on Jameco was 4 MB @ \$6
  - Need 7 of these at \$42??
- Let's see if we can do better



# Reducing the ROM needed

- Idea: let's do a hybrid between combinational logic and a lookup table
  - Use basic hardware (AND / OR) gates where we can, and a ROM for everything more complicated
  - AND / OR gates are mass producible & cheap!
    - ~\$0.15 each on Jameco
 
## IC 74HC08 QUAD 2-INPUT POSITIVE AND GATE



[View larger image](#)

Jameco Part no.: 45225  
Manufacturer: [Major Brands](#)  
Manufacturer p/n: 74HC08  
HTS code: 8542390000  
[Fairchild Semiconductors](#) [83 KB]  
[Data Sheet \(current\)](#) [83 KB]  
Representative Datasheet, MFG may vary

**\$0.49** ea

1,061 In Stock  
More Available - 7 weeks

Qty


[Add to cart](#)

[+ Add to my favorites](#)

# Reducing the ROM needed

- Observation: overall logic doesn't really need to distinguish between **which** button was pressed
  - That's only relevant for choosing **which** latch is released, but overall logic is the same
- Replace 10 selector inputs and 10 pressure inputs with a **single** bit input (drink selected)
  - Use drink selection input to specify which drink release latch to activate
  - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)

# Putting it all together

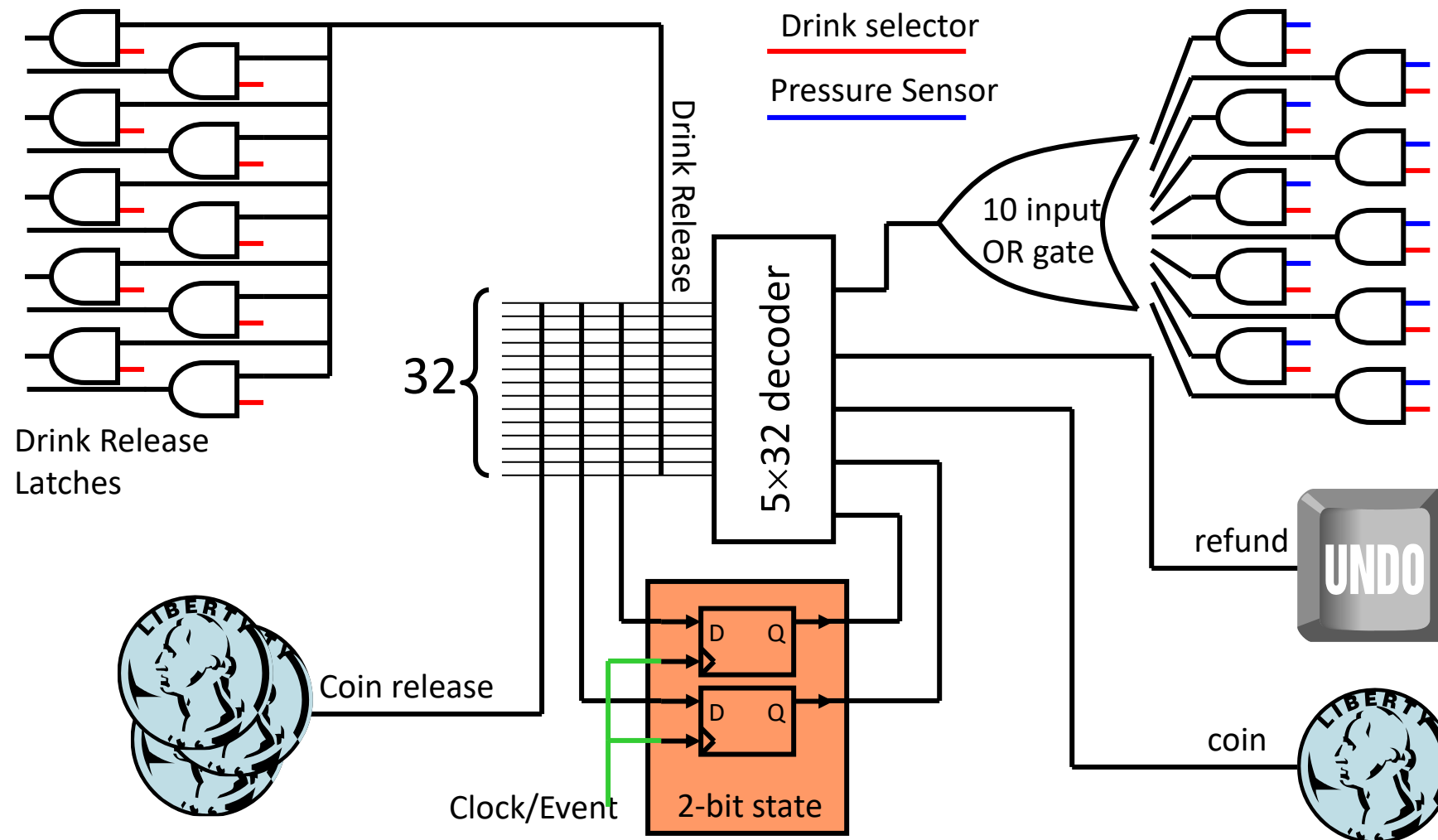



# Total cost of our controller

- Now:
  - 2 current state bits + 3 input bits (5 bit ROM address)
  - 2 next state bits + 2 control trigger bits (4 bit memory)
  - $2^5 \times 4 = 128$  bit ROM
    - 1-millionth size of our 26 MB ROM 😬
- Total cost on Jameco:
  - Flip-flops to store state: \$3
  - ROM to implement logic: \$3
  - AND/OR gates: \$5
  - **Total: \$11**
- Could probably do a lot cheaper if we buy in bulk

# Next Time

- Introduce first processor implementation
- Lingering questions / feedback? I'll include an anonymous form at the end of every lecture: <https://bit.ly/3oXr4Ah>

Me: Mom, can I have  ?

Mom: No we have  at home

