

EECS 370 - Lecture 10

FSM and Single-Cycle Datapath




Announcements

- P2
 - Two parts: part a is due **Thu 2/16**
- HW 3
 - Posted on website, due **Mon 2/20**
- Midterm exam **Thu March 9, 7-9pm**
 - More details soon
- Questions about symbol & relocation tables?
 - <https://eecs370.github.io/#resources>

Reminder

 - D-flip-flops will be the basis of storing bits in this class




Finite State Machines

- Combine combinational logic and sequential logic
- Define a set of "states" that our machine will be in
- "Remember" what state we're in using flip-flops
- Calculate next-state and output logic using combinational logic


Note: This is very similar to Finite State Automata (FSA) from 376, but with a few differences (the input never ends, and the FSM always outputs something)

Input and Output

 - Inputs:
 - Coin trigger
 - Refund button
 - 10 drink selectors
 - 10 pressure sensors
 - Detect if there are still drinks left
- Outputs:
 - 10 drink release latches
 - Coin refund latch



FSM for Vending Machine

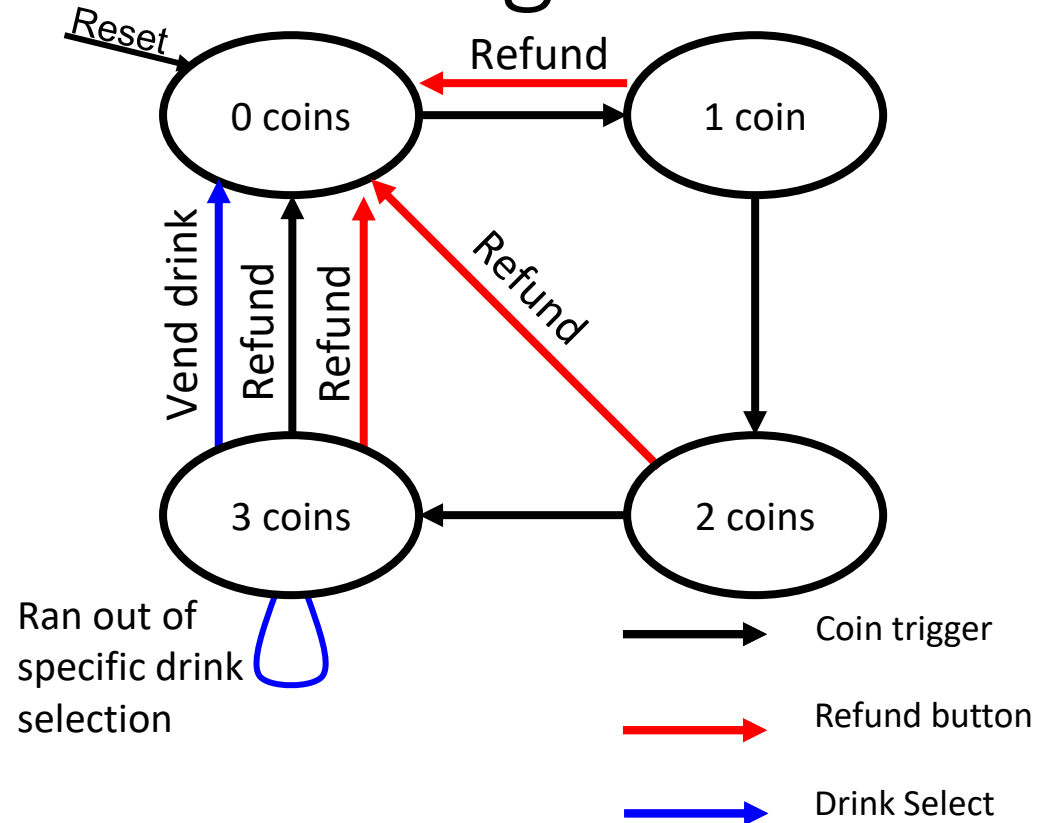


Is this a Mealy or Moore Machine?

This is Mealy: Mealy output is based on current state *AND* input



Implementing an FSM

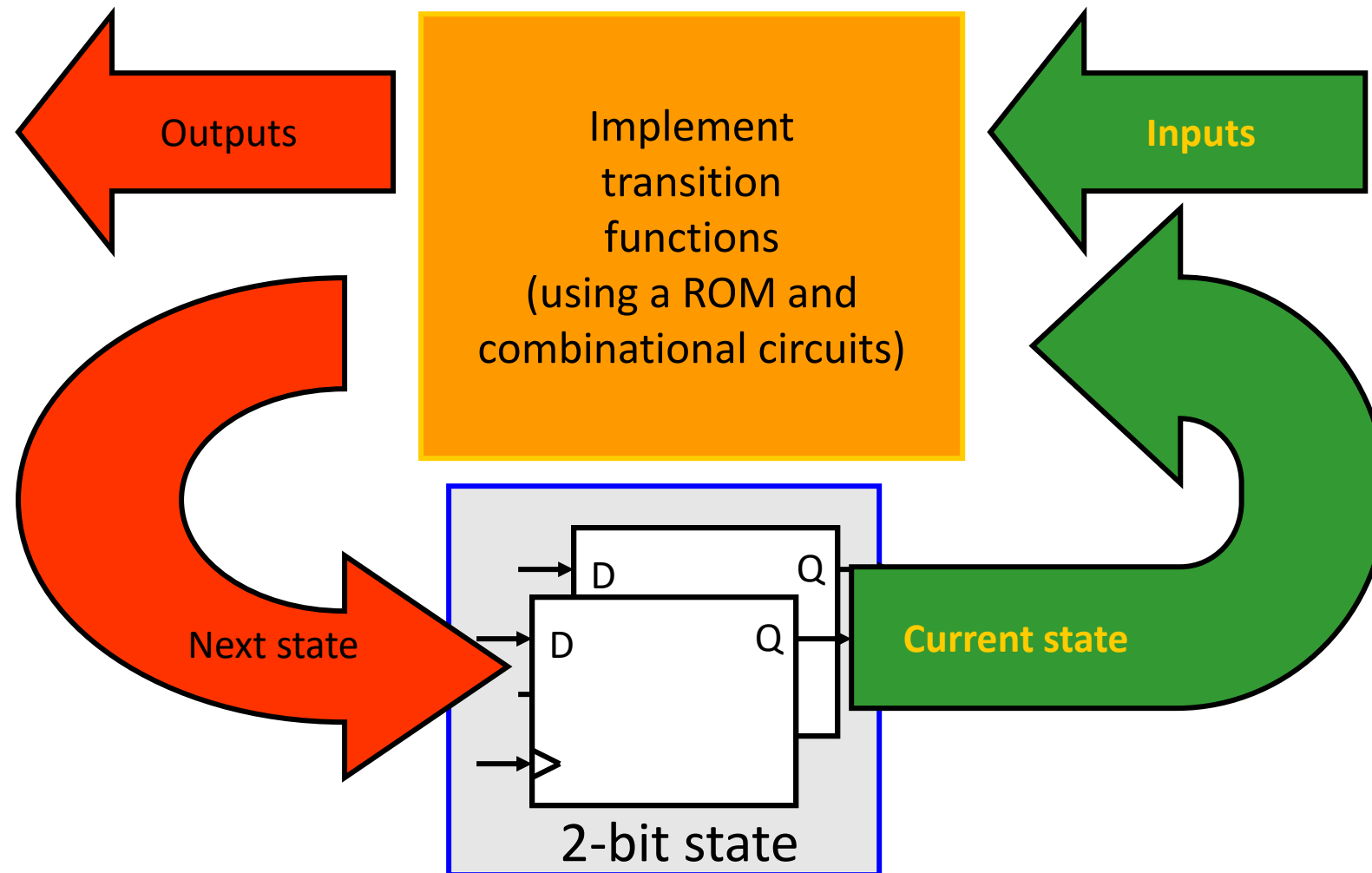

Implementing an FSM

- Let's see how cheap we can build this vending machine controller!
- [Jameco.com](https://www.jameco.com) sells electronic chips we can use
 - D-Flip-flops: \$3, includes several in one package
- For custom combinational circuits, would need to design and send to a fabrication facility
 - Thousands or millions of dollars!!
 - Alternative?

JAMECO ELECTRONICS | Log In/Register | Track Orders | Cart 0
Serving our customers since 1974
Customer Care 1-800-831-4242

PRODUCTS ▾ MANUFACTURERS ▾ ORDERING ▾ QUOTE REQUEST ▾ WORKSHOP ▾

Product Search: SEARCH

Home / ICs & Semiconductors / Logic, TTL / 74 Series

IC 7474 DUAL D TYPE FLIP-FLOP

Jameco Part no.: 50551
Manufacturer: Major Brands
Manufacturer p/n: 7474
HTS code: 8542310000
Fairchild Semiconductors [59 KB]
Data Sheet (current) [52 KB]
Representative Datasheet, MFG may vary

\$2.95 ea
1,121 In Stock
More Available - 7 weeks

Qty

Add to cart

+ Add to my favorites





# of units	Price (USD)
1+	\$2.95
10+	\$2.59
100+	\$2.39

Request a Large Quantity Quote

WARNING: Proposition 65

View larger image


You may also like:

 74HCT74 Major Brands	 74HC74 Major Brands	 74LS74 Major Brands	 74189 Major Brands
---	--	--	---

Implementing Combinational Logic


If I have a truth table:

 - I can either implement this using combinational logic:



- ...or I could literally just store the entire truth table in a memory and just "index" it by treating the input as a number!
 - Can be implemented cheaply using "Read Only Memories", or "ROMS"

A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

ROMs and PROMs

IC 28C256-15 EEPROM 256K-Bit CMOS Parallel



[View larger image](#)

Jameco Part no.: 74843
Manufacturer: [Major Brands](#)
Manufacturer p/n: 28C256-15
HTS code: 8542320050

[Data Sheet \(current\)](#) [116 KB]

[Data Sheet \(current\)](#) [499 KB]

[ST MICRO](#) [62 KB]

[Atmel](#) [371 KB]

[Atmel](#) [67 KB]

Representative Datasheet, MFG may vary

\$12.25 ea

36 In Stock
More Available - 7 weeks

Qty


1

[Add to cart](#)

[+ Add to my favorites](#)

- Read Only Memory (ROM)
 - Array of memory values that are constant
 - Non-volatile (doesn't need constant power to save values)
- Programmable Read Only Memory
 - Array of memory values that can be written exactly once
- Electronically Erasable PROM (EEPROM)
 - Can write to memory, deploy in field
 - Use special hardware to reset bits if need to update
- 256 KBs of EEPROM costs ~\$10 on Jameco
 - Much better then spending thousands on design costs unless we're gonna make **tons** of these


8-entry 4-bit ROM

 

8-entry 4-bit ROM

Input	Output
000	
001	
010	
011	
100	
101	
110	
111	

This ROM
corresponds to this
truth table

 


8-entry 4-bit ROM

Poll: What's the formula for size of ROM needed?

Input	Output
000	1001
001	0100
010	0010
011	1001
100	0010
101	0001
110	1000
111	0000

This ROM corresponds to this truth table

 

Aside: Other Memories


- Static RAM (random access memory)
 - Built from sequential circuits
 - Takes 4-6 transistors to store 1 bit
 - Fast access (< 1 ns access possible)
- Dynamic RAM
 - Built using a single transistor and a capacitor
 - 1's must be refreshed often to retain value
 - Slower access than static RAM
 - Much more dense layout than static RAM
- Both require constant power, or they will lose their data (i.e. are **volatile**)
- These will be used to build computer memory hierarchies (later in class)



Implementing Combinational Logic

- Custom logic
 - Pros:
 - Can optimize the number of gates used
 - Cons:
 - Can be expensive / time consuming to make custom logic circuits
- Lookup table:
 - Pros:
 - Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly
 - Cons:
 - Size requirement grows exponentially with number of inputs (adding one just more bit **doubles** the storage requirements!)

Controller Design So far

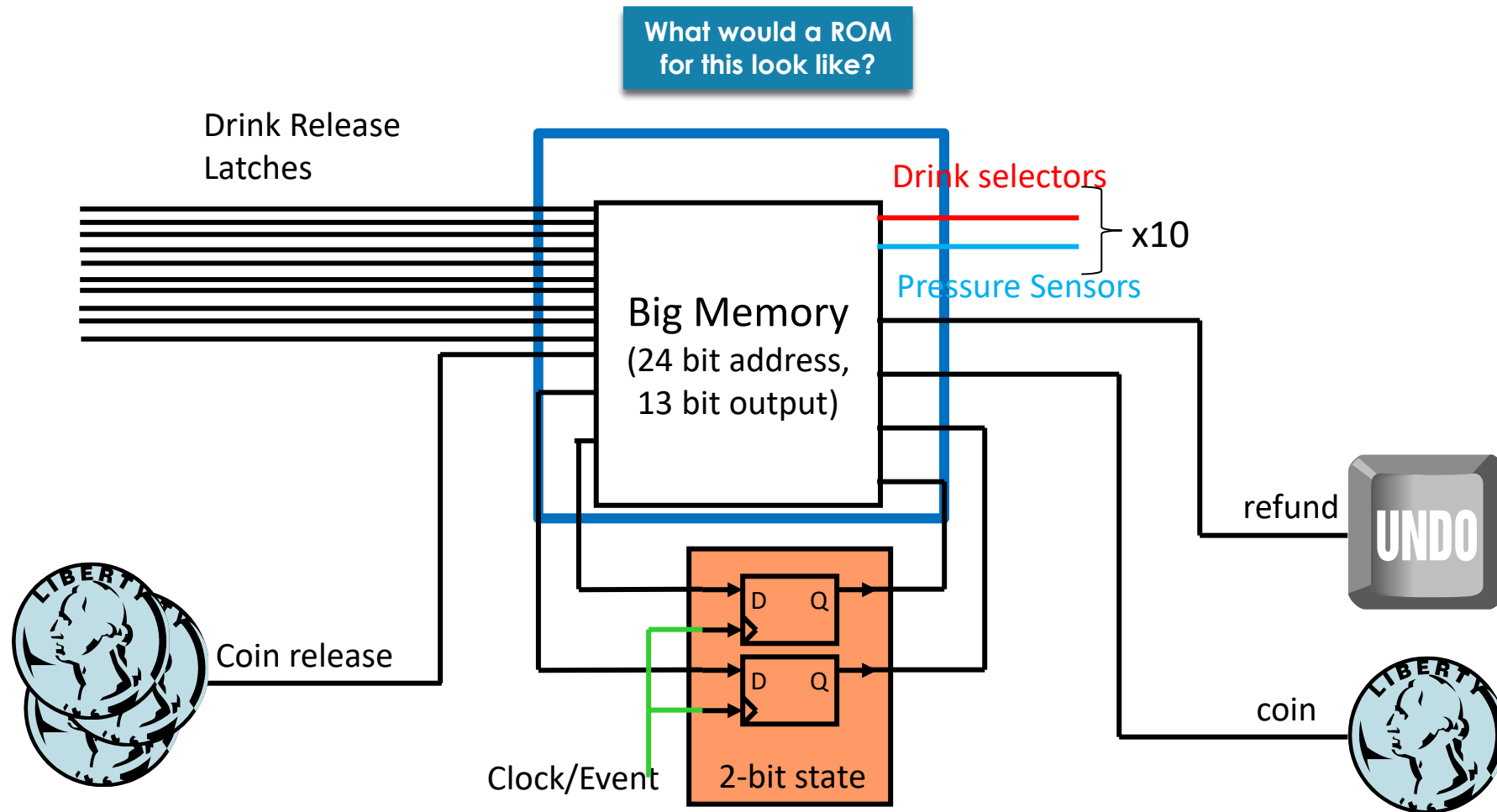

ROM for Vending Machine

Size of ROM is (# of ROM entries * size of each entry)

- # of ROM entries = $2^{\text{input_size}} = 2^{24}$
- Size of each entry = output size = 13 bits


We need 2^{24} entry, 13 bit ROM memories

- **218,103,808 bits of ROM (26 MB)**
- Biggest ROM I could find on Jameco was 4 MB @ \$6
 - Need 7 of these at \$42??
- Let's see if we can do better

Reducing the ROM needed

- Idea: let's do a hybrid between combinational logic and a lookup table
 - Use basic hardware (AND / OR) gates where we can, and a ROM for everything more complicated
 - AND / OR gates are mass producible & cheap!
 - ~\$0.15 each on Jameco

IC 74HC08 QUAD 2-INPUT POSITIVE AND GATE

 

[View larger image](#)

Jameco Part no.: 45225
Manufacturer: [Major Brands](#)
Manufacturer p/n: 74HC08
HTS code: 8542390000
[Fairchild Semiconductors](#) [83 KB]
[Data Sheet \(current\)](#) [83 KB]
Representative Datasheet, MFG may vary

\$0.49 ea

1,061 In Stock
More Available - 7 weeks

Qty

1


Add to cart

[+ Add to my favorites](#)

Reducing the ROM needed

- Observation: overall logic doesn't really need to distinguish between **which** button was pressed
 - That's only relevant for choosing **which** latch is released, but overall logic is the same
- Replace 10 selector inputs and 10 pressure inputs with a **single** bit input (drink selected)
 - Use drink selection input to specify which drink release latch to activate
 - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)


Putting it all together

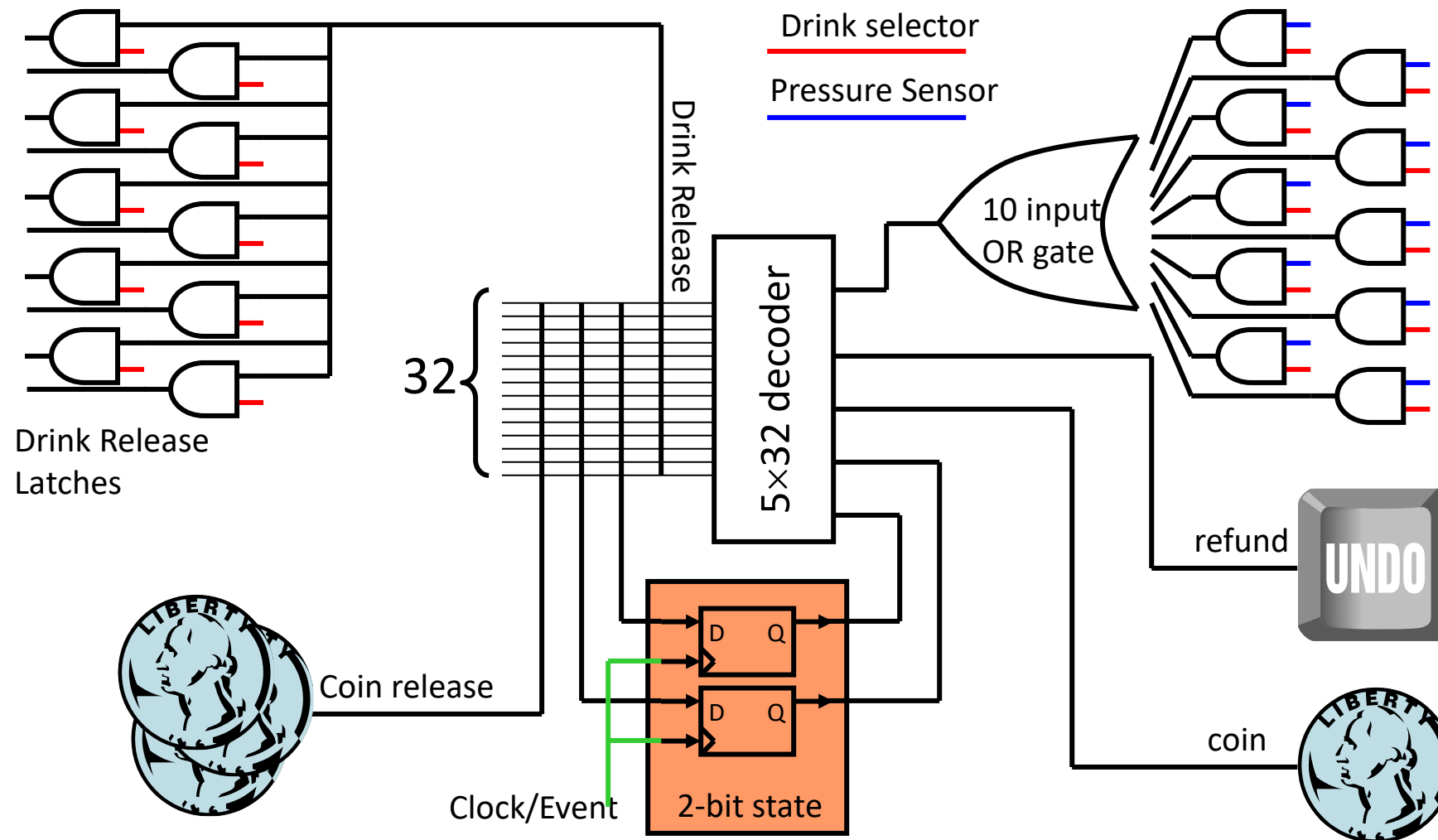

Total cost of our controller

- Now:
 - 2 current state bits + 3 input bits (5 bit ROM address)
 - 2 next state bits + 2 control trigger bits (4 bit memory)
 - $2^5 \times 4 = 128$ bit ROM
 - 1-millionth size of our 26 MB ROM 😬
- Total cost on Jameco:
 - Flip-flops to store state: \$3
 - ROM to implement logic: \$3
 - AND/OR gates: \$5
 - **Total: \$11**
- Could probably do a lot cheaper if we buy in bulk


Can we design LC2K Processor as FSM?

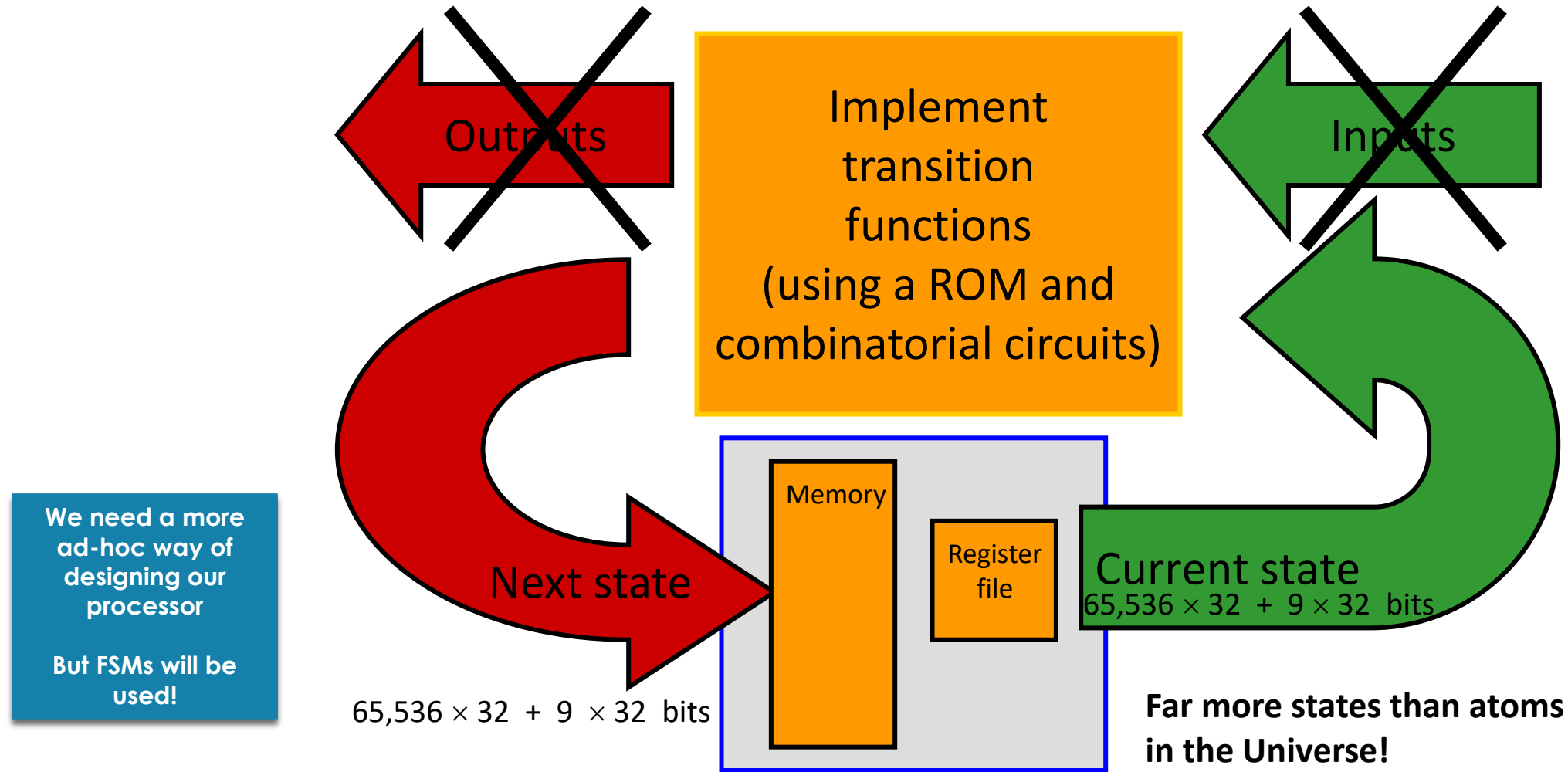


Single-Cycle Processor Design

- General-Purpose Processor Design
 - Fetch Instructions
 - Decode Instructions
 - Instructions are input to control ROM
 - ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
 - Clock drives it all
 - Single-cycle datapath: Each instruction completes in one clock cycle

LC2K Datapath Implementation

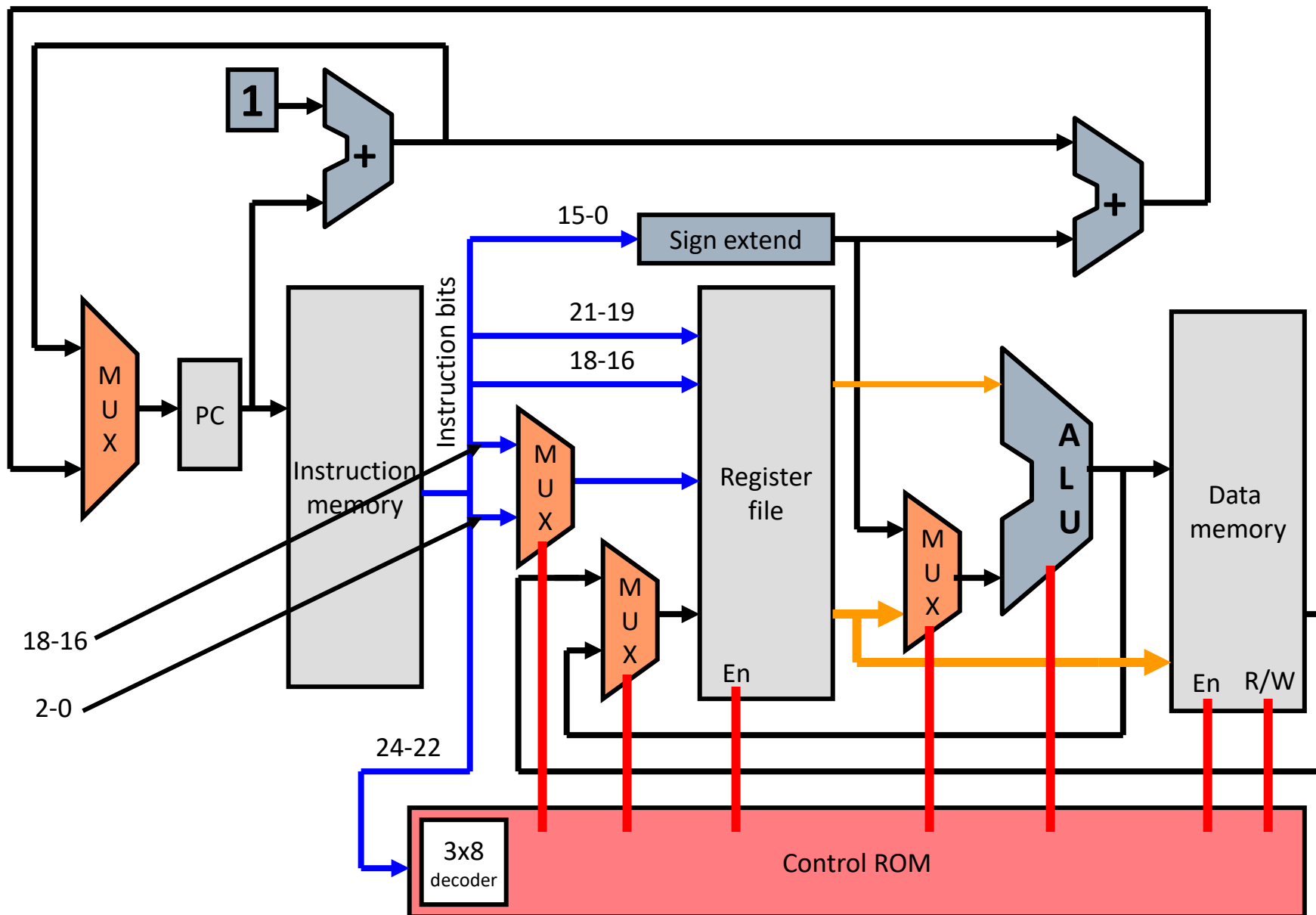


Building Blocks for the LC2K

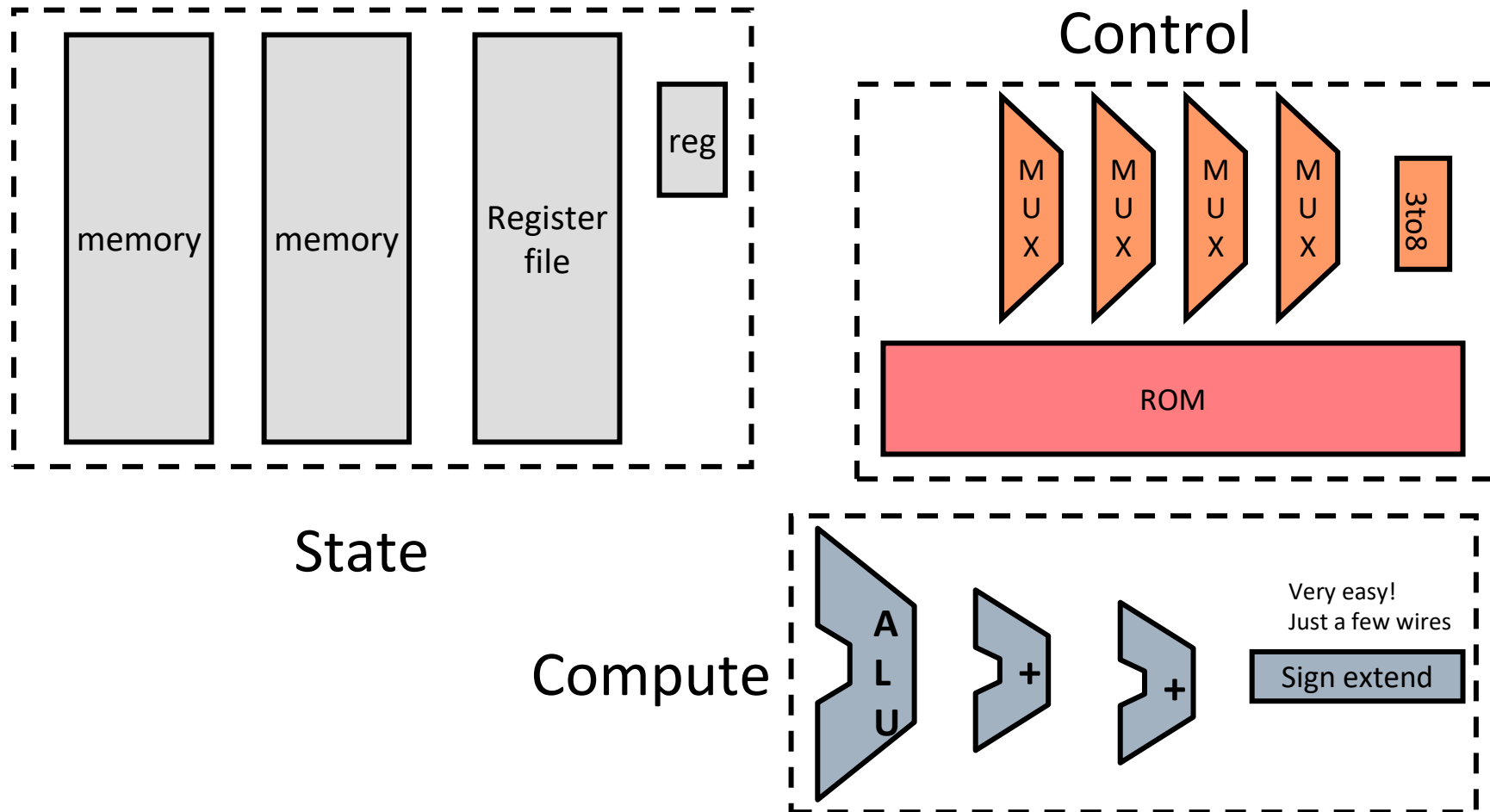

Here are the pieces, go build yourself a processor!


Control Building Blocks (1)

 

Connect one of the inputs to OUT based on the value of select

If (! select)
 OUT = IN1
Else
 OUT = IN2

Control Building Blocks (2)

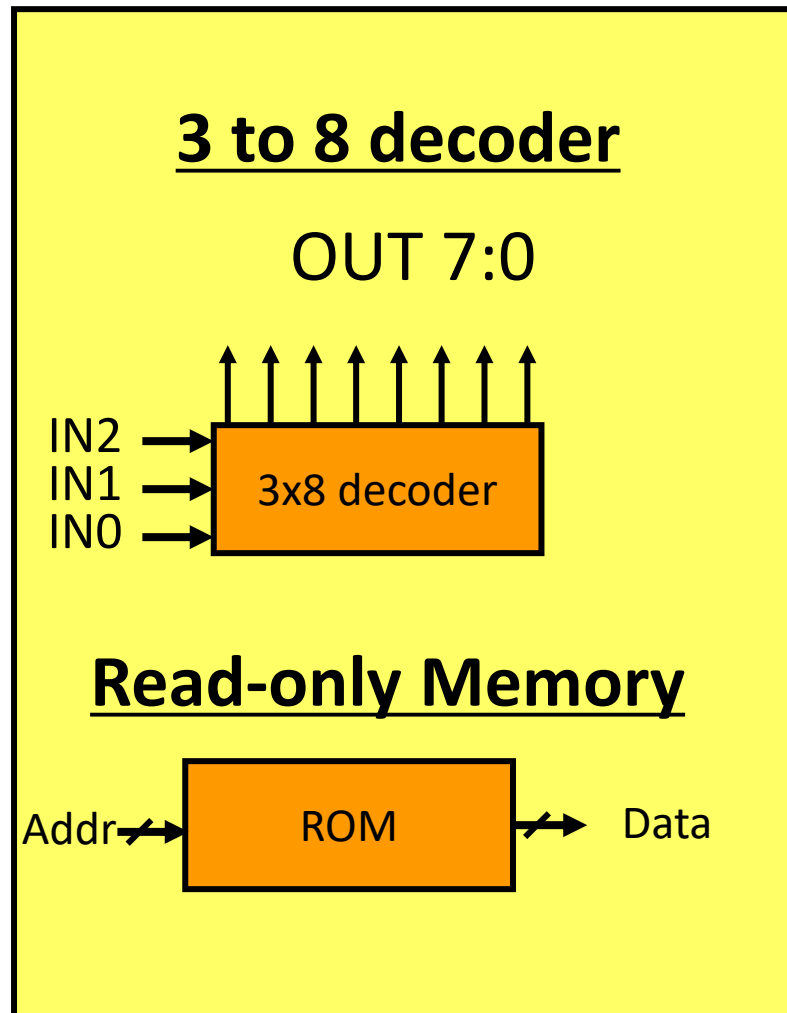


Decoder activates one of the output lines based on the input

IN	OUT
<u>210</u>	<u>76543210</u>
000	00000001
001	00000010
010	00000100
011	00001000
etc.	

ROM stores preset data in each location

- Give address, get data.

Compute Building Blocks (1)

 

Perform basic arithmetic functions

$$\text{OUT} = f(\text{IN1}, \text{IN2})$$

$$\text{EQ} = (\text{IN1} == \text{IN2})$$

For LC2K:


f=0 is add

f=1 is nor

For other processors, there are many more functions.

Just adds

Compute Building Blocks (2)

 

Sign extend (SE) input by replicating the MSB to width of output


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

State Building Blocks (1)

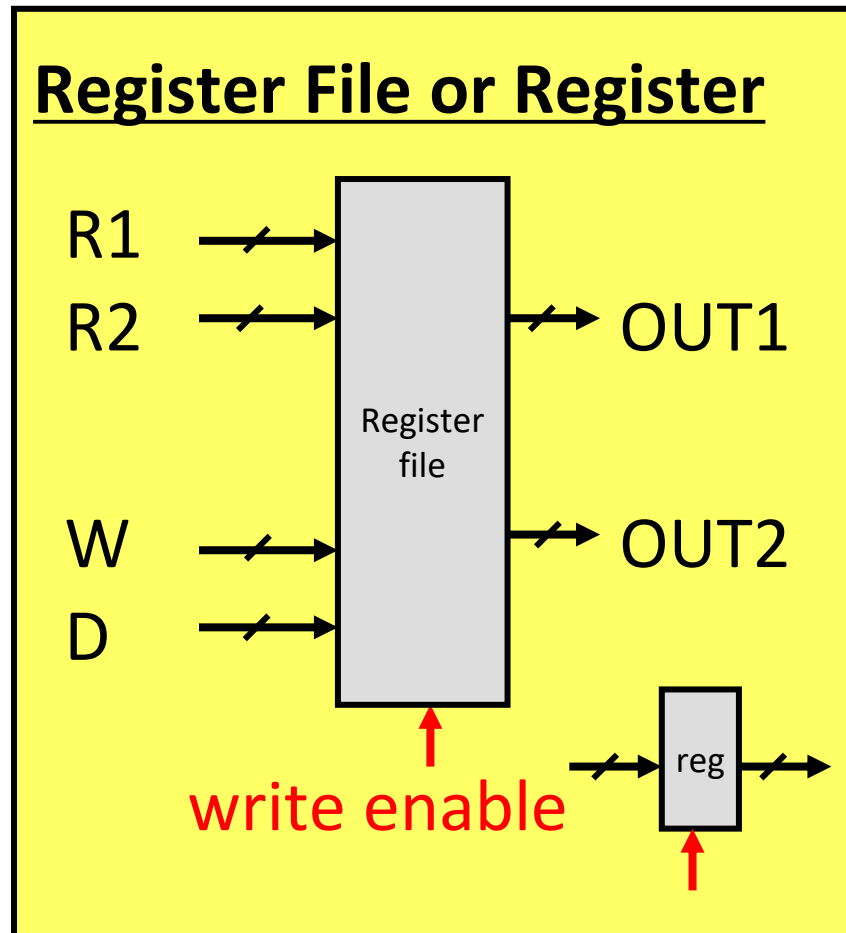

Small/fast memory to store temporary values

n entries (LC2 = 8)

r read ports (LC2 = 2)

w write ports (LC2 = 1)


* R_i specifies register number to read

* W specifies register number to write

* D specifies data to write

Poll: How many bits are R_i and W in LC2K?

State Building Blocks (2)

 


Slower storage structure to hold large amounts of stuff.

Use 2 memories for LC2K


- * Instructions
- * Data
- * 65,536 total words

Recap: LC2K Instruction Formats

 
- Tells you which bit positions mean what
- R type instructions (add '000', nor '001')



 
- I type instructions (lw '010', sw '011', beq '100')




LC2K Datapath Implementation

 

Executing an **ADD** Instruction

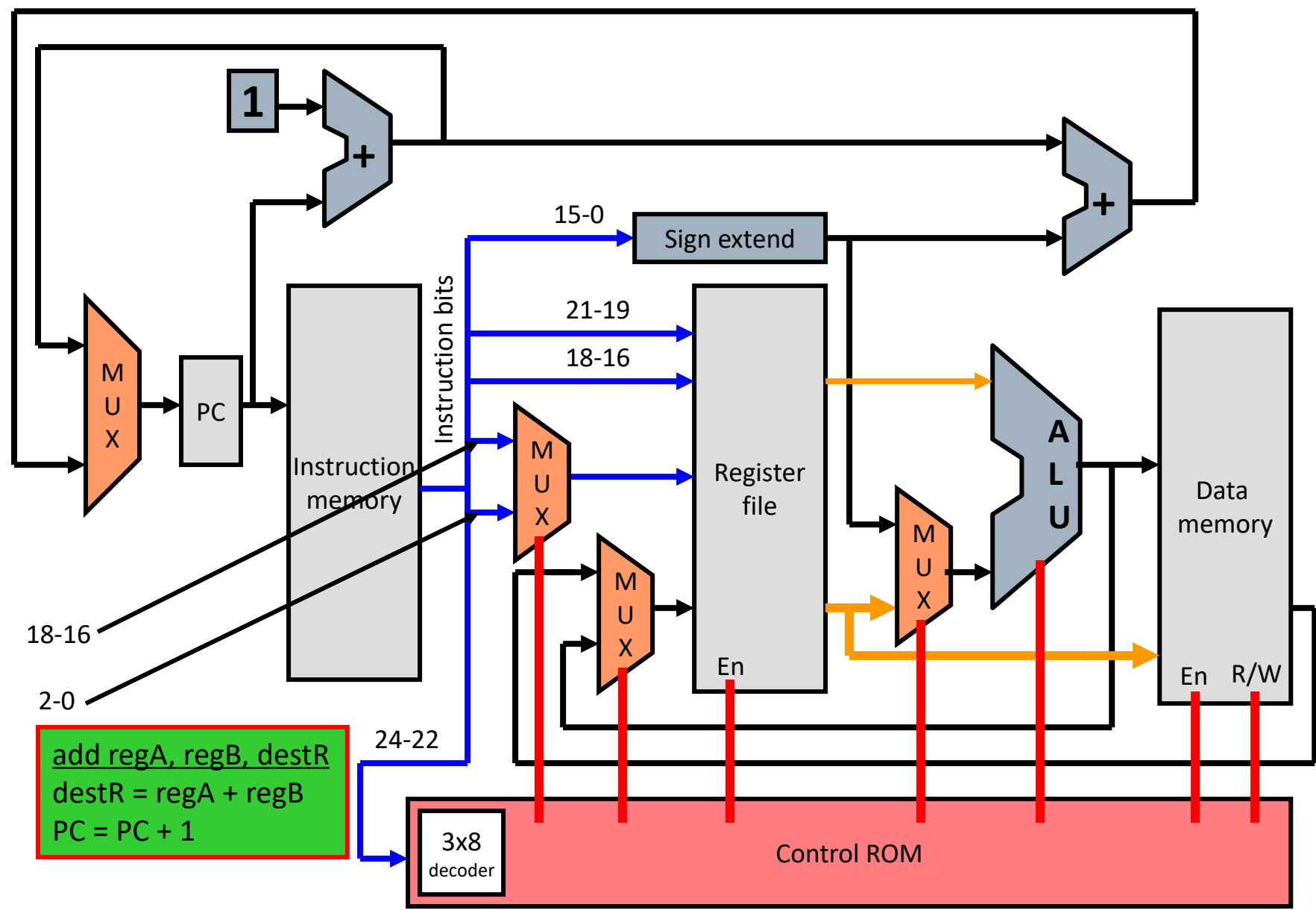

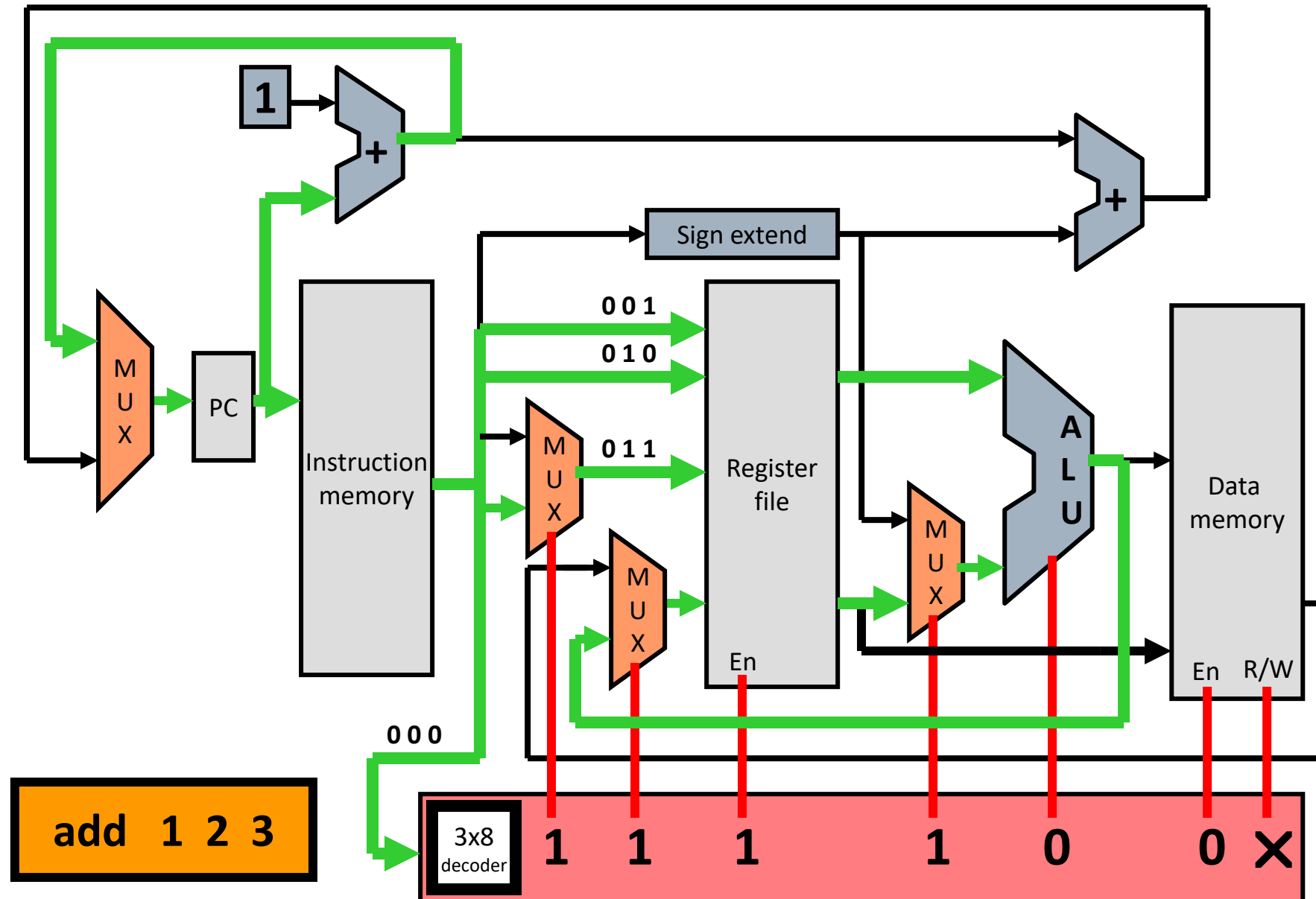Executing an **ADD** Instruction on LC2K Datapath




Next Time

- Finish up single-cycle and talk about multi-cycle
- Lingering questions / feedback? I'll include an anonymous form at the end of every lecture: <https://bit.ly/3oXr4Ah>




Executing a NOR Instruction

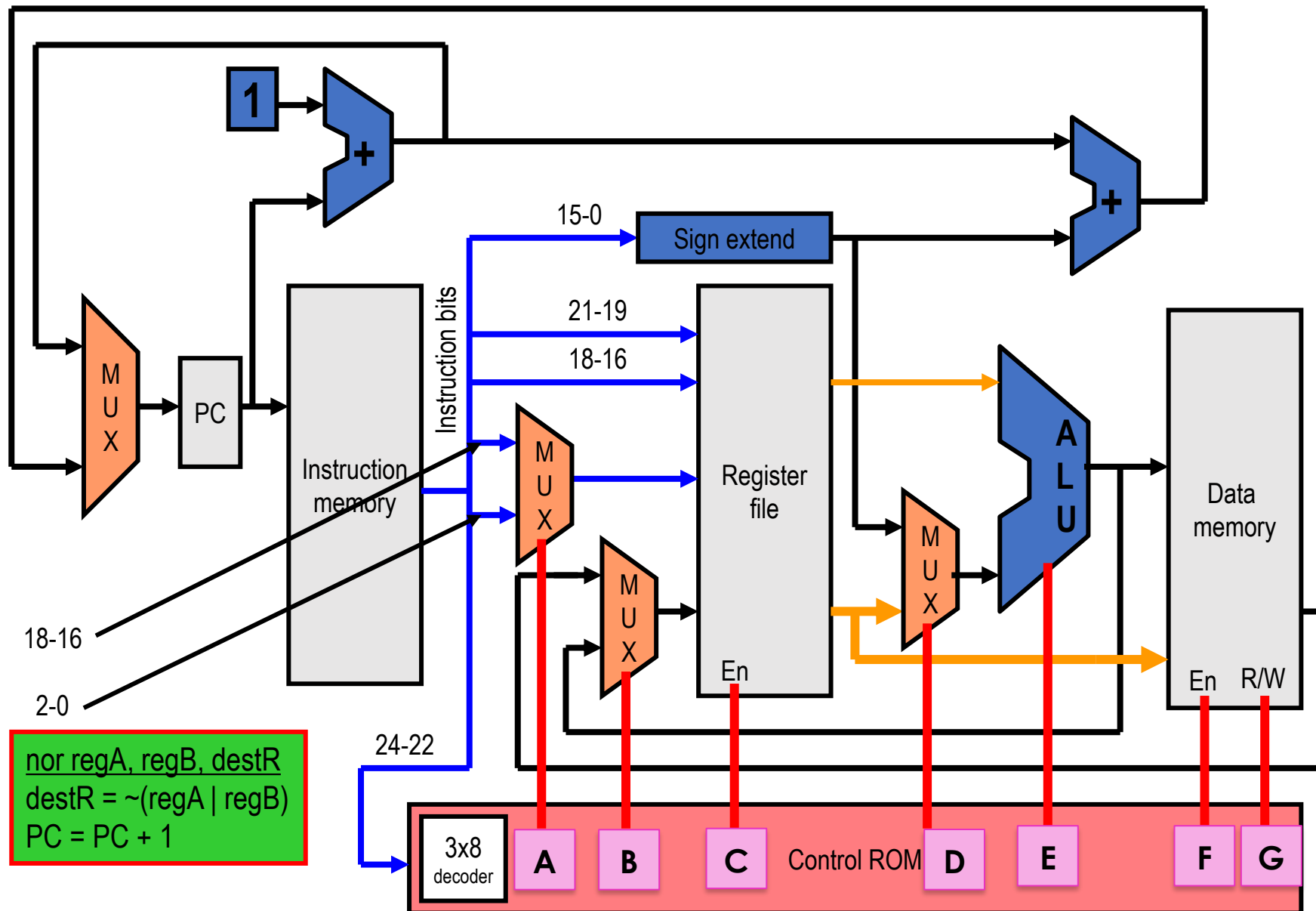Poll: Which control bits need to be different from ADD?




```
nor regA, regB, destR
destR = ~(regA | regB)
PC = PC + 1
```


Executing **NOR** Instruction on LC2K

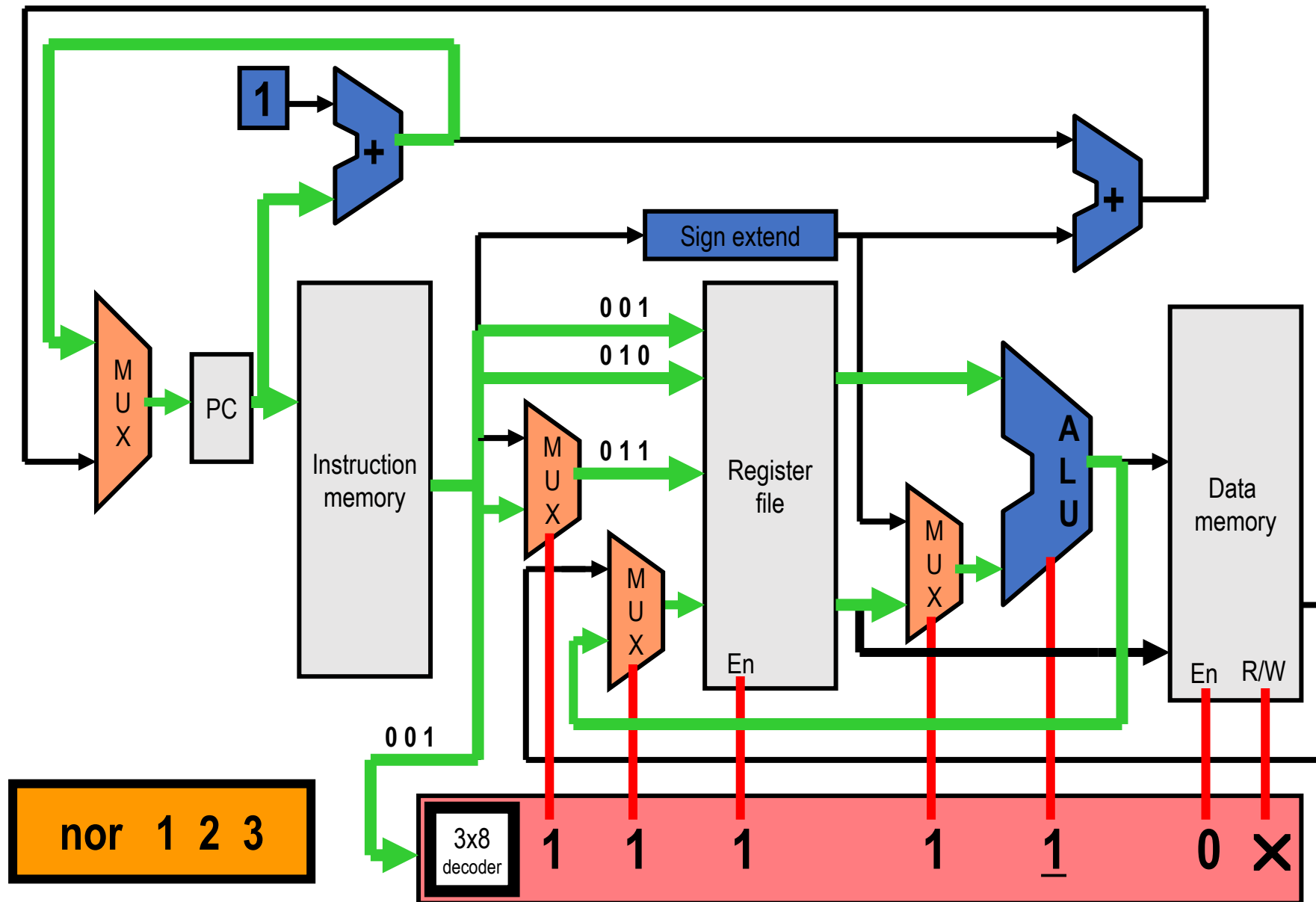


Executing a **LW** Instruction

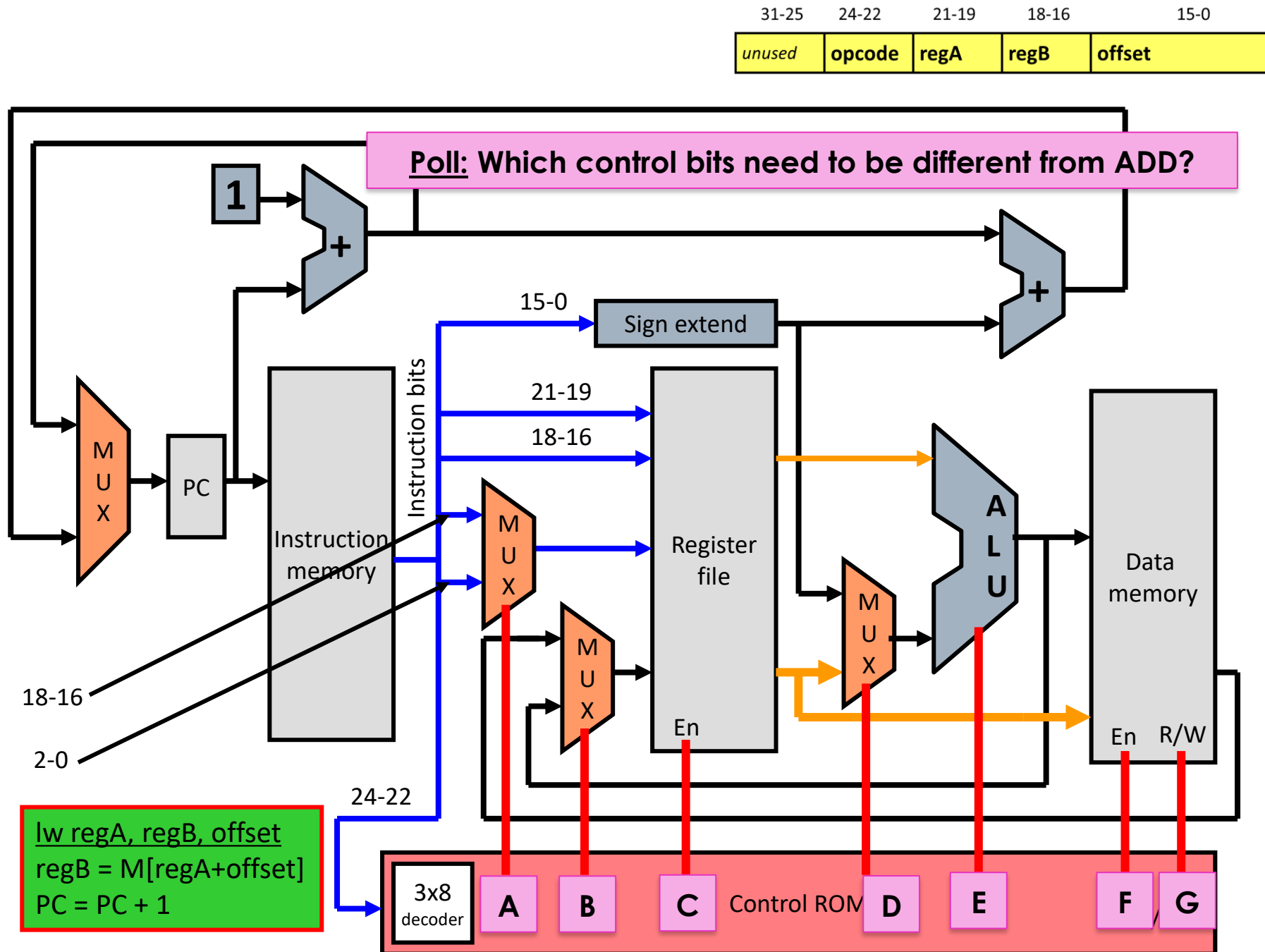

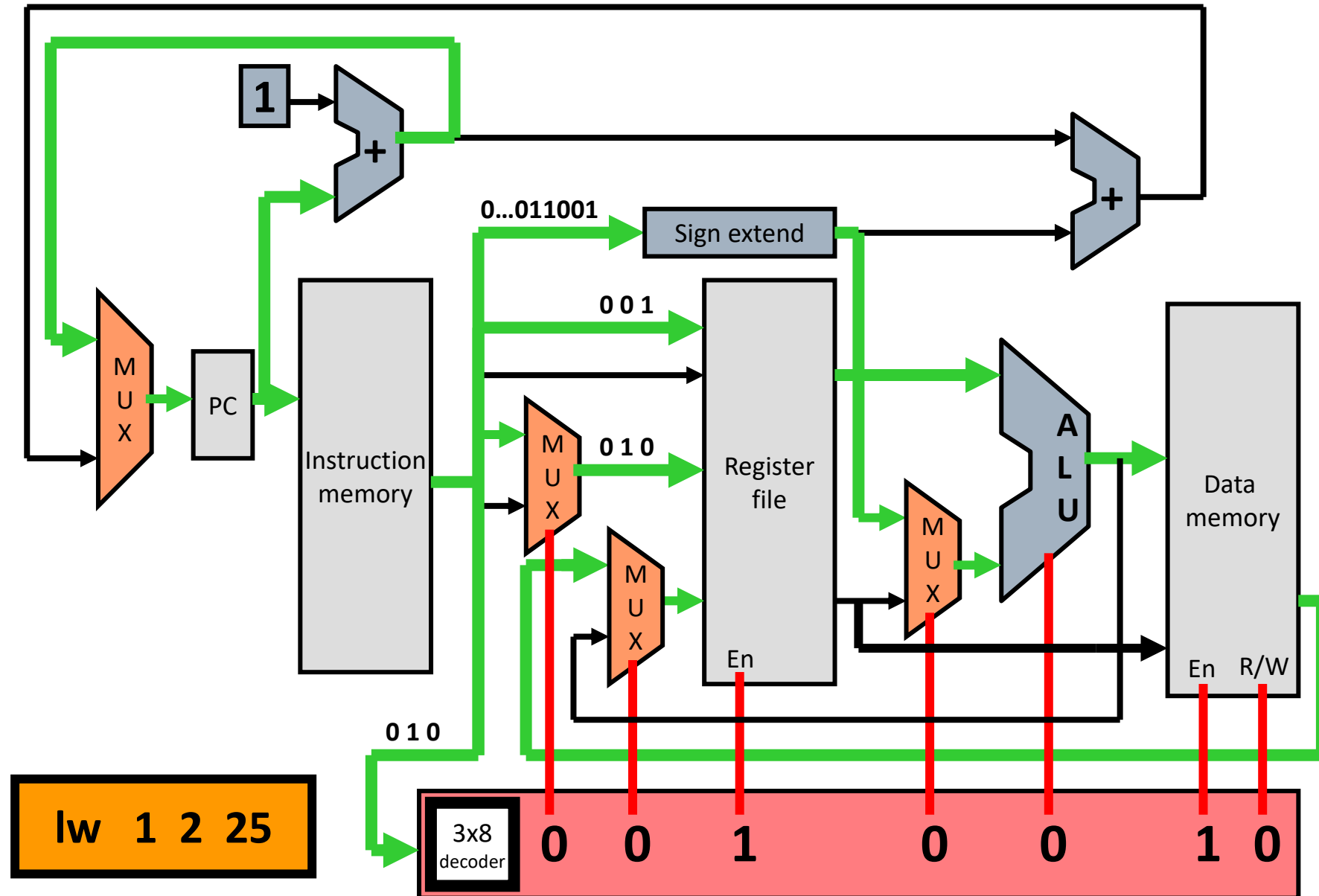Executing a **LW** Instruction on LC2Kx Datapath



Executing a **SW** Instruction

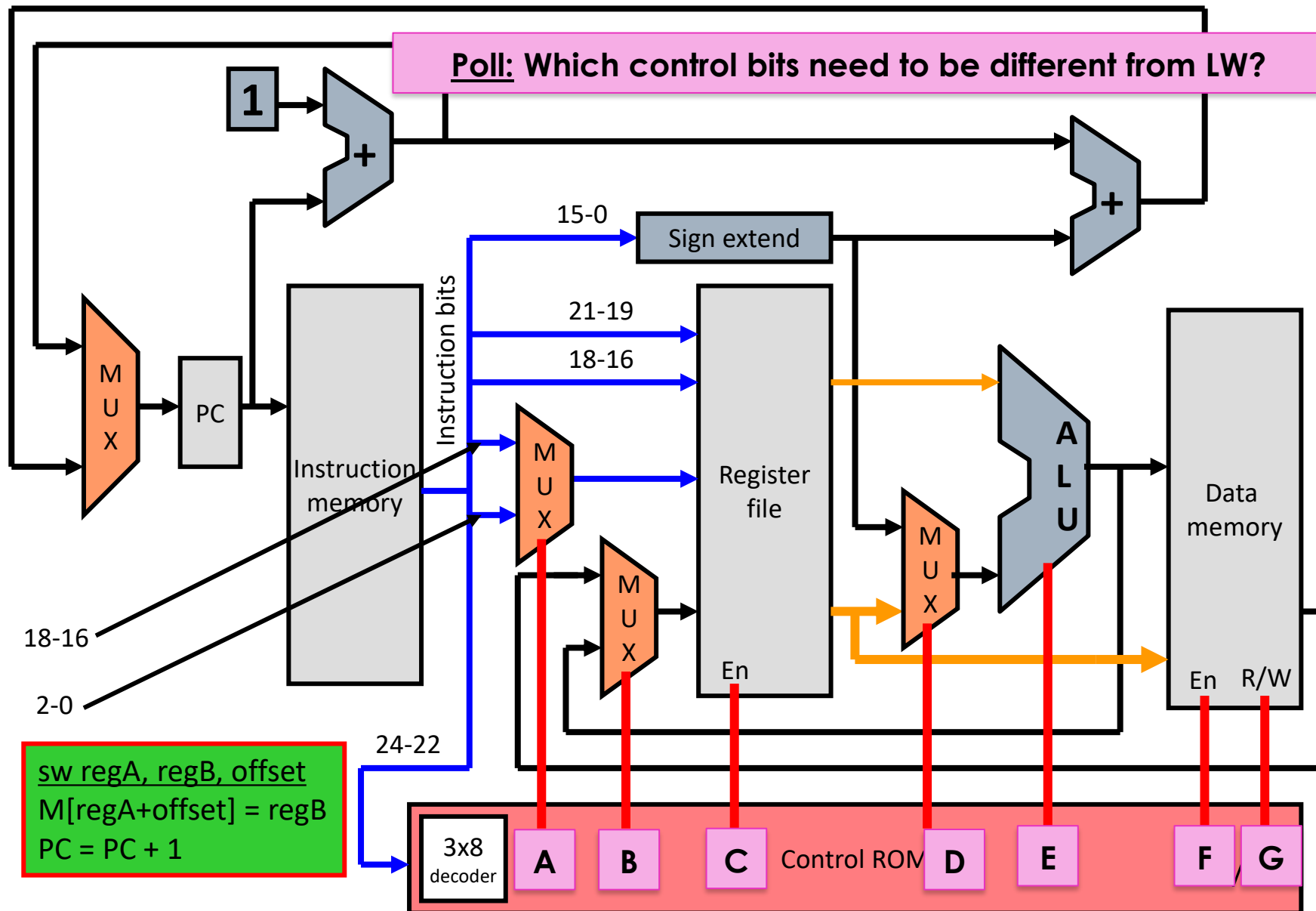

Executing a **SW** Instruction on LC2Kx Datapath

