

EECS 370 - Lecture 8

Combinational Logic



Announcements



Floating Point Arithmetic

See end of slides for
bonus material (not
covered in HW or
exams)




Why floating point

- Have to represent real numbers somehow
- Rational numbers
 - Ok, but can be cumbersome to work with
- Fixed point
 - Do everything in thousandths (or millionths, etc.)
 - Not always easy to pick the right units
 - Different scaling factors for different stages of computation
- **Scientific notation: this is good!**
 - Exponential notation allows HUGE dynamic range
 - Constant (approximately) relative precision across the whole range

IEEE Floating point format (single precision)

- Sign bit: (0 is positive, 1 is negative)
- Significand: (also called the *mantissa*; stores the 23 most significant bits after the decimal point)
- Exponent: used biased base 127 encoding
 - Add 127 to the value of the exponent to encode:
 - -127 → 00000000 1 → 10000000
 - -126 → 00000001 2 → 10000001
 -
 - 0 → 01111111 128 → 11111111
- How do you represent zero ? Special convention:
 - Exponent: -127 (all zeroes), Significand 0 (all zeroes), Sign + or -

 Some other exception cases (e.g. NaN) we won't cover




Floating Point Representation

$$10.625_{10} \Rightarrow 1010.101_2$$

- ❑ Step 1: convert from decimal to binary
 - 1st bit after "binary" point represents 0.5 (i.e. 2^{-1})
 - 2nd bit represents 0.25 (i.e. 2^{-2})
 - etc.



Floating Point Representation
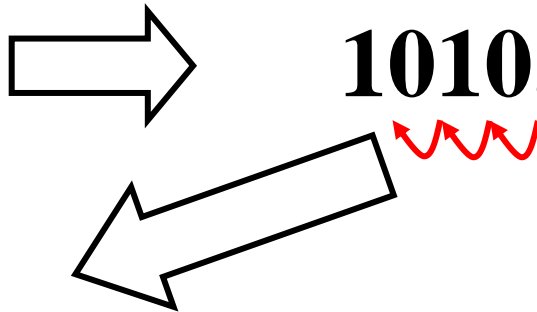
$$10.625_{10} \quad \Rightarrow \quad 1010.101_2$$


$$1.010101 \times 2^3$$

- Step 2: normalize number by shifting binary point until you get $1.XXX \times 2^Y$

Floating Point Representation

$$10.625_{10} \longrightarrow 1010.101_2$$

$$1.010101 \times 2^3$$

This must be a 1!
So don't store it.




- Step 3: store relevant numbers in proper location (ignoring initial 1 of significand)

Floating Point Representation

$$10.625_{10} \longrightarrow 1010.101_2$$

$$1.010101 \times 2^3$$

This must be a 1!
So don't store it.

 

$$10.625_{10} = 0 \ 10000010 \ 010101000000000000000000$$

Class Problem

Poll

- What is the value of the following IEEE 754 floating point encoded number?

1 **10000101** **010110010000000000000000**

```
1 = -  
10000101 = 133 - 127 -> exponent 6  
01011001 = mantissa  
  
-1.01011001 x 2^6  
  
-1010110.01  
-(2^6+2^4+2^2+2^1+2^-2)  
-(64+16+4+2+1/4)  
  
-86.25
```


What matters to a CS person?

- When you are adding small numbers to big numbers, the result may not change
 - E.g. $1.00 \times 10^3 + 1.00 \times 10^1 = 1000 + 1 = 1.00 \times 10^3$
- This can be a real problem when writing scientific code.
 - For the above example, imagine you did that addition a million times
 - You'd still have 1000 when the answer should be 1,001,000
- So you need to be aware of the issue.
 - This is why most people use “double” instead of “float”
 - The problem can still exist, it's just less likely.

More precision and range

- We've described IEEE-754 binary32 floating point format, i.e. “single precision” (“float” in C/C++)
 - 24 bits precision; equivalent to about 7 decimal digits
 - $3.4 * 10^{38}$ maximum value
 - Good enough for most but not all calculations
- IEEE-754 also defines larger binary64 format, “double precision” (“double” in C/C++)
 - 53 bits precision, equivalent to about 16 decimal digits
 - $1.8 * 10^{308}$ maximum value
 - Most accurate physical values currently known only to about 47 bits precision, about 14 decimal digits

Single (“float”) precision

 

Next few lectures: Digital Logic

- Lectures 1-7:
 - LC2K and ARMv8/LEGV8 ISAs
 - Converting C to Assembly
 - Function Calls
 - Linking
- **Today:**
 - **Floating Point**
 - **Combinational Logic**
- Next lecture:
 - Sequential Logic



Up Until Now...

- We've covered high-level C code to an executable
 - Compilation
 - Assembly
 - Linking
 - Loading
- Now, we'll talk about the hardware that runs this code
 - First step: the basics of digital logic

Next 3 Lectures

1. Combinational Logic:

- Basics of electronics; logic gates, muxes, decoders

2. Sequential Logic


- Clocks, latches and flip-flops

3. State Machines


- Building a simple processor

Transistors

 - ❑ At the heart of digital logic is the transistor
- ❑ Electrical engineers draw it like this



 - ❑ The physics is complicated, but at the end of the day, all it is a **really** small and **really** fast electric switch





Basic gate: Inverter

CS abstraction
- logic function

Truth Table

I	O
0	1
1	0

Schematic symbol (CS/EE)

  


We won't focus on
this part in 370. Take
270 and 312 to
learn more

Basic gates: AND and OR

AND

Truth Table


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

OR

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

Basic gate: NAND


Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


Bubble is symbolic for "invert", so this is equivalent to negating an AND gate

Transistor-level schematic

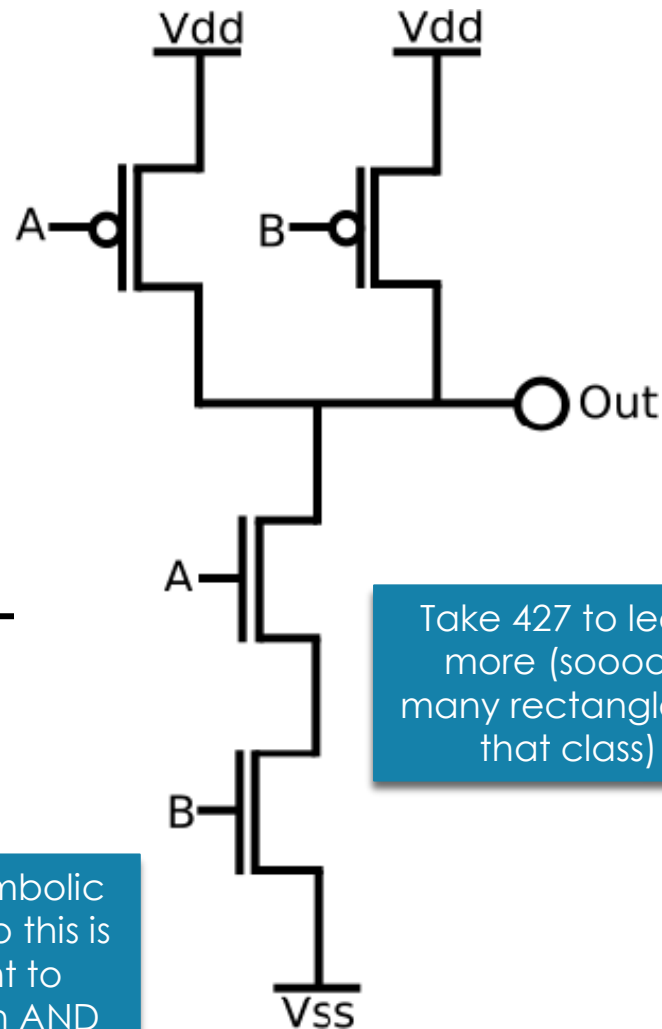

Take 427 to learn more (sooooo many rectangles in that class)


Layout schematic

 


Basic gate: XOR (eXclusive OR)

Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

 

 Poll: How do we fill in the truth table for XOR? XNOR?




Building Complexity: Selecting

- We want to design a circuit that can select between two inputs (multiplexer or **mux**)
- Let's do a one-bit version
 1. Draw a truth table

Poll: How do we fill in the truth table for this?

A	B	S	O
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Symbol

 

$$O = S ? B : A$$


Building Complexity: Selecting

- We want to design a circuit that can select between two inputs (multiplexor or **mux**)
- Let's do a one-bit version
 1. Draw a truth table


Muxes are universal! A 2^N entry truth table can be implemented by passing each output value into an input of a 2^N -to-1 mux

A	B	S	O
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Circuit

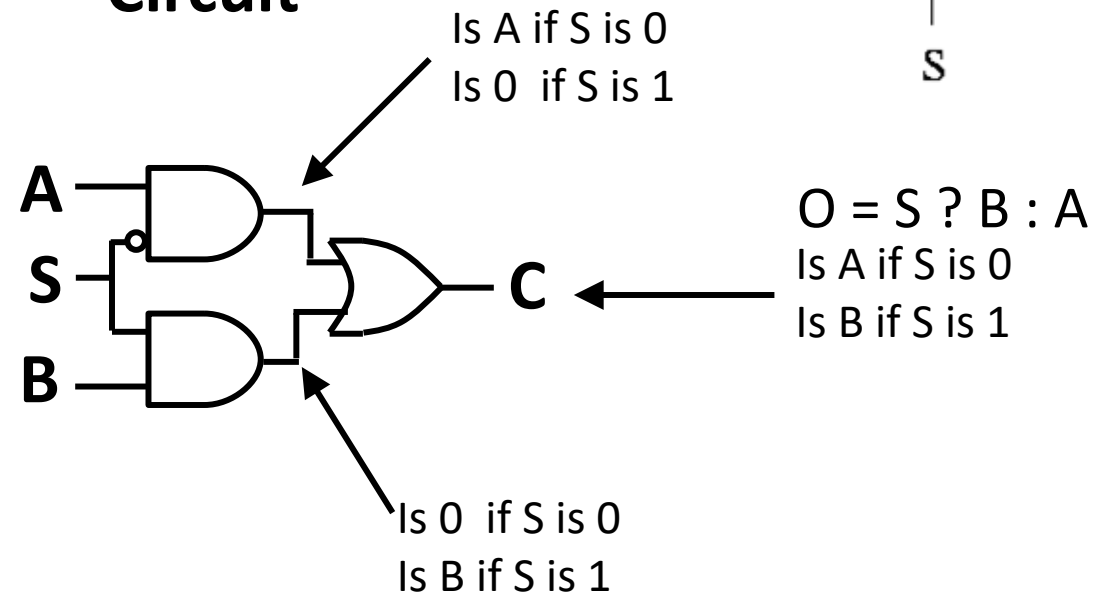

Symbol

 

Building Complexity: Addition

- We want to design a circuit that performs binary addition
- Let's start by adding two bits
 - Design a circuit that takes two bits (**A** and **B**) as input
 - Generates a sum and carry bit (S and C)
 1. Make a truth table
 2. Design a circuit


$$\begin{array}{r} 10011 \\ + 00110 \\ \hline \end{array}$$

A	B	C	S

Building Complexity: Addition

- We want to design a circuit that performs binary addition
- Let's start by adding two bits
 - Design a circuit that takes two bits (**A** and **B**) as input
 - Generates a sum and carry bit (S and C)
 - 1. Make a truth table
 - 2. Design a circuit

 
$$\begin{array}{r} 0\ 1\ 1\ 0 \\ 1\ 0\ 0\ 1\ 1 \\ + 0\ 0\ 1\ 1\ 0 \\ \hline 1\ 1\ 0\ 0\ 1 \end{array}$$



A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Building Complexity: Addition

 - Now we can add two bits, but how do we deal with carry bits?
- This is a **full adder**
 - We have to design a circuit that can add three bits
 - Inputs: A, B, C_{in}
 - Outputs: S, C_{out}
- 1. Design a truth table
- 2. Circuit
- This is a **full adder**




$$\begin{array}{r} 0110 \\ 10011 \\ + 00110 \\ \hline 11001 \end{array}$$

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

8-bit Ripple Carry Adder

 If we invert B's bits and set C to 1, we also have a subtractor! Why?




This will be very slow for 32 or 64 bit adds, but is sufficient for our needs

Building Complexity: Decoding

- Another common device is a decoder
 - Input: N-bit binary number
 - Output: 2^N bits, exactly one of which will be high
 - Allows us to **index** into things (like a register file)


Decoder

 


Poll: What will be the output for 101?

Propagation delay in combinational gates

 - Gate outputs do not change exactly when inputs do.
 - Transmission time over wires (\sim speed of light)
 - Saturation time to make transistor gate switch
- ⇒ Every combinatorial circuit has a propagation delay
(time between input and output stabilization)



Timing in Combinational Circuits

 


What is the input/output delay (or simply, delay) of the MUX?

What is the delay of this Circuit?

Each oval represents one gate,
the type does not matter



Poll : What is the delay?

 

We only care about the longest
path, or critical path

  
Exercise

- Use the blocks we have learned about so far (full adder, NOR, mux) to build this circuit
 - Input A, 32 bits
 - Input B, 32 bits
 - Input S, 1 bit
 - Output, 32 bits
 - When S is low, the output is $A+B$, when S is high, the output is $\text{NOR}(a,b)$
- Hint: you can express multi-bit gates like this:



 Exercise

- This is a basic ALU (Arithmetic Logic Unit)
- It is the heart of a computer processor!



Next Time

- Logic circuits that "remember"
 - Aka "sequential logic"
- Lingering questions / feedback? I'll include an anonymous form at the end of every lecture: <https://bit.ly/3oXr4Ah>



BONUS Floating Point Slides

Not
testable

Bonus slides – this material is not testable

- This material is here for those folks that may care.
 - **You *may* find it useful when considering the gap between representations**
 - But the material isn't directly testable.
- It is interesting if you are into that kind of thing.
- It can be useful if you are going to do scientific programming for a living.
- So it is provided as a reference, but isn't part of the class (we may cover a bit of it in lecture if we have time)

*Not
testable*

Floating point multiplication


- Add exponents (don't forget to account for the bias of 127)
- Multiply significands (don't forget the implicit **1** bits)
- Renormalize if necessary
- Compute sign bit (simple exclusive-or)

Floating point multiply

Not testable

$$10.625_{10} = 1010.101_2 \Rightarrow$$

$$10_{10} = 1010_2$$

 

0	10000010	010101000000000000000000
	+	×
0	10000010	010000000000000000000000
	-127	

$$\begin{array}{r}
 1010101 \\
 \times 101 \\
 \hline
 1010101 \\
 101010100 \\
 \hline
 110101001
 \end{array}$$

$$0 \ 10000101 \ 101010010000000000000000$$

$$1101010.01_2 = 106.25_{10}$$


*Not
testable*

Floating point addition

- More complicated than floating point multiplication!
- If exponents are unequal, must shift the significand of the smaller number to the right to align the corresponding place values
- Once numbers are aligned, simple addition (could be subtraction, if one of the numbers is negative)
- Renormalize (which could be messy if the numbers had opposite signs; for example, consider addition of $+1.5000$ and -1.4999)
- Added complication: rounding to the correct number of bits to store could denormalize the number, and require one more step

Floating point Addition

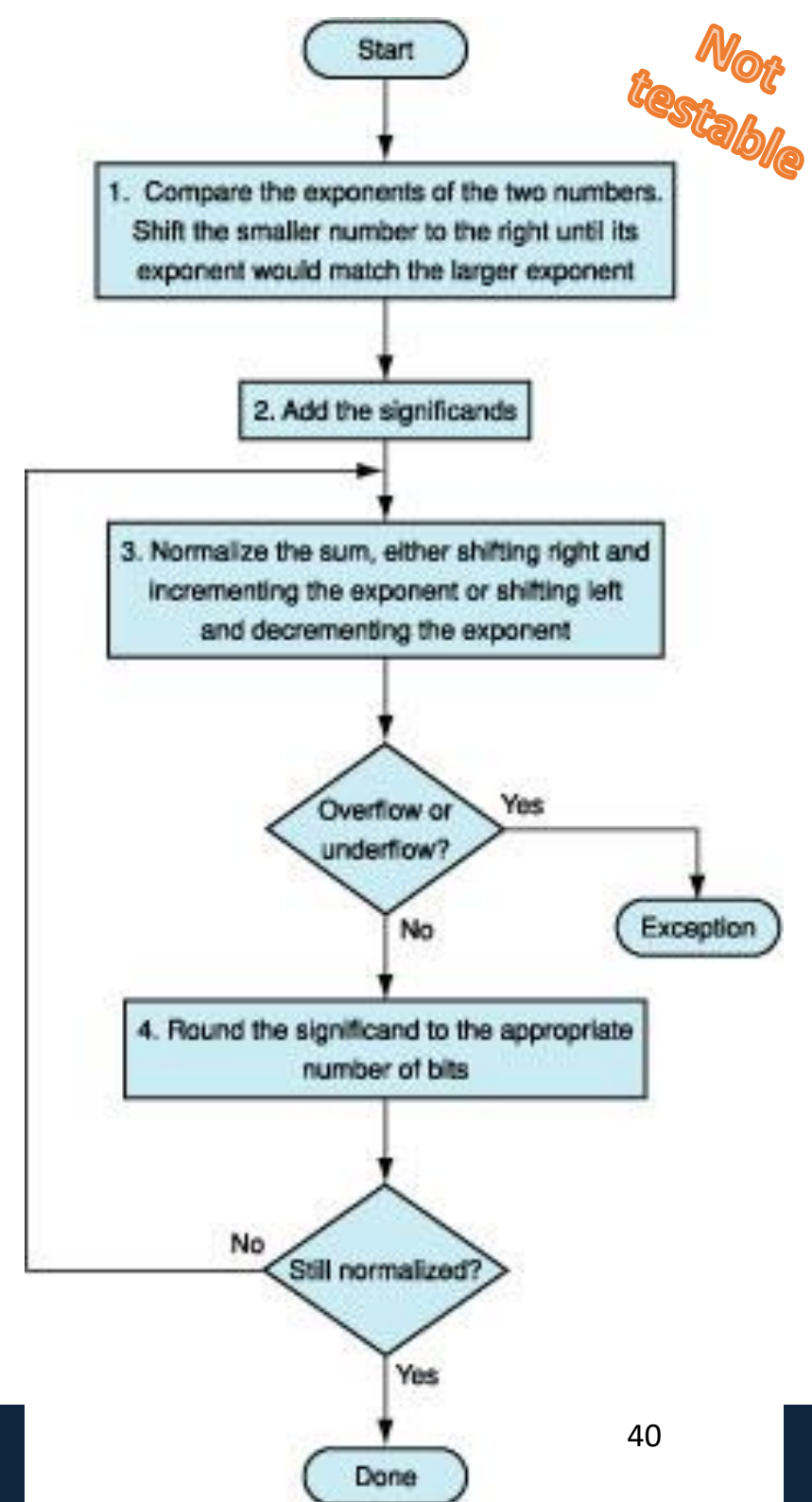1. Shift smaller exponent right to match larger.
2. Add significands
3. Normalize and update exponent
4. Check for “out of range”



*Not
testable*

Class Problem

Show how to add the following 2 numbers using IEEE floating point addition: $101.125 + 13.75$

Not testable

Class Problem


101.125

0 10000101 100101001000000000000000

13.75

0 10000010 101100000000000000000000

Shift by $6-3 = 3$

 

Shift mantissa by difference in exponent

001101100000000000000000

Note: When shifting to the right, the first shift should put the implicit 1, then 0's

Sum Significands

1 1 0 0 1 0 1 0 0 1
+ 0 0 0 1 1 0 1 1 1 0

1 1 1 0 0 1 0 1 1 1

Sum didn't overflow, so no re-normalization needed

0 10000101 110010110000000000000000

= 114.875

Class Problem

*Not
testable*

Show how to add the following 2 numbers using IEEE floating point addition: $117.125 + 13.75$

Not testable

Class Problem


117.125

0 10000101 110101001000000000000000

13.75

0 10000010 101110000000000000000000

Shift by $6-3 = 3$

 

Shift mantissa by difference in exponent

001101110000000000000000

Note: When shifting to the right, the first shift should put the implicit 1, then 0's

Sum Significands

1 1 1 0 1 0 1 0 0 1
+ 0 0 0 1 1 0 1 1 1 0

1 0 0 0 0 0 1 0 1 1 1

Sum overflows, re-normalize by adding one to exponent and shifting mantissa by one

0 10000110 0000010111000000000000

= 130.875