

11. Foundations of Processor Design: Multi-cycle Processors

EECS 370 – Introduction to Computer Organization – Winter 2023

**EECS Department
University of Michigan in Ann Arbor, USA**

What's on the schedule?

❑ P2a due Thursday 2/16

- If you didn't get full points on P1a, you'll need help.
See Piazza post @1247

❑ P2I due Thursday 2/23


- This is the harder one!

❑ HW3 due 2/20


Last time...

- ❑ We discussed the single-cycle processor.
- ❑ We walked through the various elements of the datapath
 - MUXes, adders, ALUs, memories, register files, and more.
- ❑ We looked at the way we'd implement the add, nor, beq, lw, and sw.
- ❑ Today we'll review the single-cycle processor and start on an improved version: the multi-cycle processor.
 - First, let's look back at the single-cycle datapath and the add instruction.


LC2K Datapath Implementation

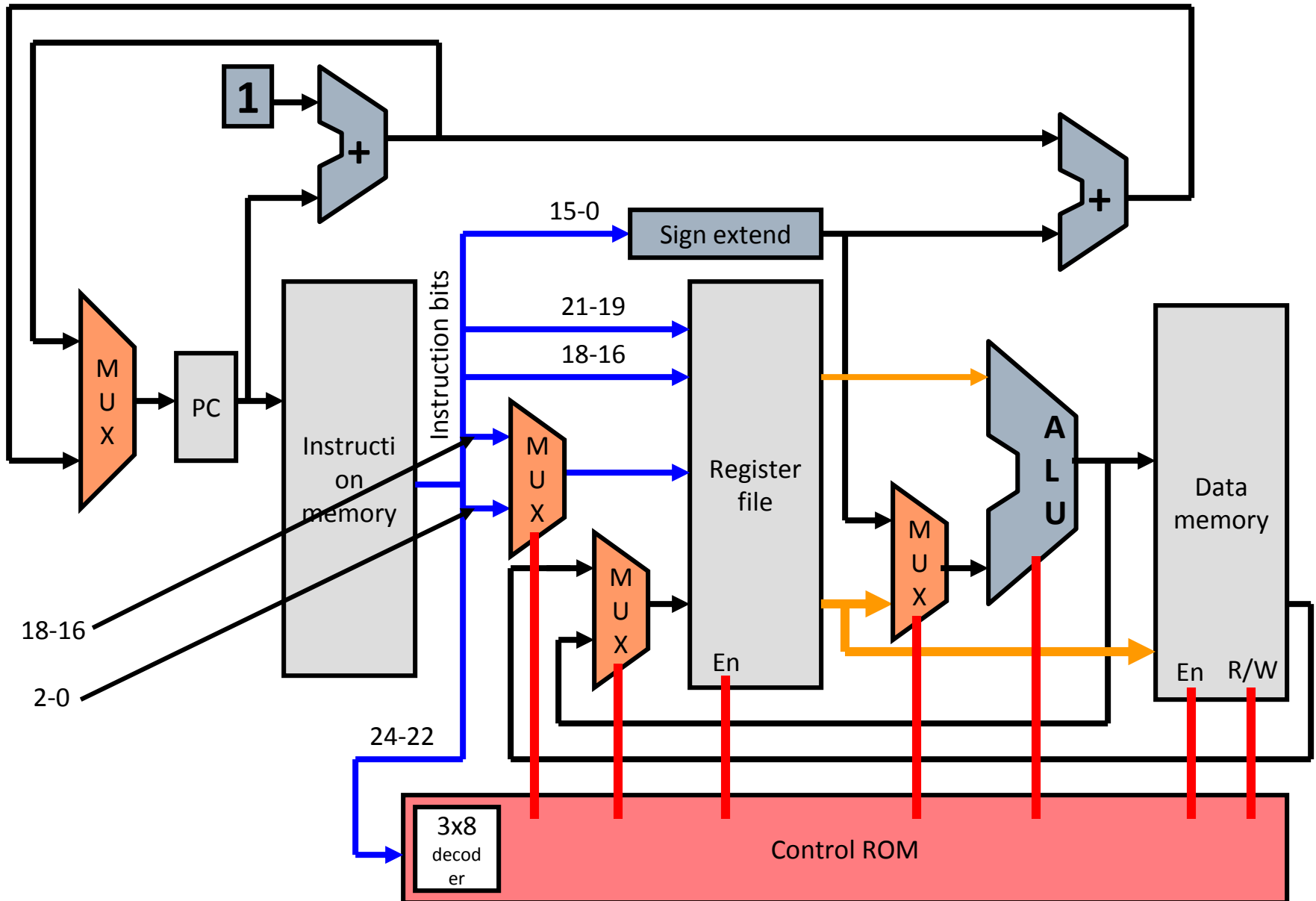

Executing an **ADD** Instruction

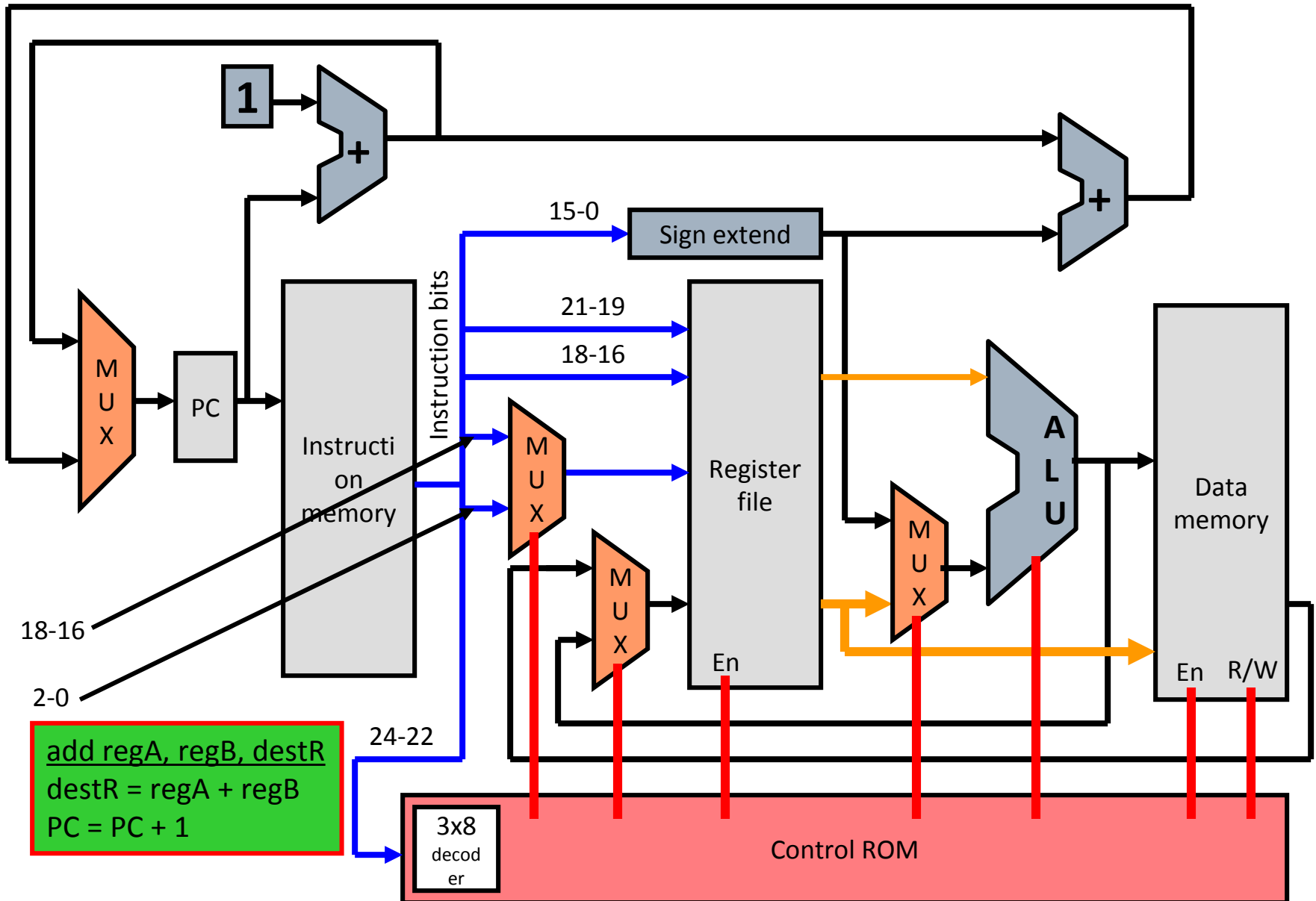

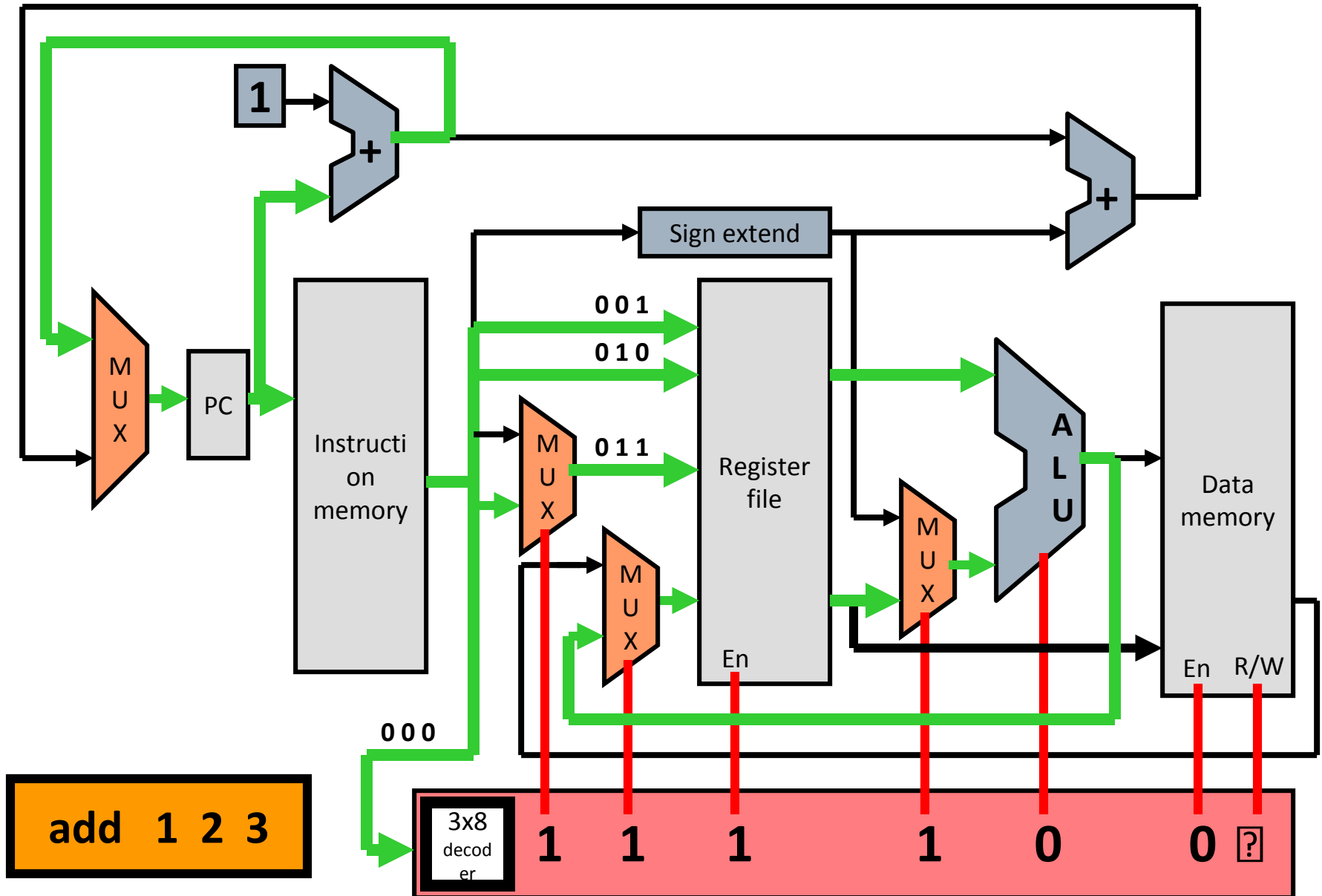Executing an **ADD** Instruction on LC2Kx Datapath



What's Wrong with Single Cycle?

- ❑ **All instructions run at the speed of the slowest instruction.**
- ❑ Adding a long instruction can hurt performance
 - What if you wanted to include multiply?
- ❑ You cannot reuse any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- ❑ No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

What's Wrong with Single Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,
10% of instructions are stores,
45% of instructions are adds, and
20% of instructions are branches.

Single-cycle execution:

??

Optimal execution:

??

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,
10% of instructions are stores,
45% of instructions are adds, and
20% of instructions are branches.

Single-cycle execution:


$$100 * 8\text{ns} = \underline{\mathbf{800}} \text{ ns}$$

Optimal execution:


$$25*8\text{ns} + 10*7\text{ns} + 45*6\text{ns} + 20*5\text{ns} = \underline{\mathbf{640}} \text{ ns}$$

Multiple-Cycle Execution


- ❑ Each instruction takes multiple cycles to execute
 - Cycle time is reduced
 - Slower instructions take more cycles
 - Can reuse datapath elements each cycle
- ❑ What is needed to make this work?
 - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
 - You may need extra registers if you need to remember an output for 1 or more cycles.
 - Control is more complicated since you need to send new signals on each cycle.

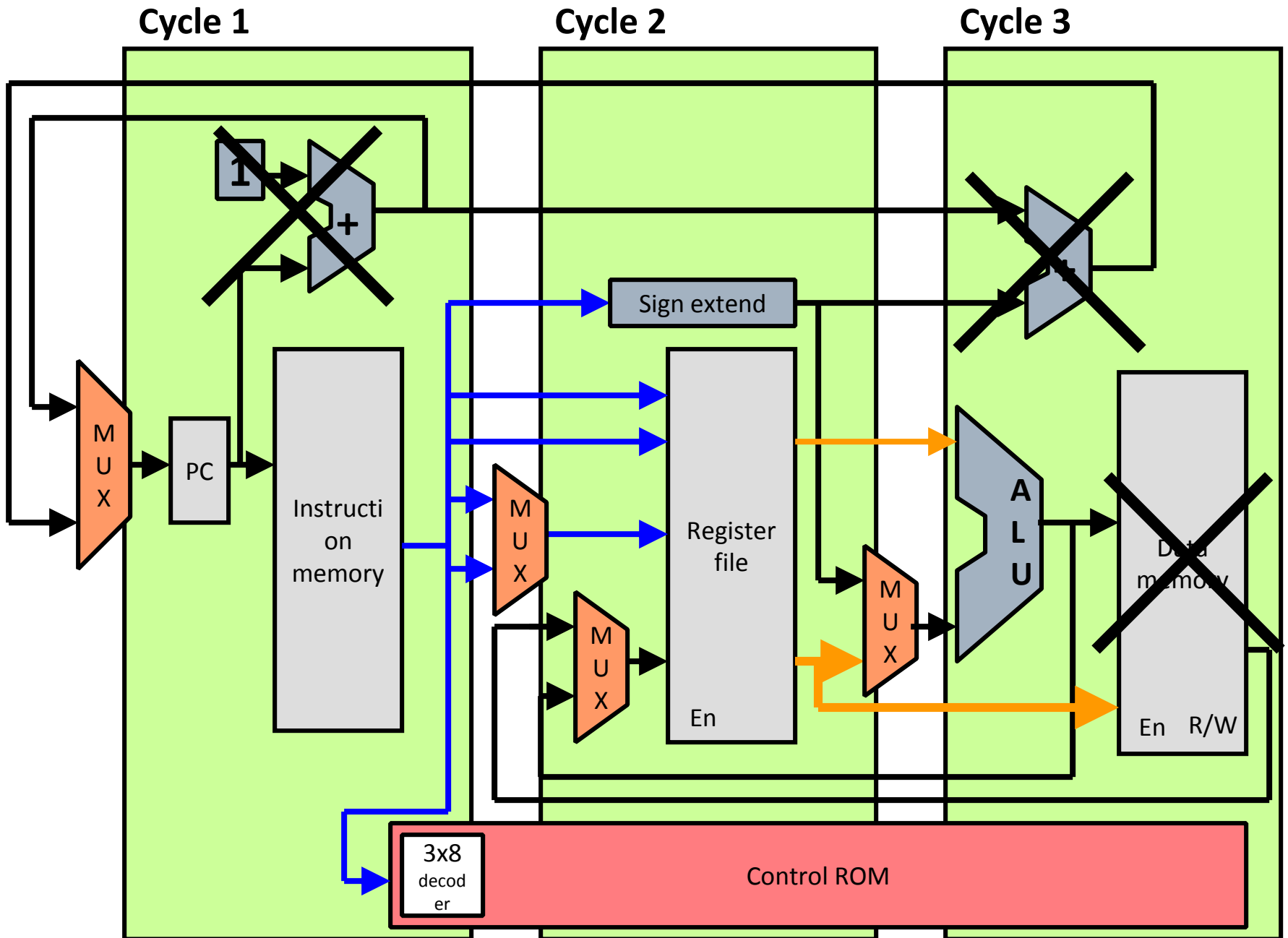


Multicycle LC2K Datapath

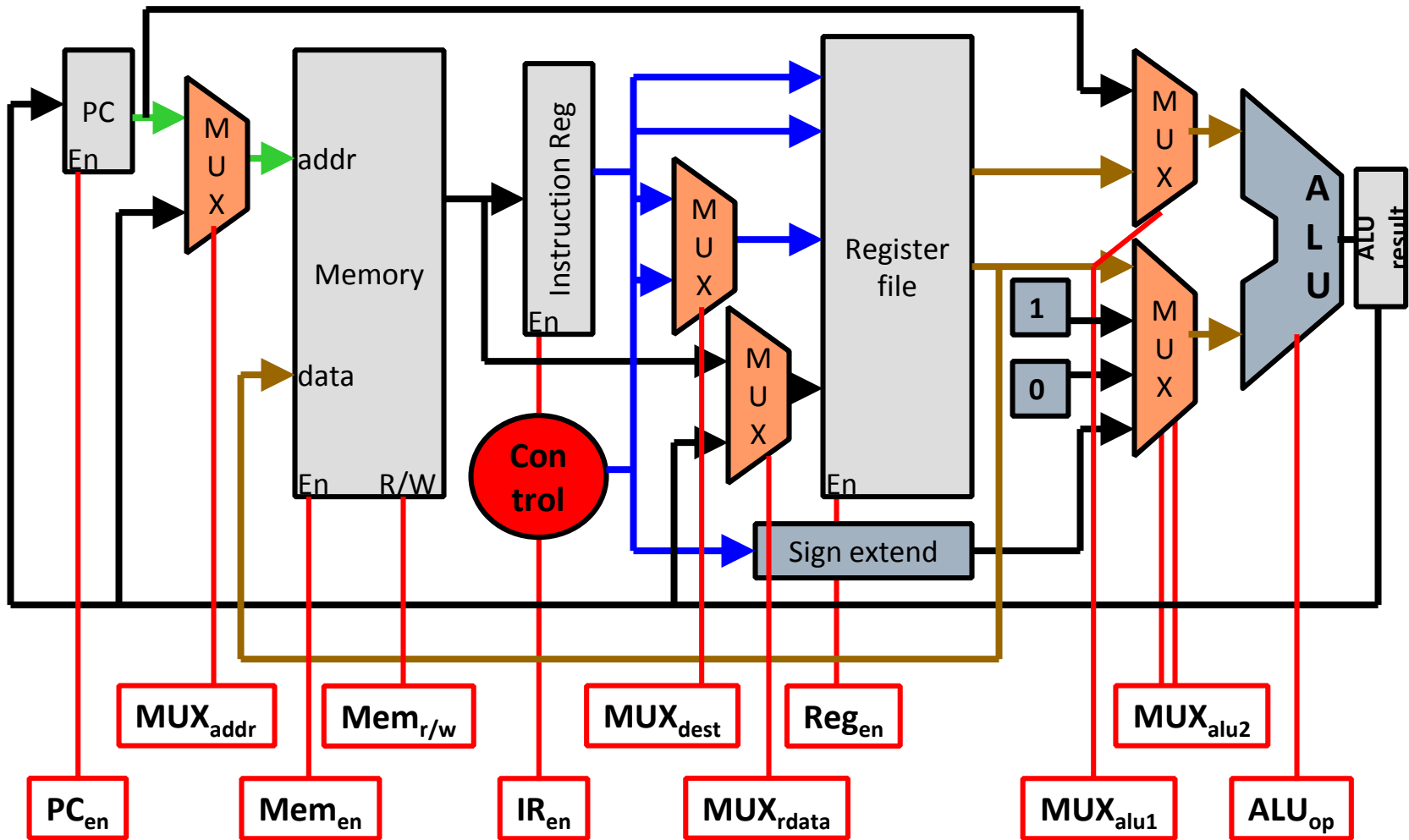

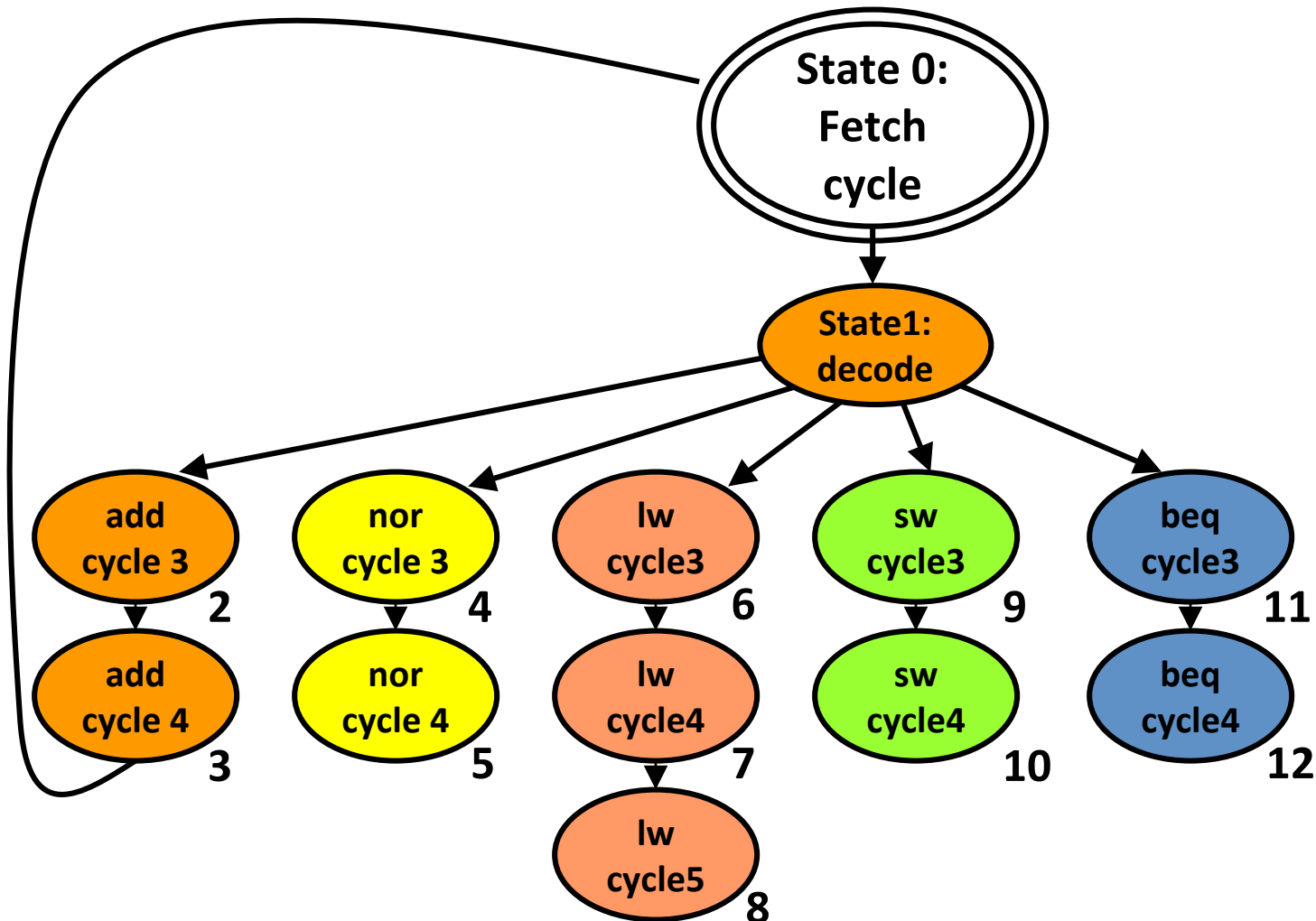
State machine for multi-cycle control signals (transition functions)



Implementing the FSM

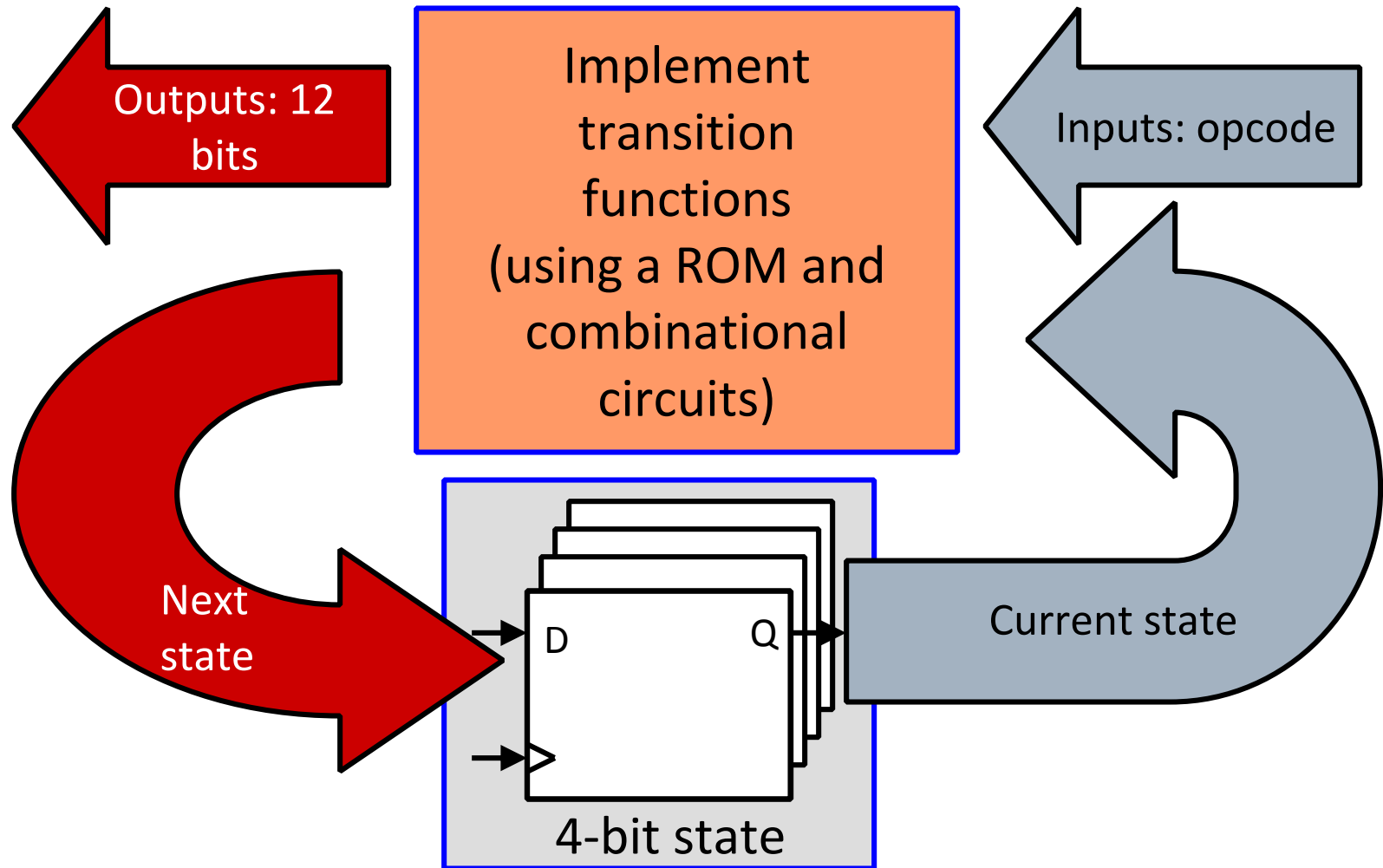

Building the Control ROM

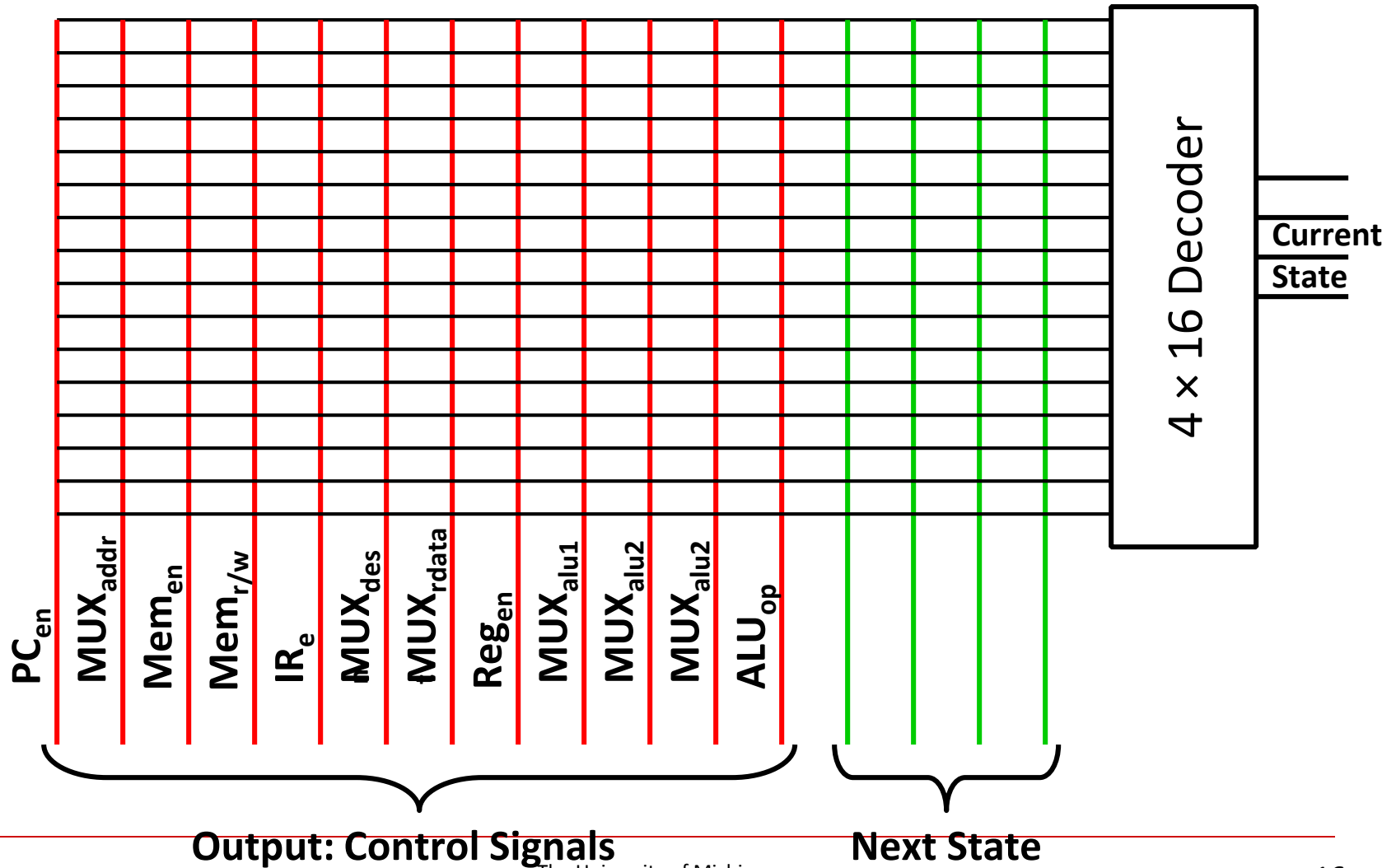


First Cycle (State 0) Fetch Instr

❑ What operations need to be done in the first cycle of executing any instruction?

- Read memory[PC] and store into instruction register.
 - Must select PC in memory address MUX ($MUX_{addr} = 0$)
 - Enable memory operation ($Mem_{en} = 1$)
 - R/W should be (read) ($Mem_{r/w} = 0$)
 - Enable Instruction Register write ($IR_{en} = 1$)
- Calculate PC + 1
 - Send PC to ALU ($MUX_{alu1} = 0$)
 - Send 1 to ALU ($MUX_{alu2} = 01$)
 - Select ALU add operation ($ALU_{op} = 0$)


- $PC_{en} = 0$; $Reg_{en} = 0$; MUX_{dest} and $MUX_{rdata} = X$

❑ Next State: Decode Instruction

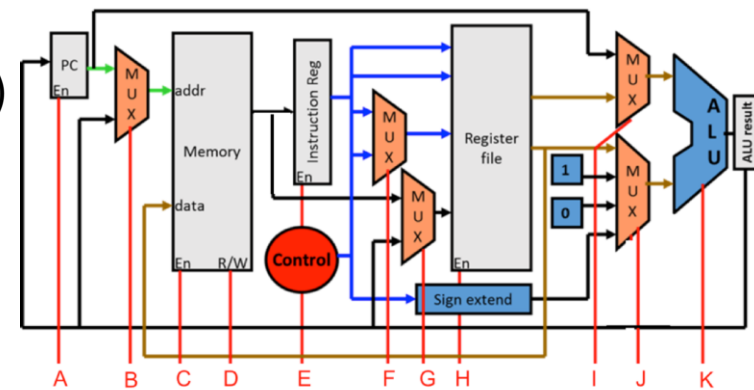


First Cycle (State 0) Operation

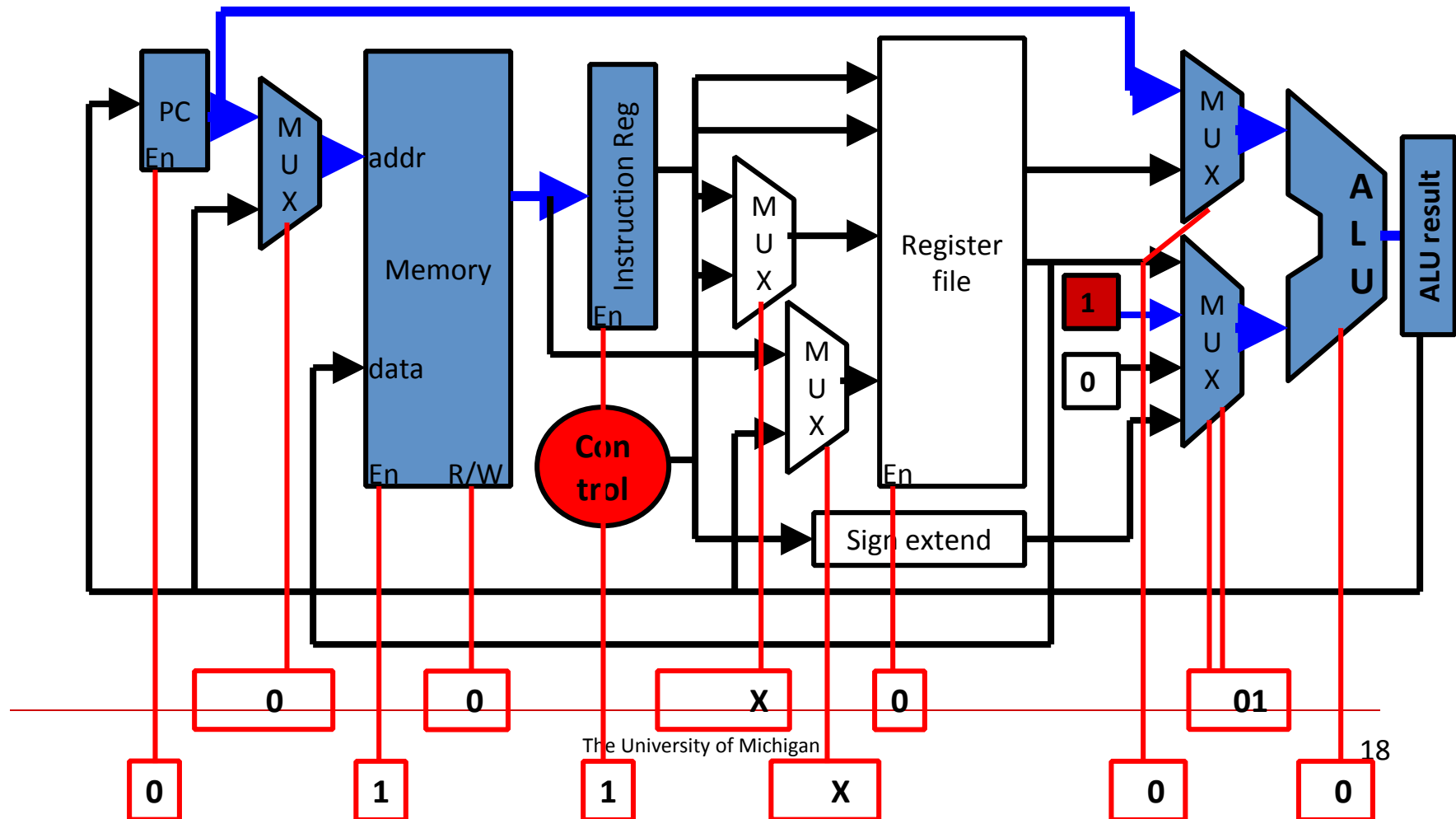
This is the same for all instructions
(since we don't know the instruction yet!)



Building the Control Rom

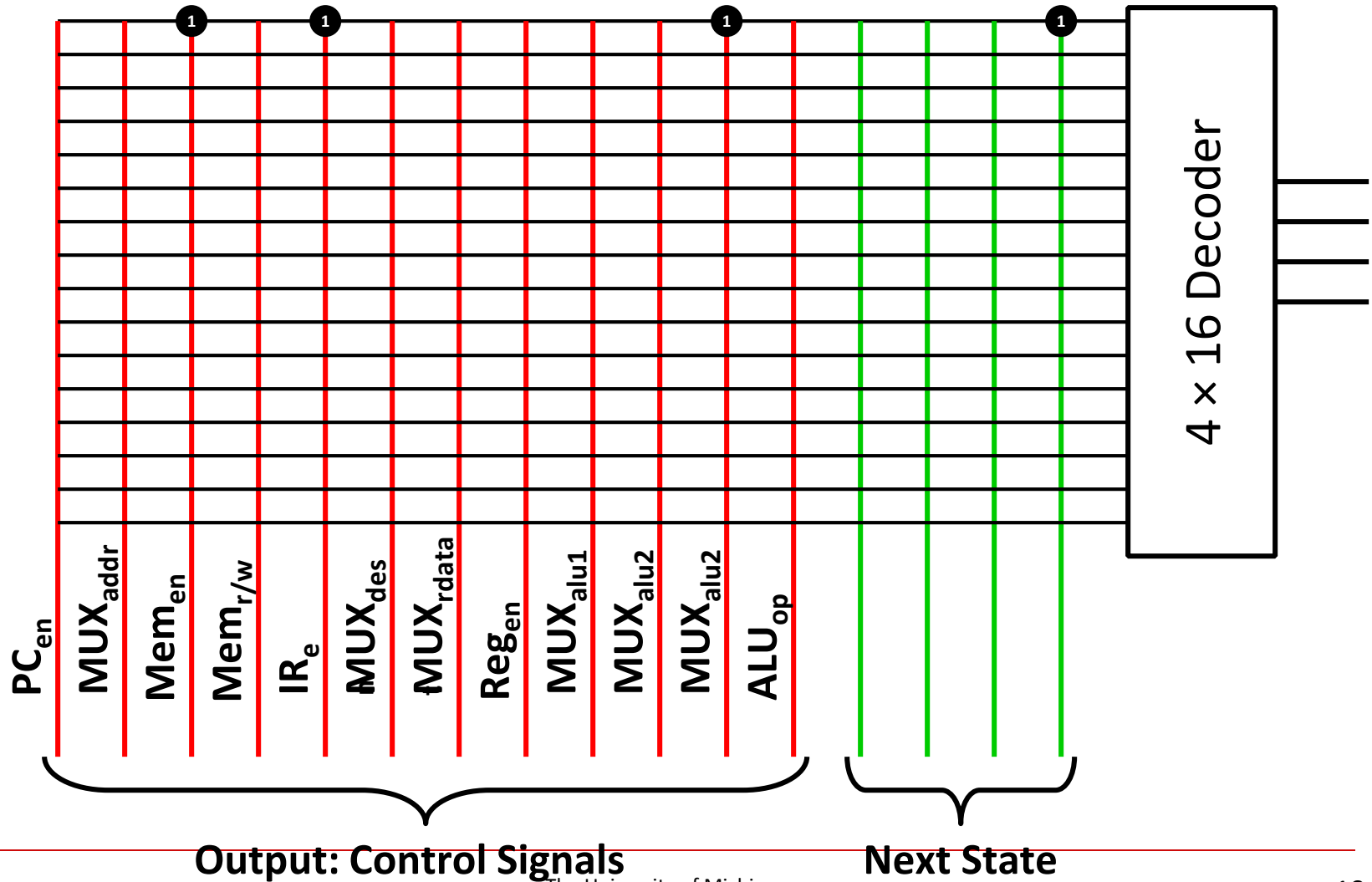


State 1: instruction decode

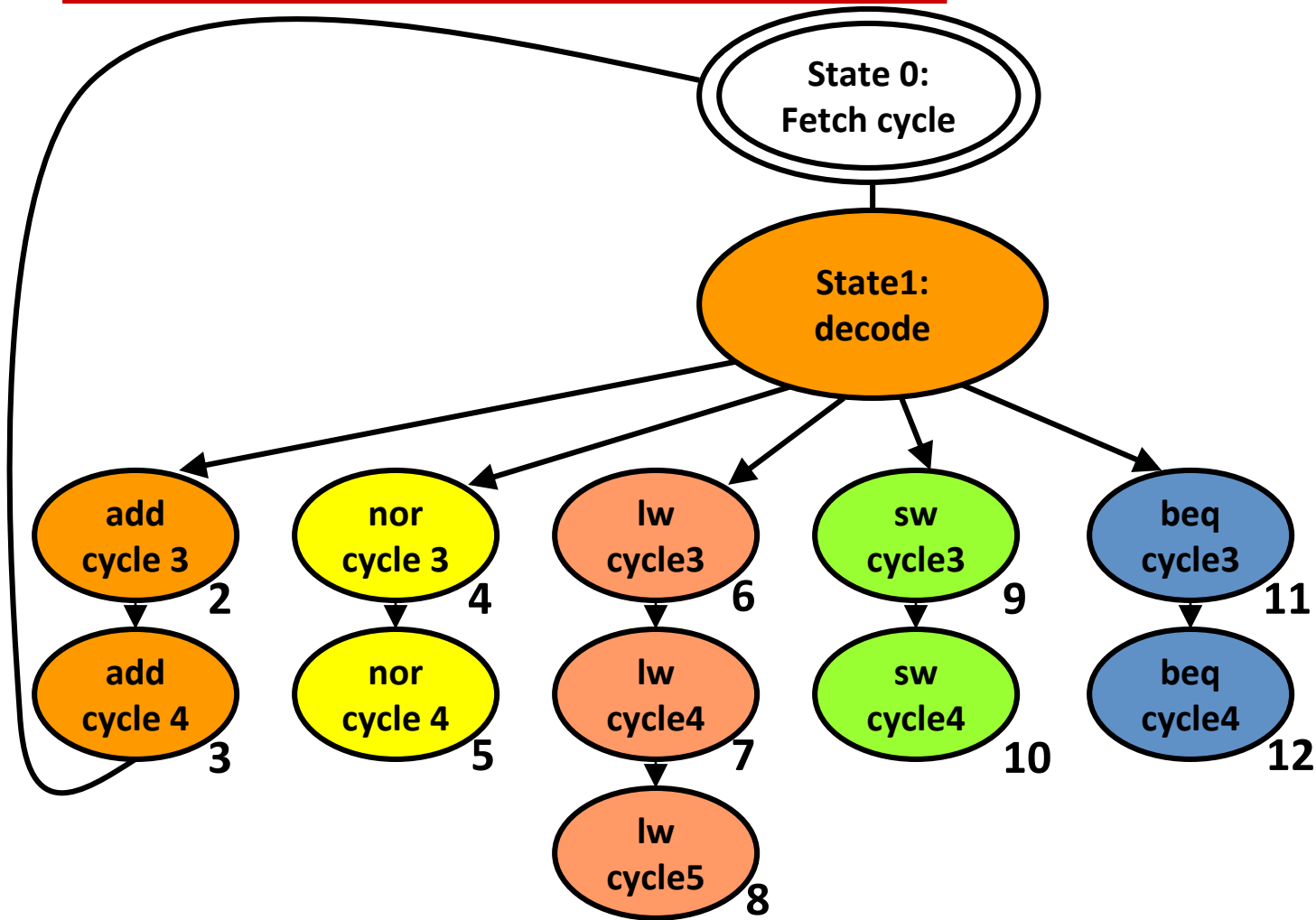


State 1: output function

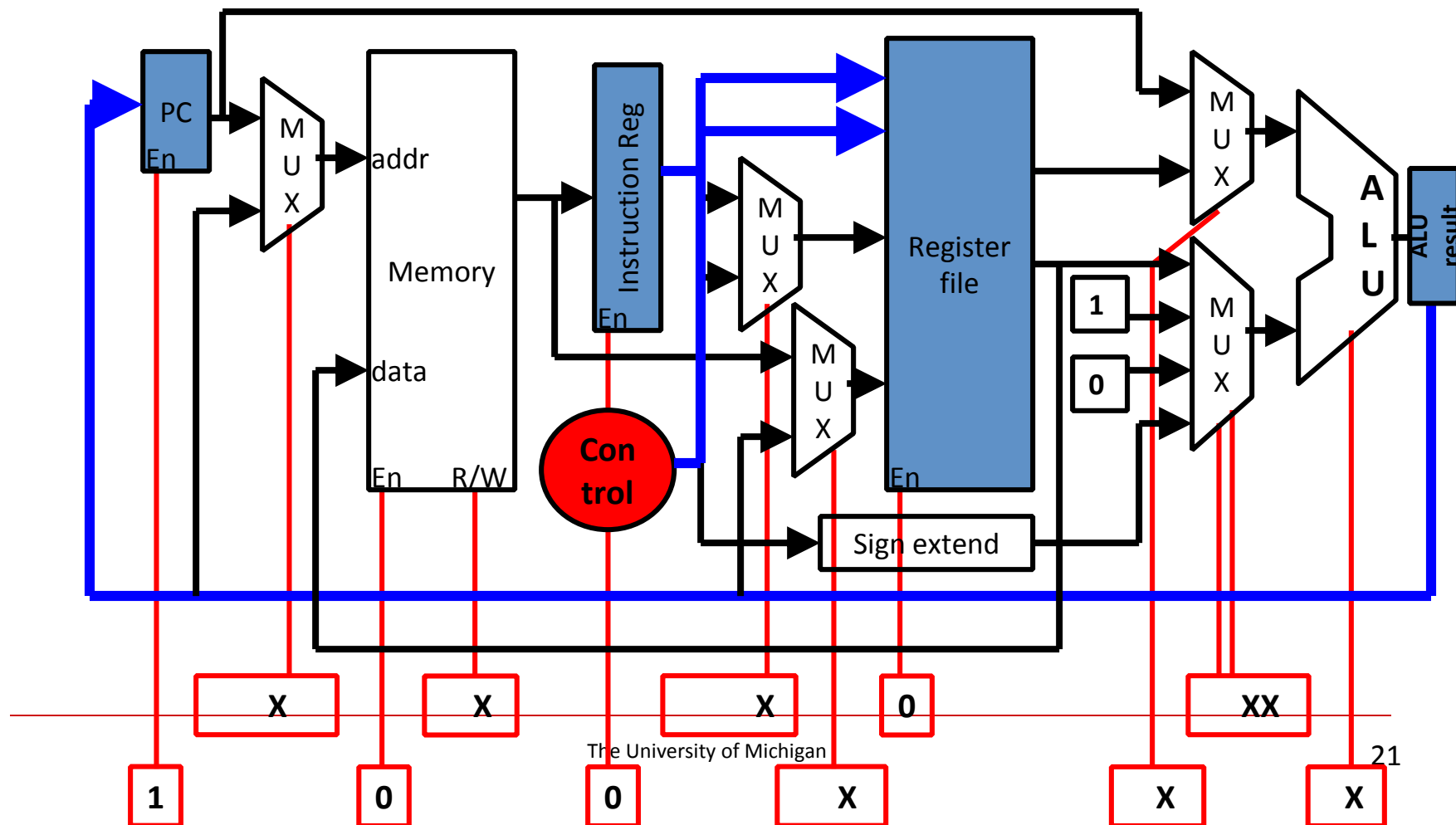
Update PC; read registers (regA and regB);
use opcode to determine next state



Building the Control Rom

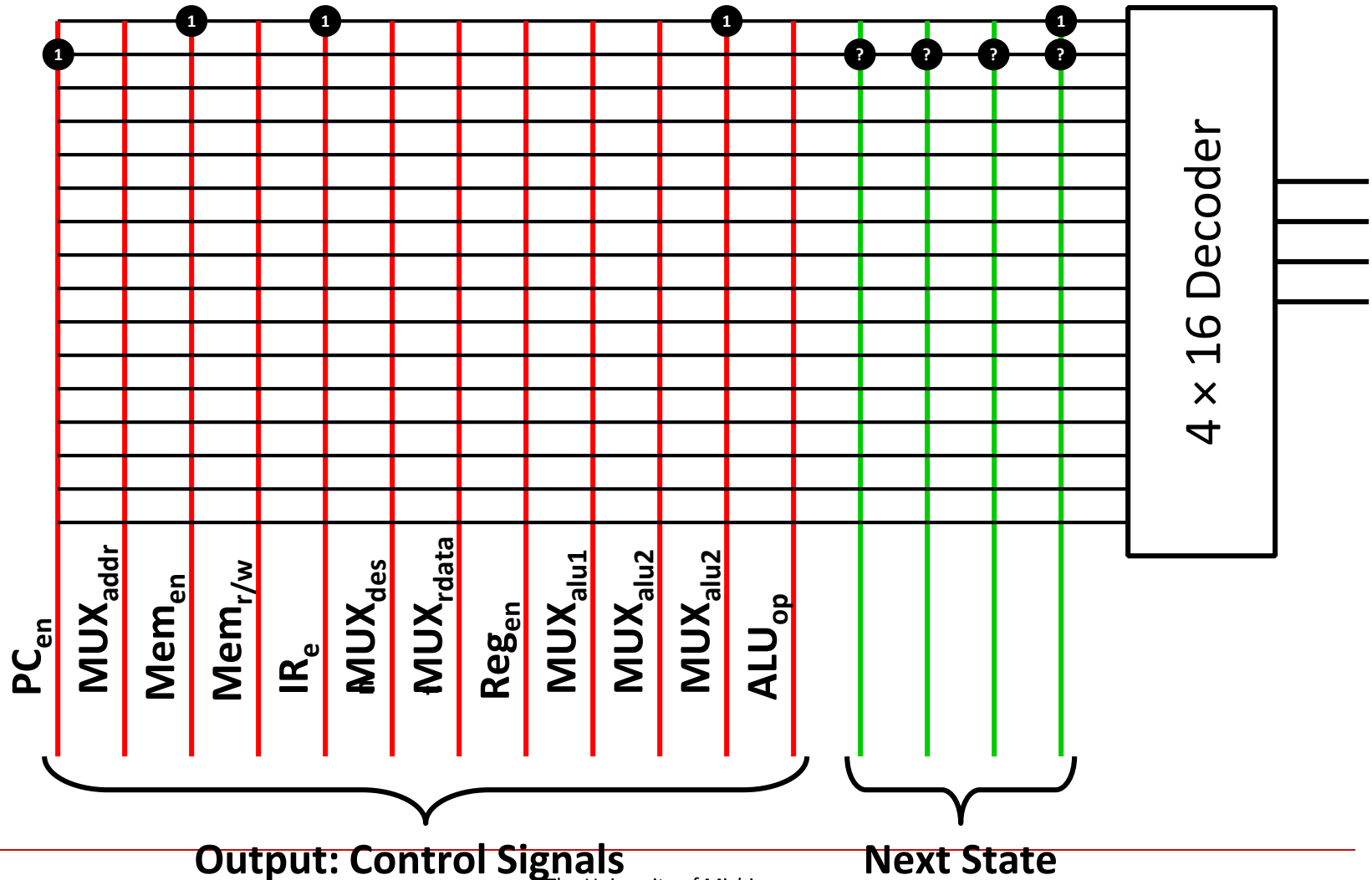


State 2: Add Cycle 3

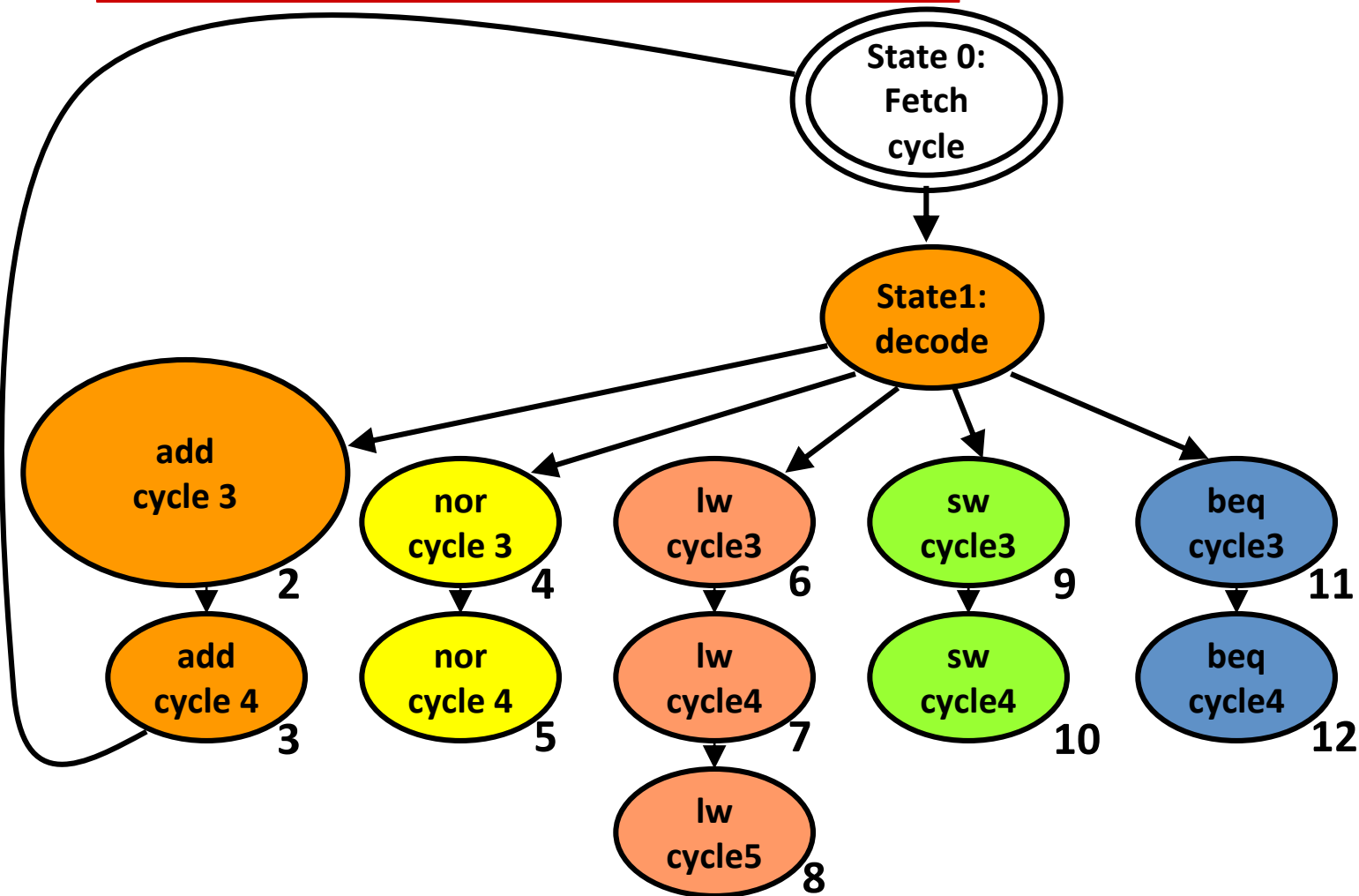


State 2: **Add** Cycle 3 Operation

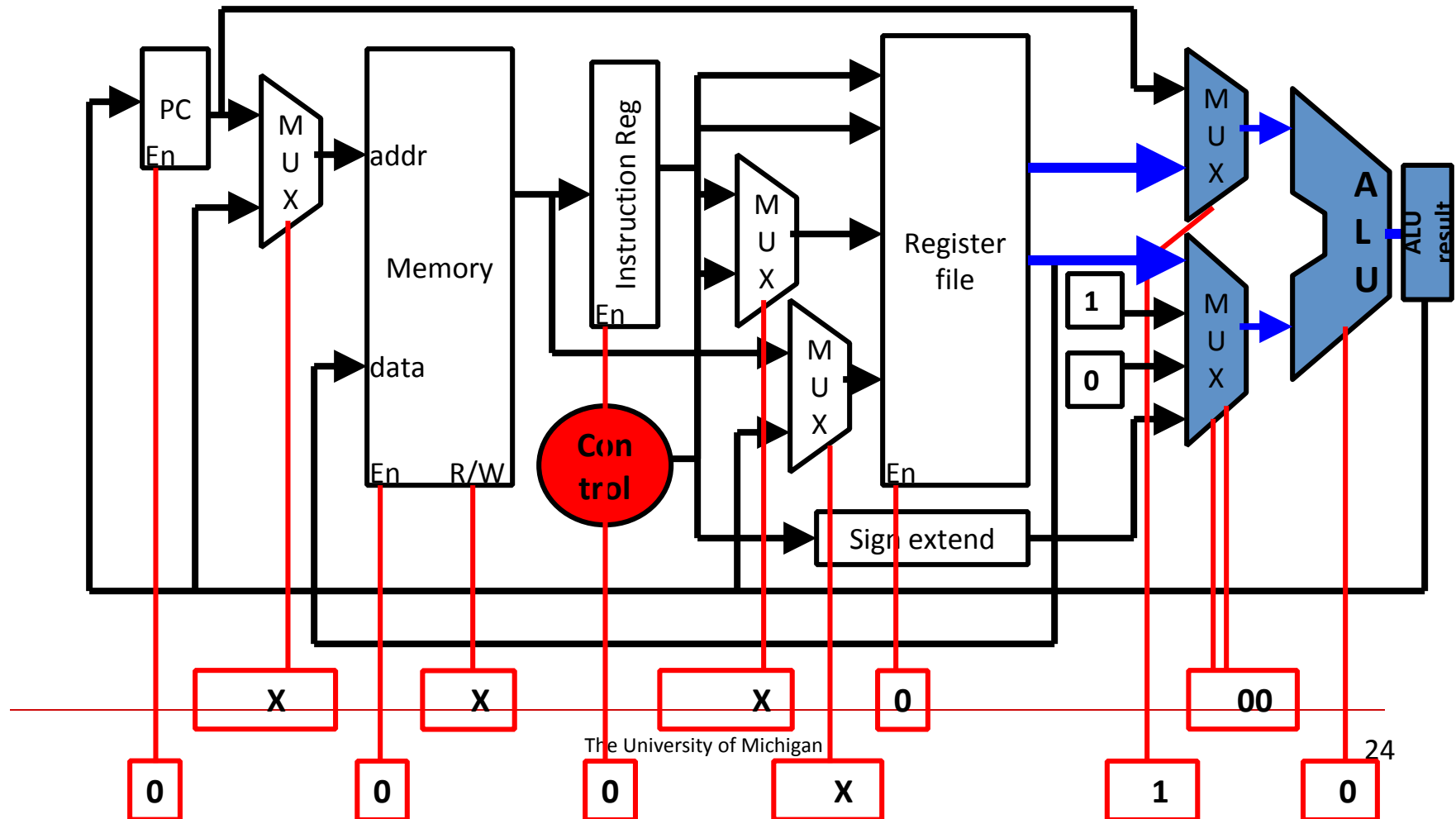
Send control signals to MUX to select values of regA and regB and control signal to ALU to add



Building the Control Rom

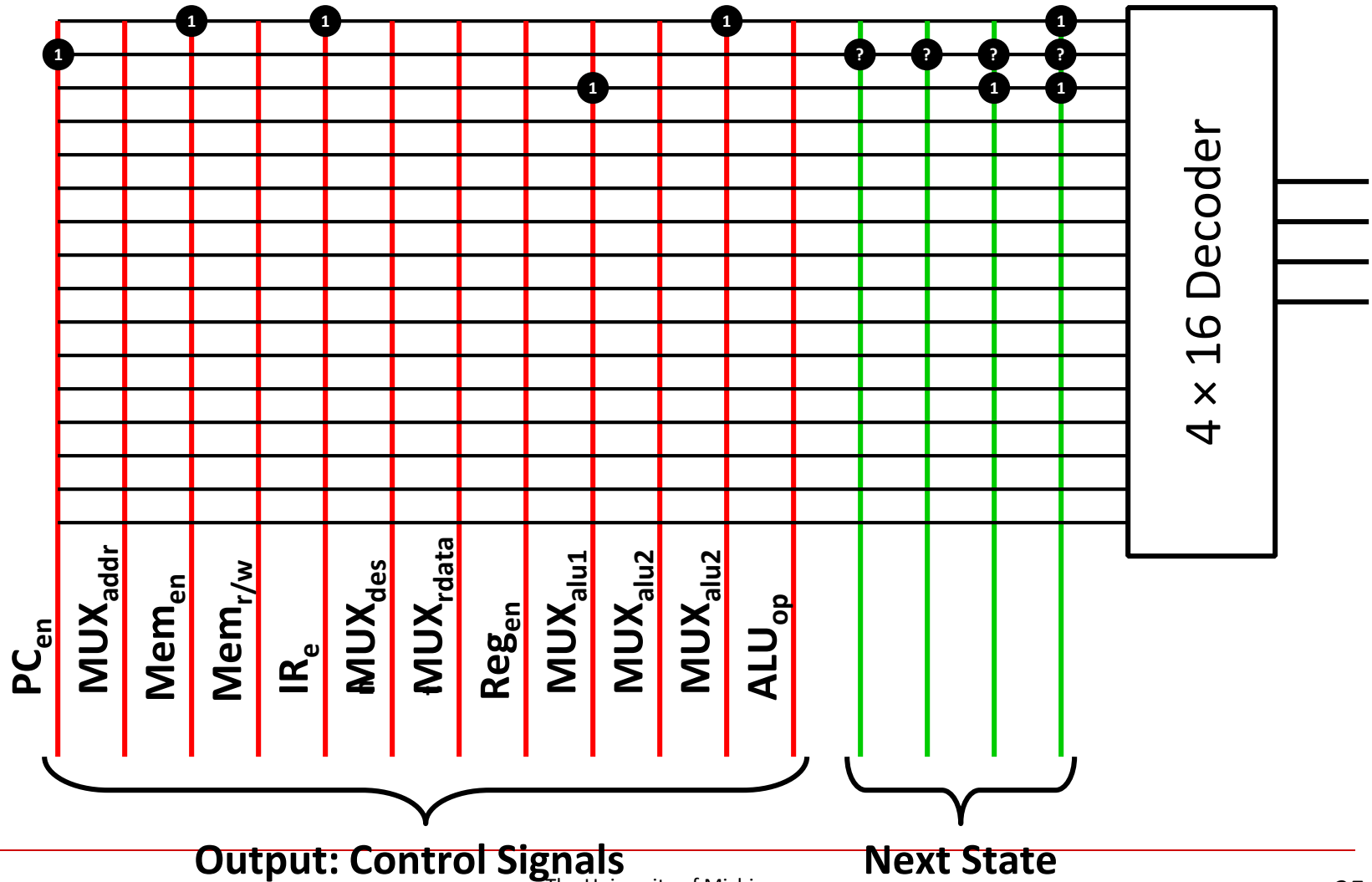


State 3: Add cycle 4

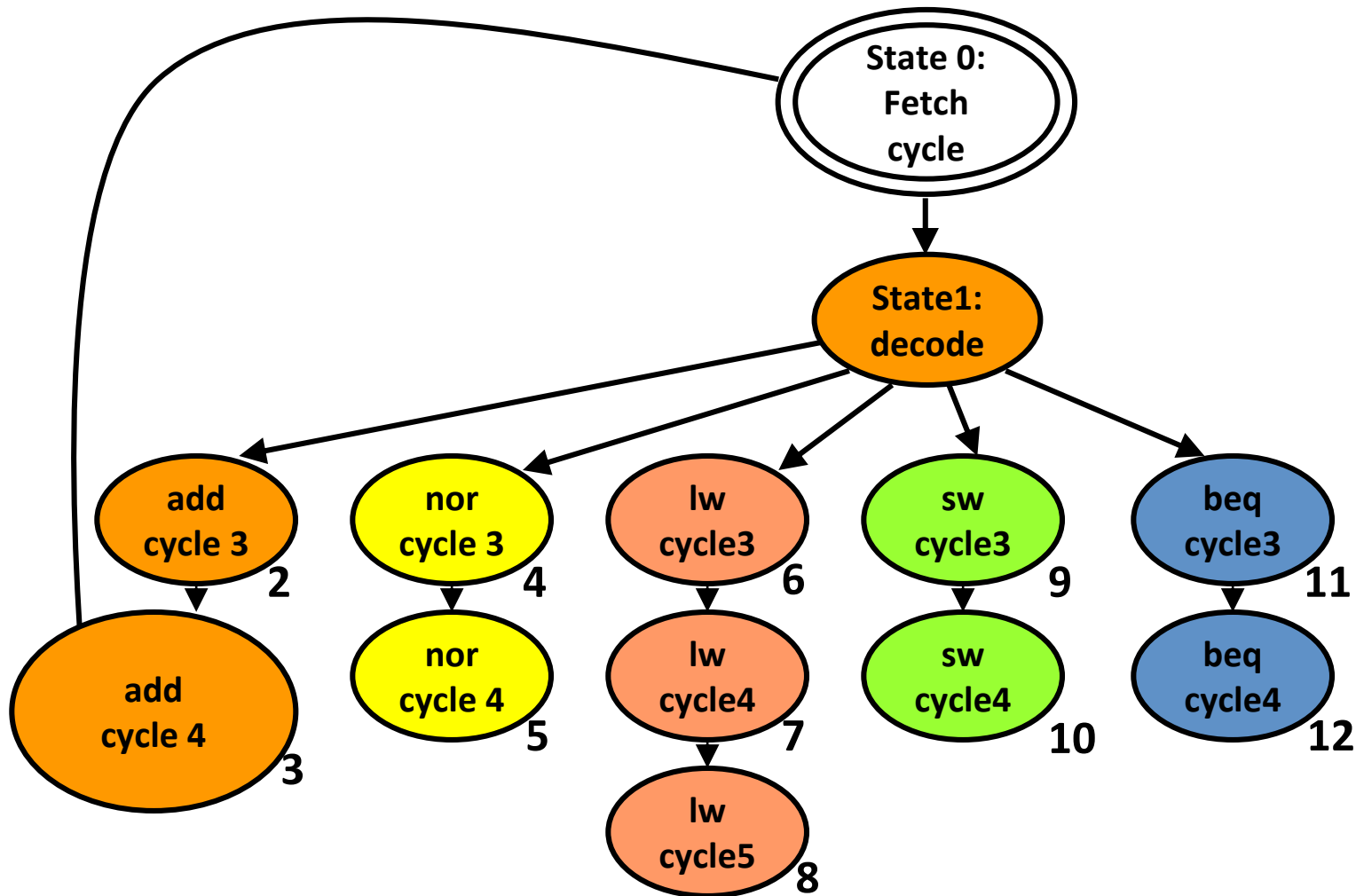


Add Cycle 4 (State 3) Operation

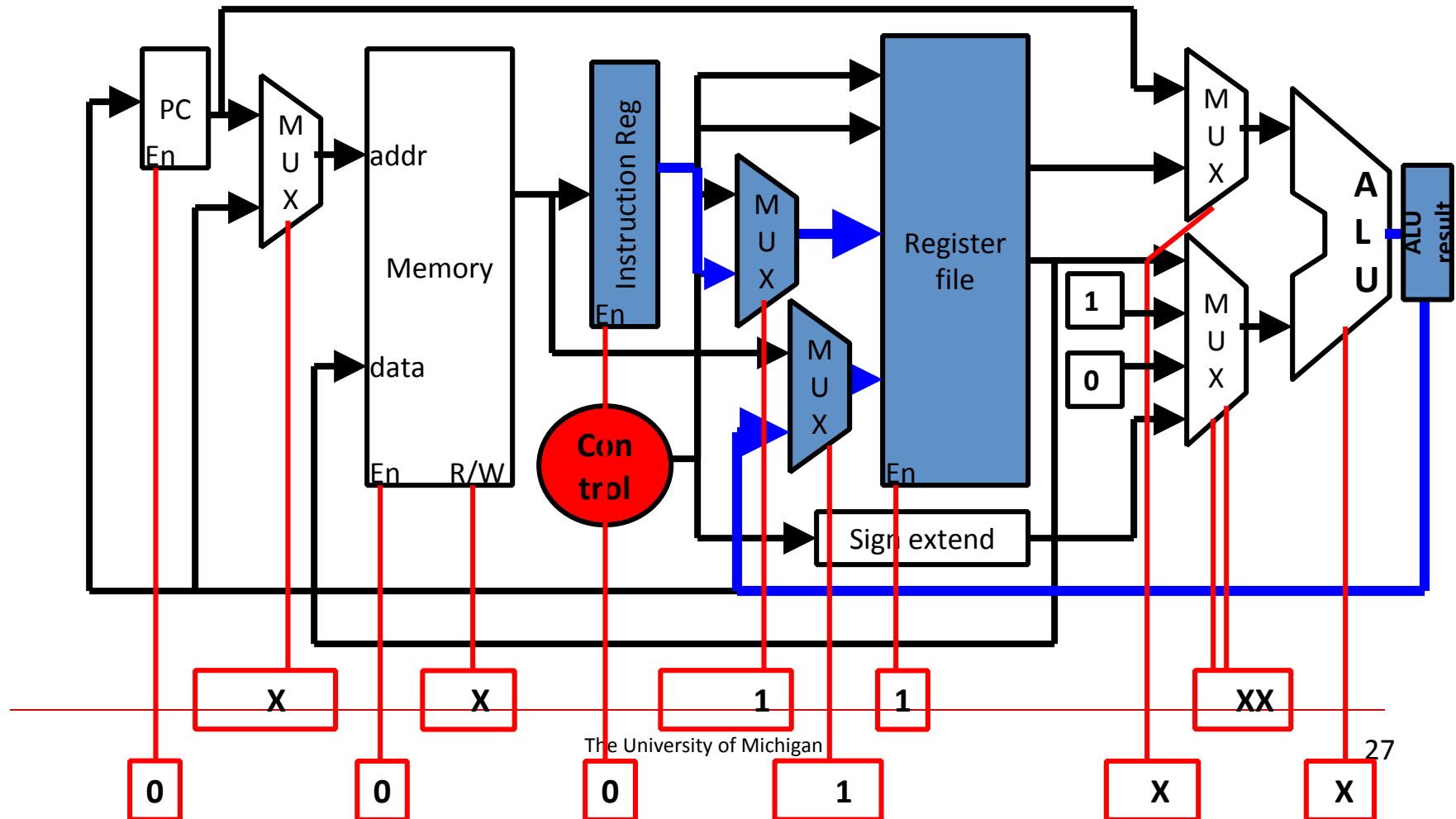
Send control signal to address MUX to select dest and to data MUX to select ALU output, then send write enable to register file.




Building the Control Rom

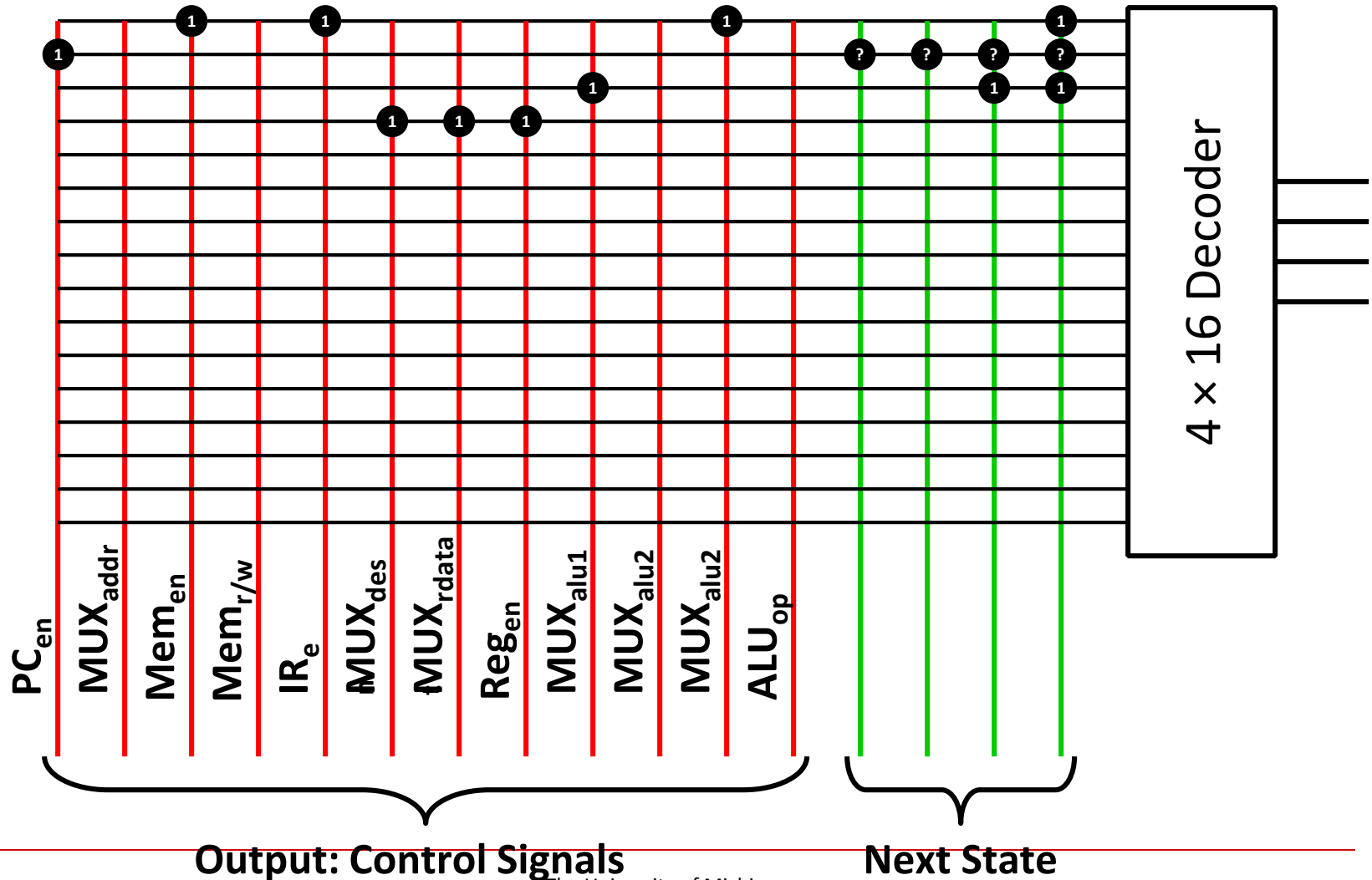

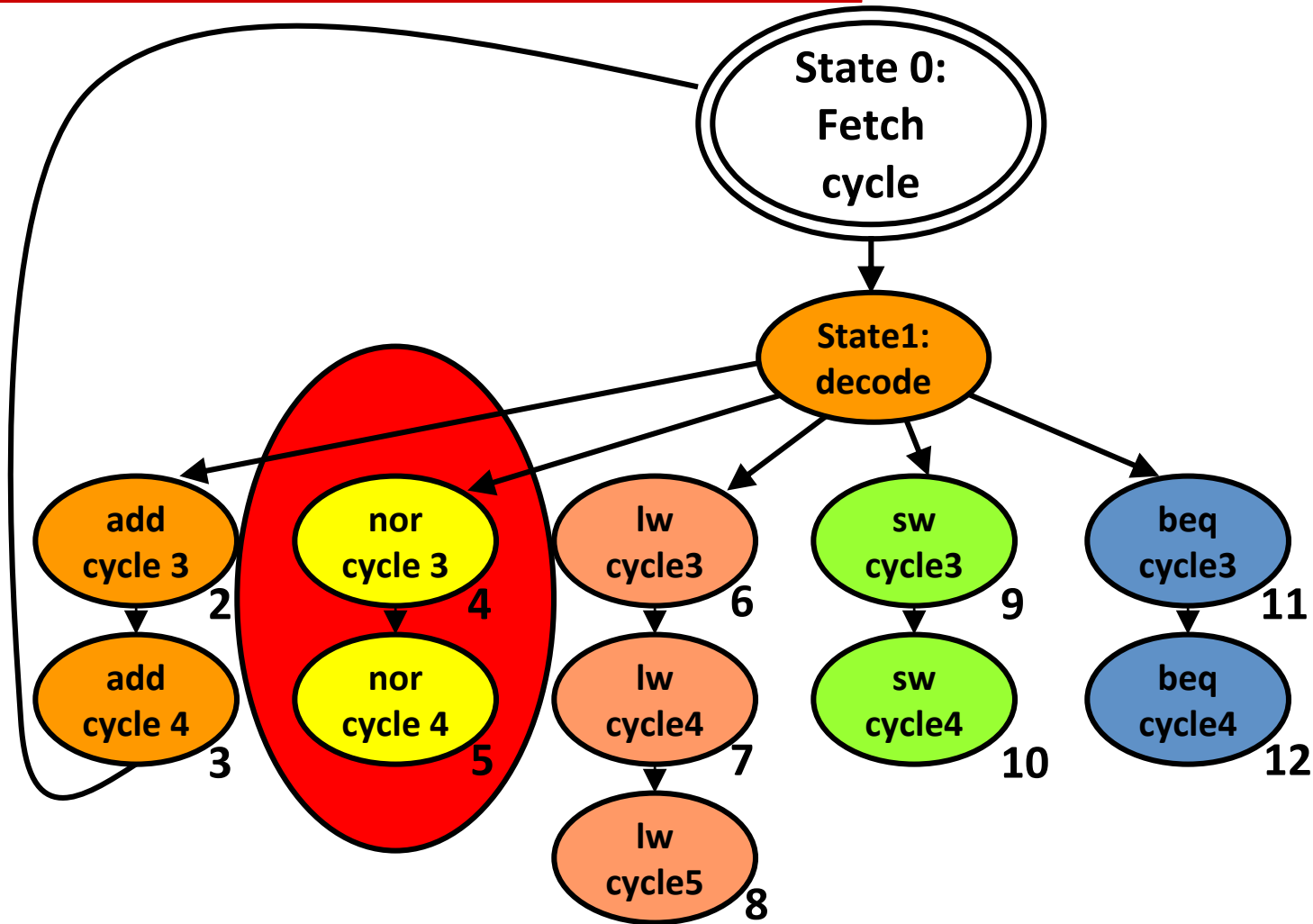
Return to State 0: Fetch cycle to execute the next instruction




Control Rom for nor (4 and 5)

 


What about the transition from state 1?

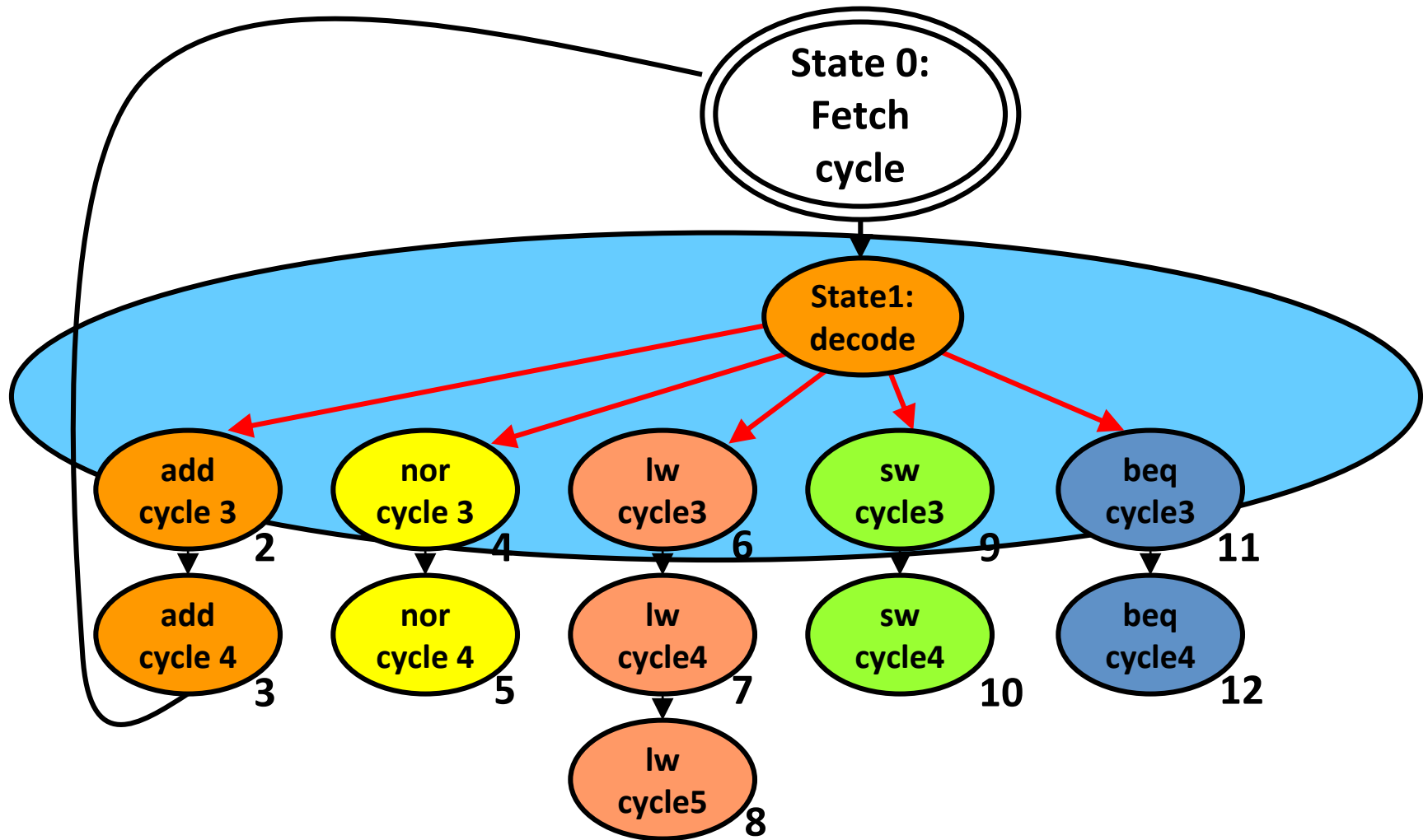

Complete transition function circuit

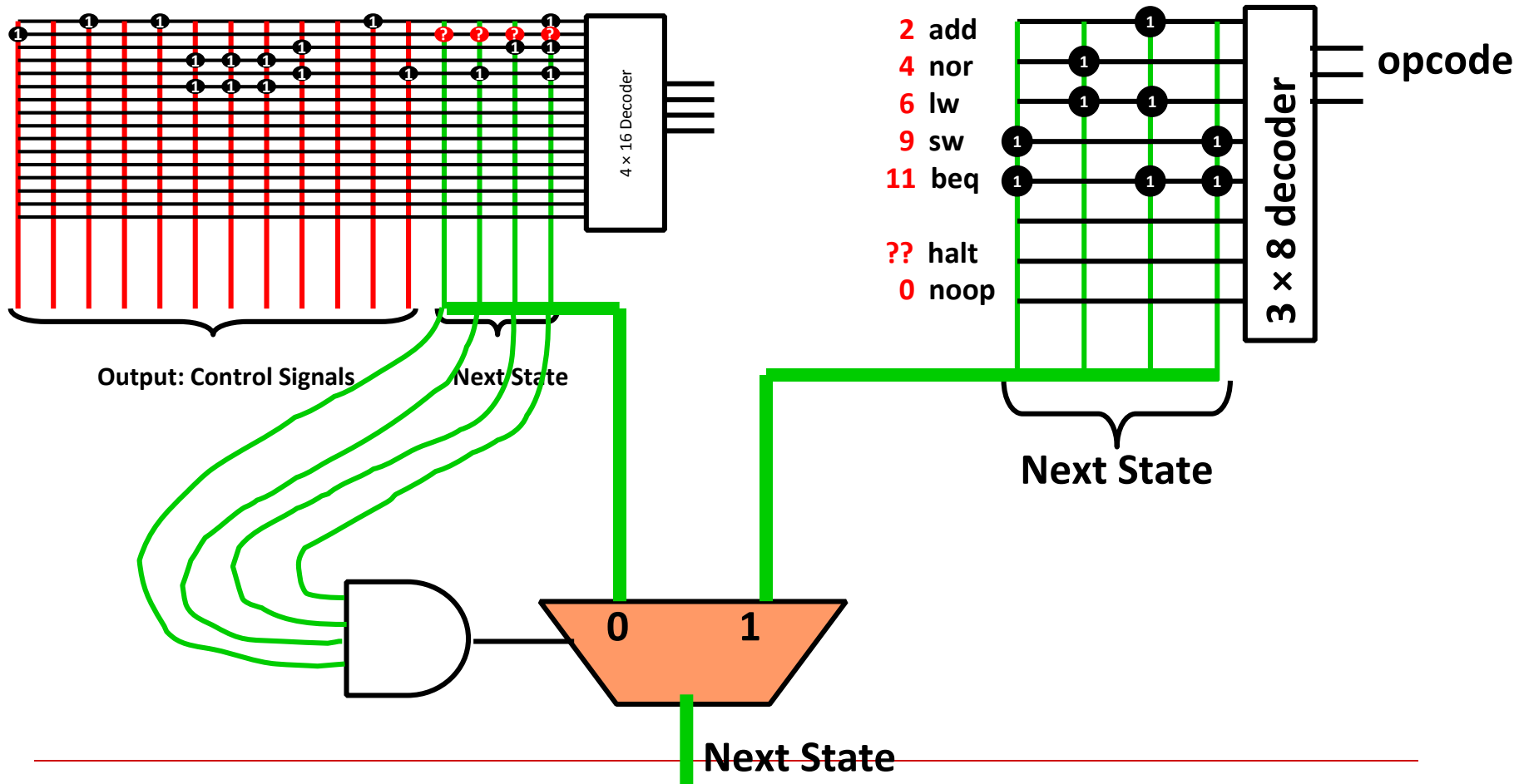


Control ROM (use of 1111 state)

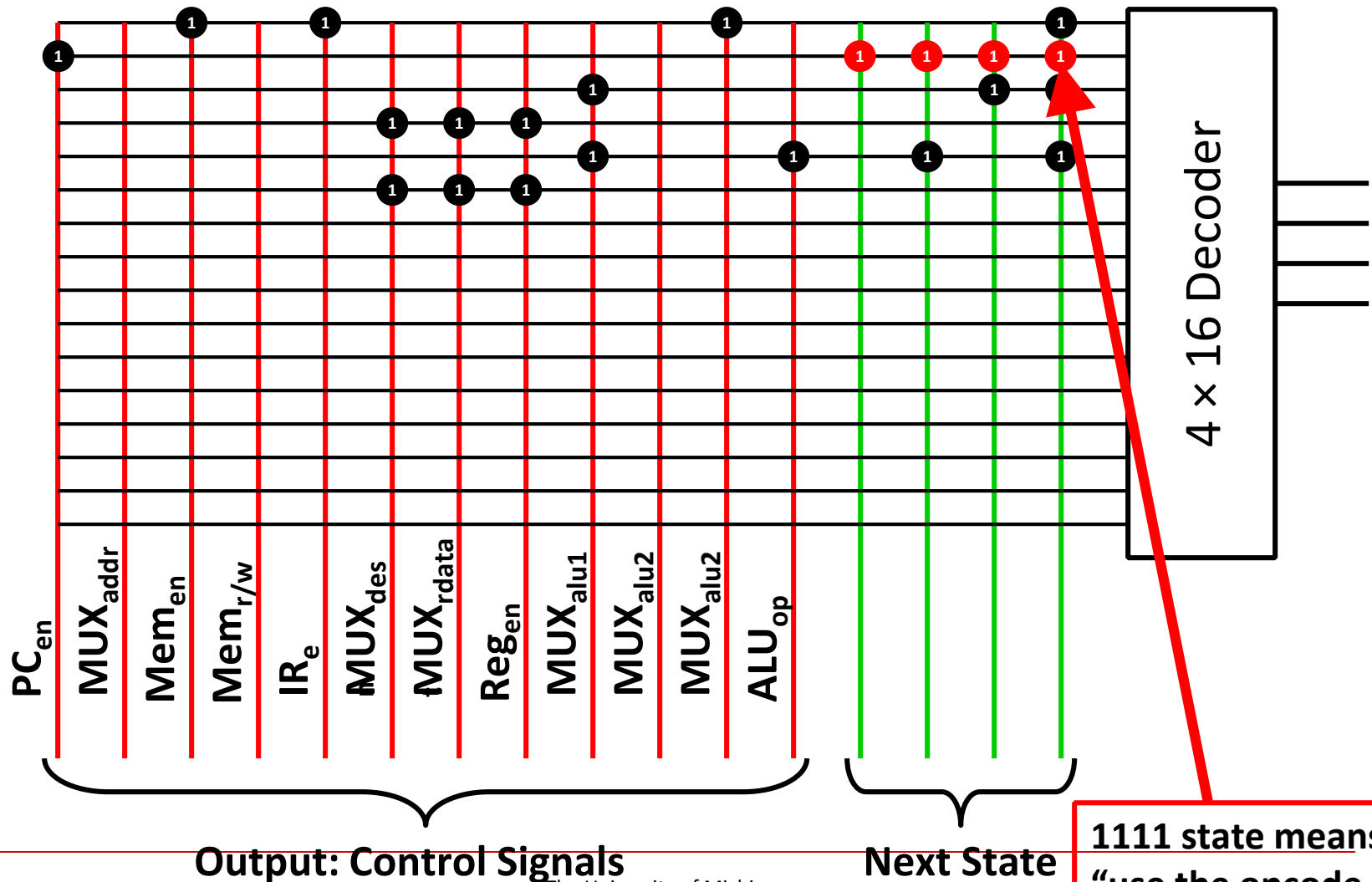

1111 state means
"use the opcode
to decide next state"


Return to State 0:

Fetch cycle to execute the next instruction

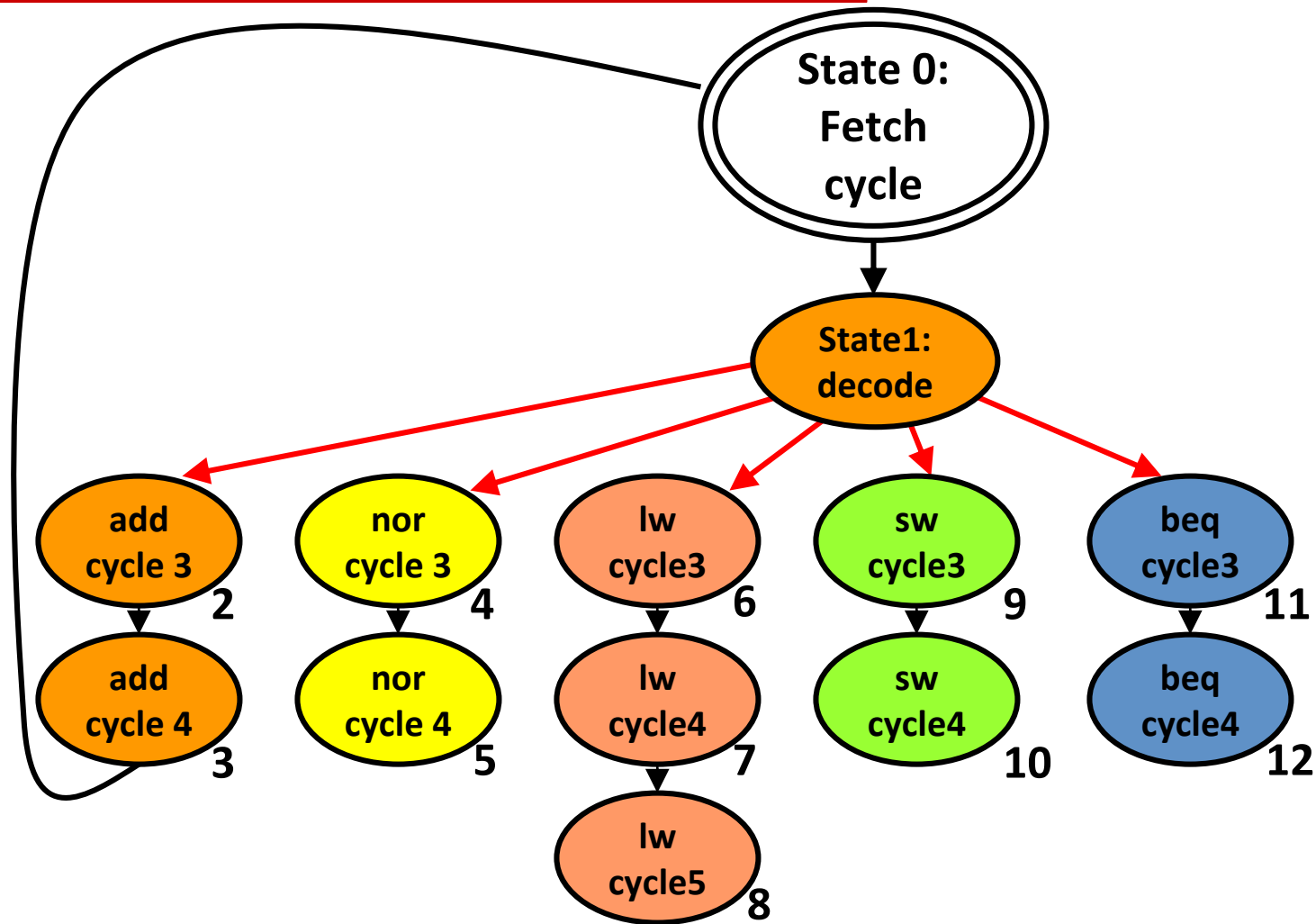


State 6: LW cycle 3

Calculate address for memory reference

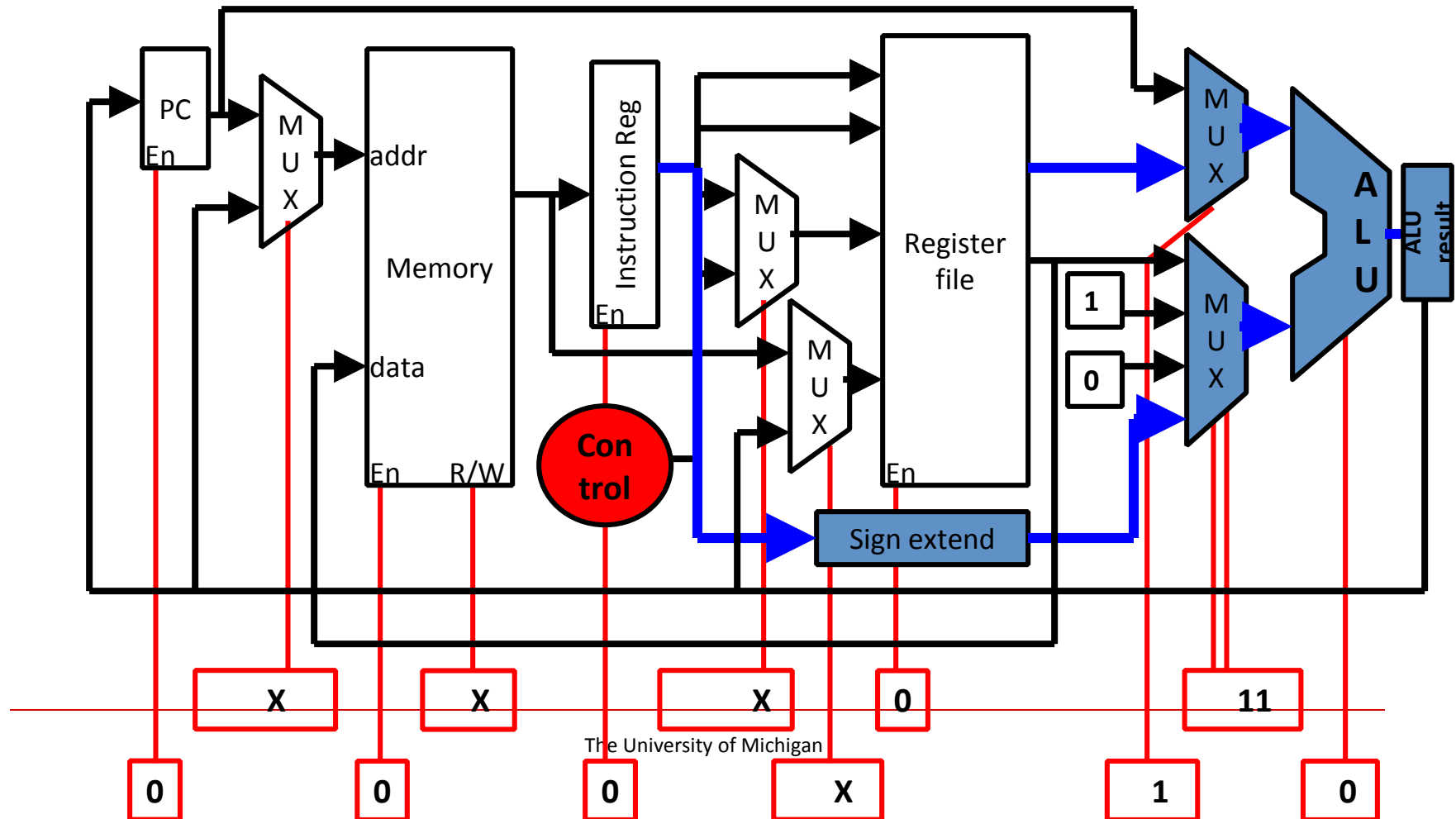


Control Rom (lw cycle 3)

 


State 7: LW cycle 4

Read memory location

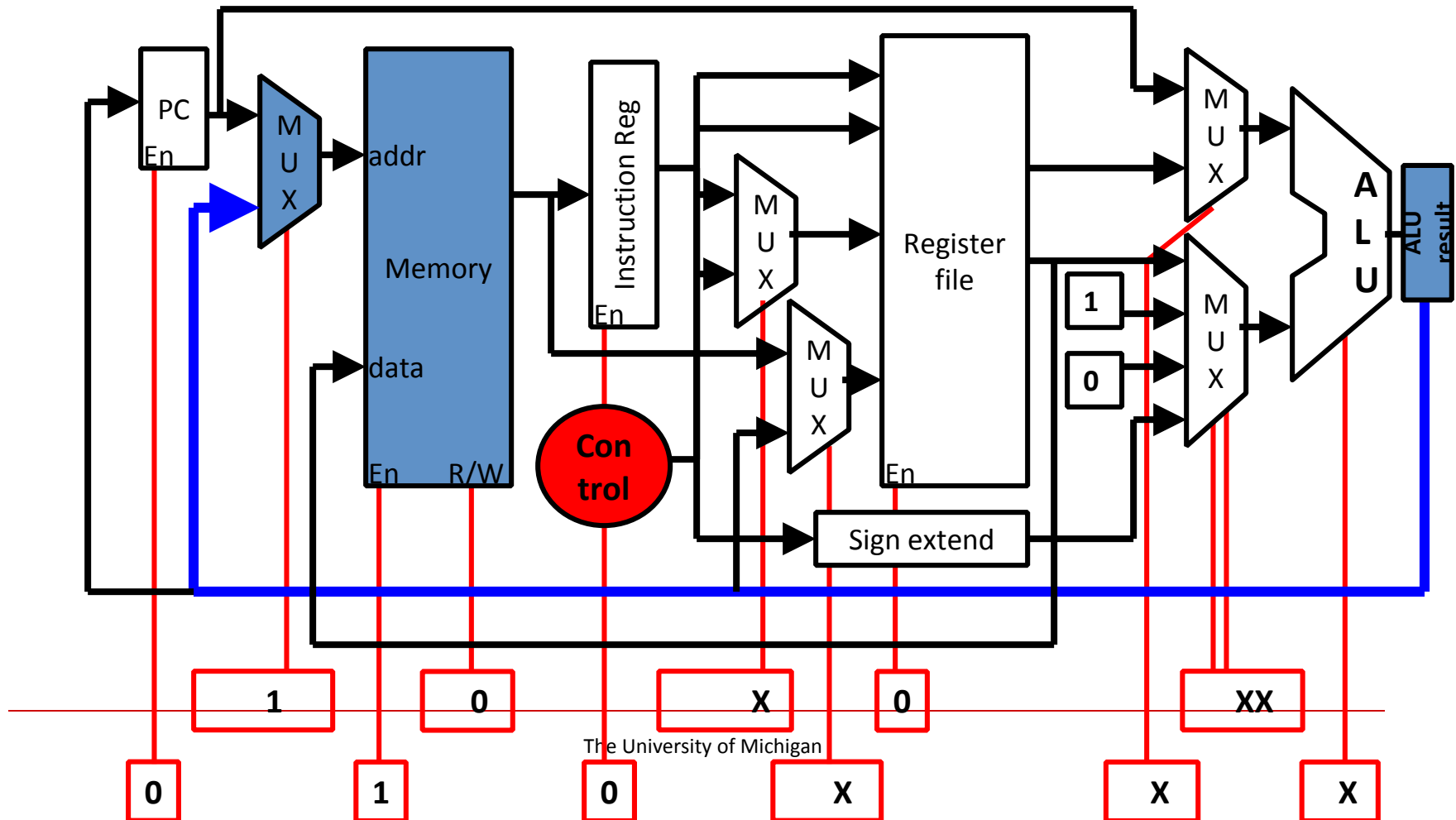


Control Rom (lw cycle 4)

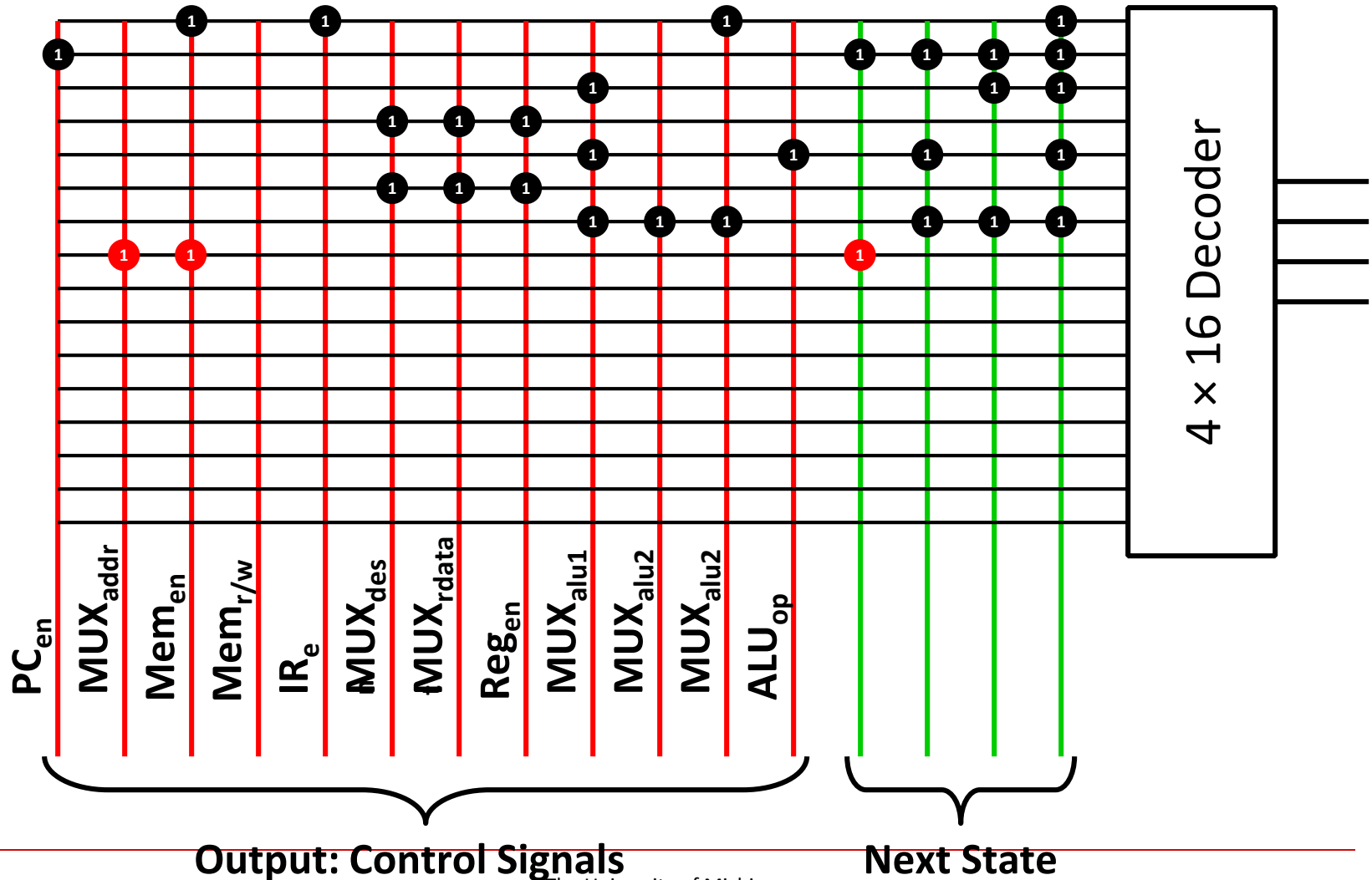


State 8: LW cycle 5


Write memory value to register file

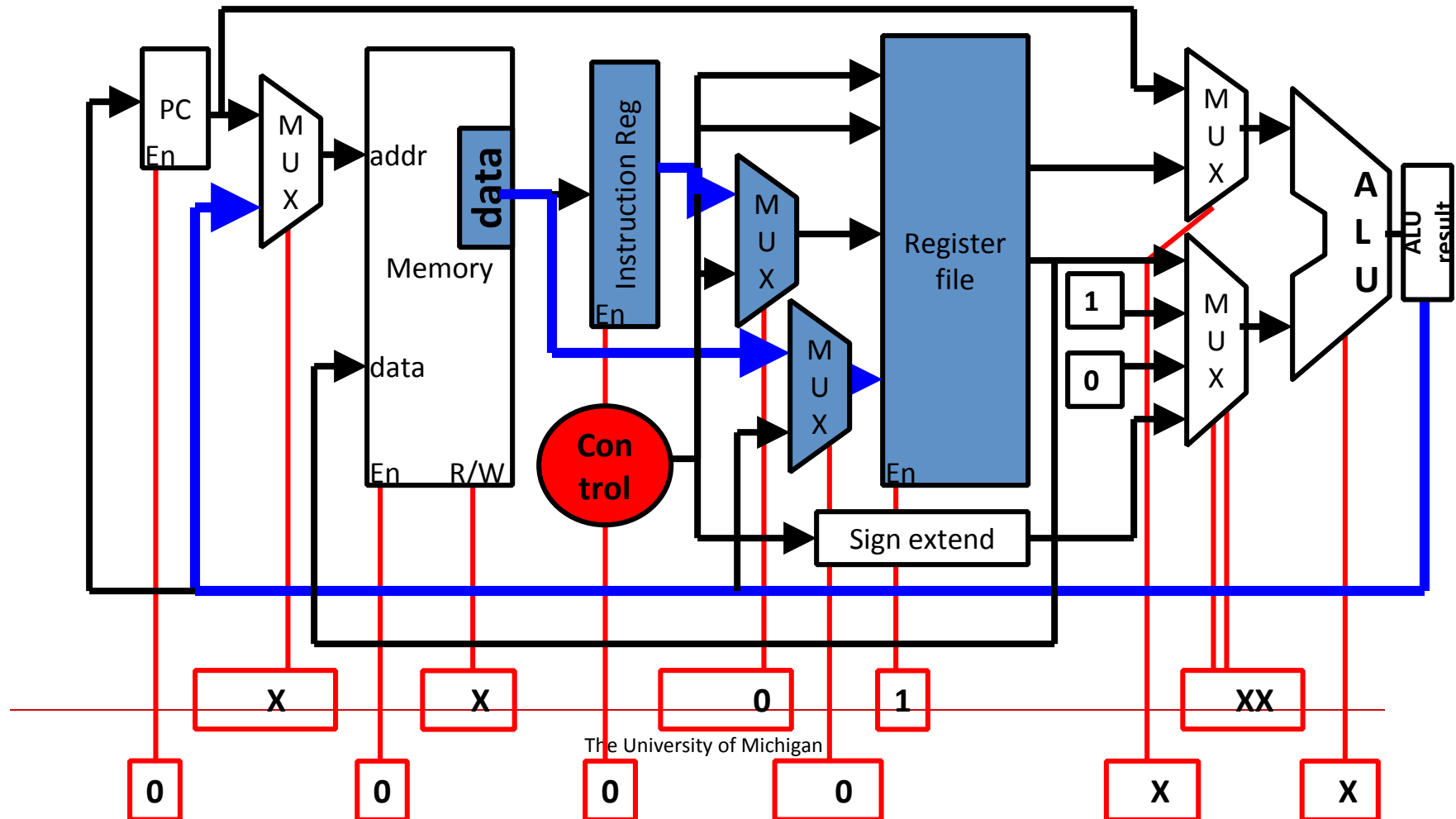


Control Rom (lw cycle 5)

 

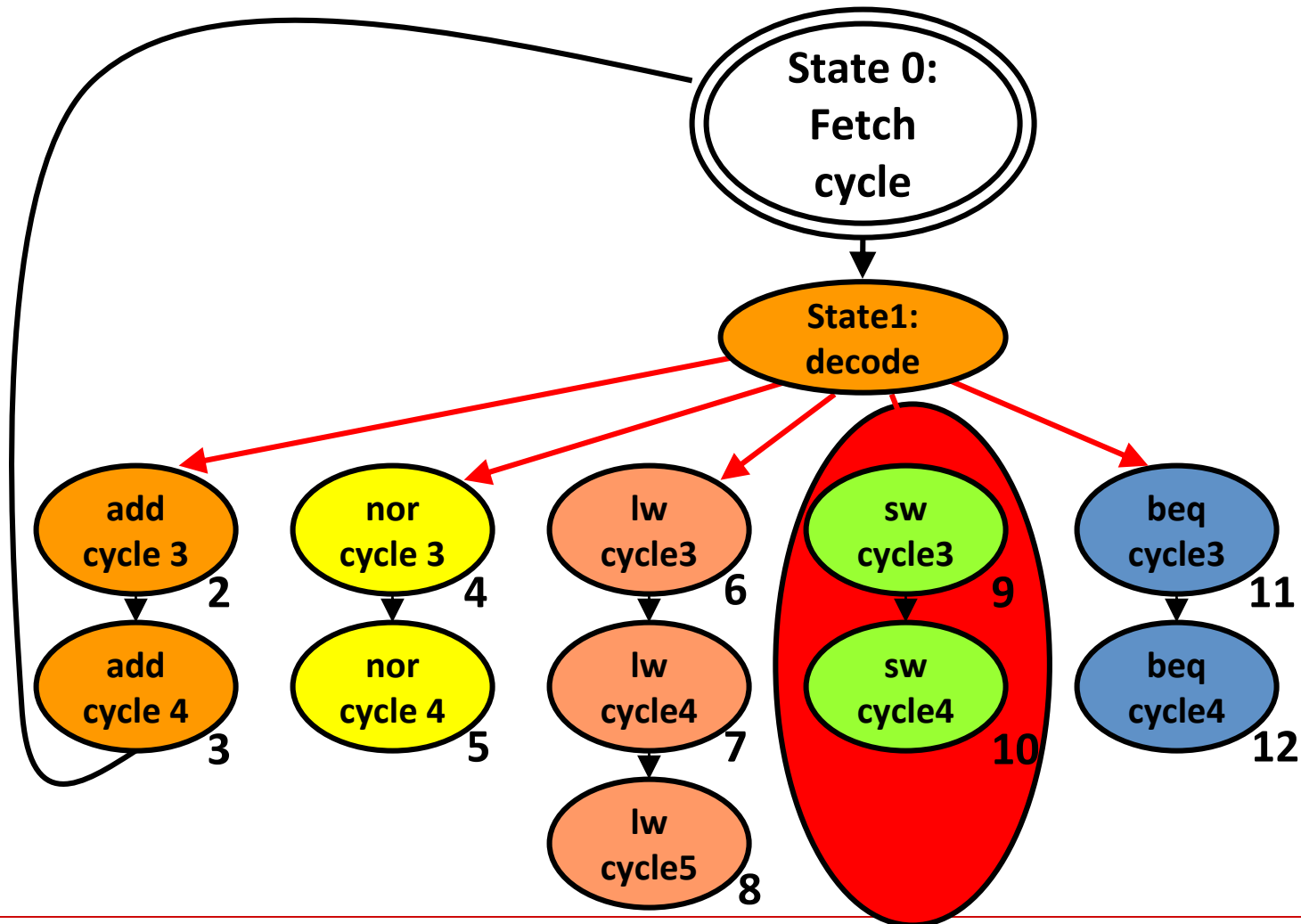Return to State 0: Fetch cycle to execute the next instruction




Control ROM (sw cycles 3 and 4)

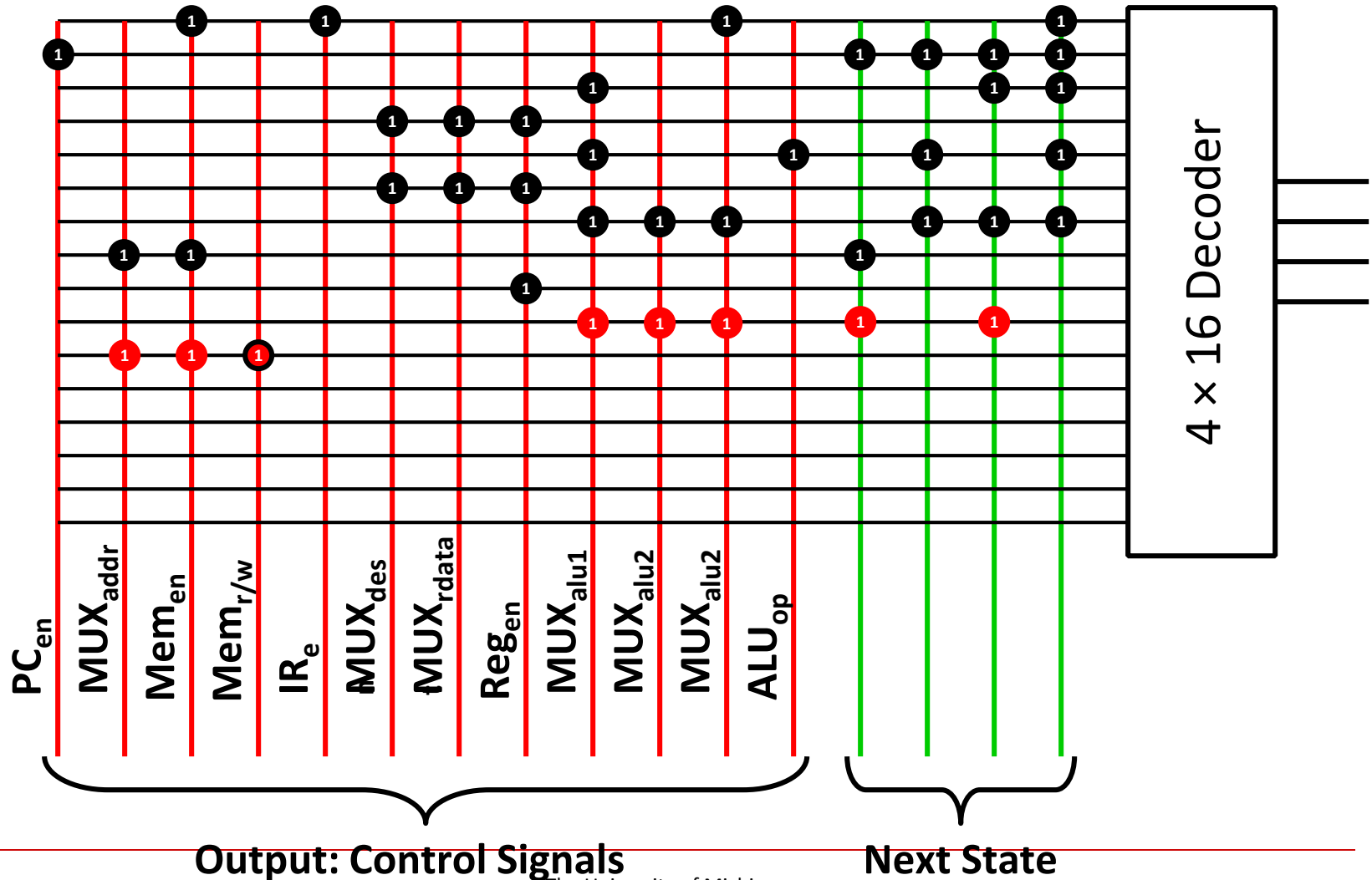


Return to State 0:

Fetch cycle to execute the next instruction

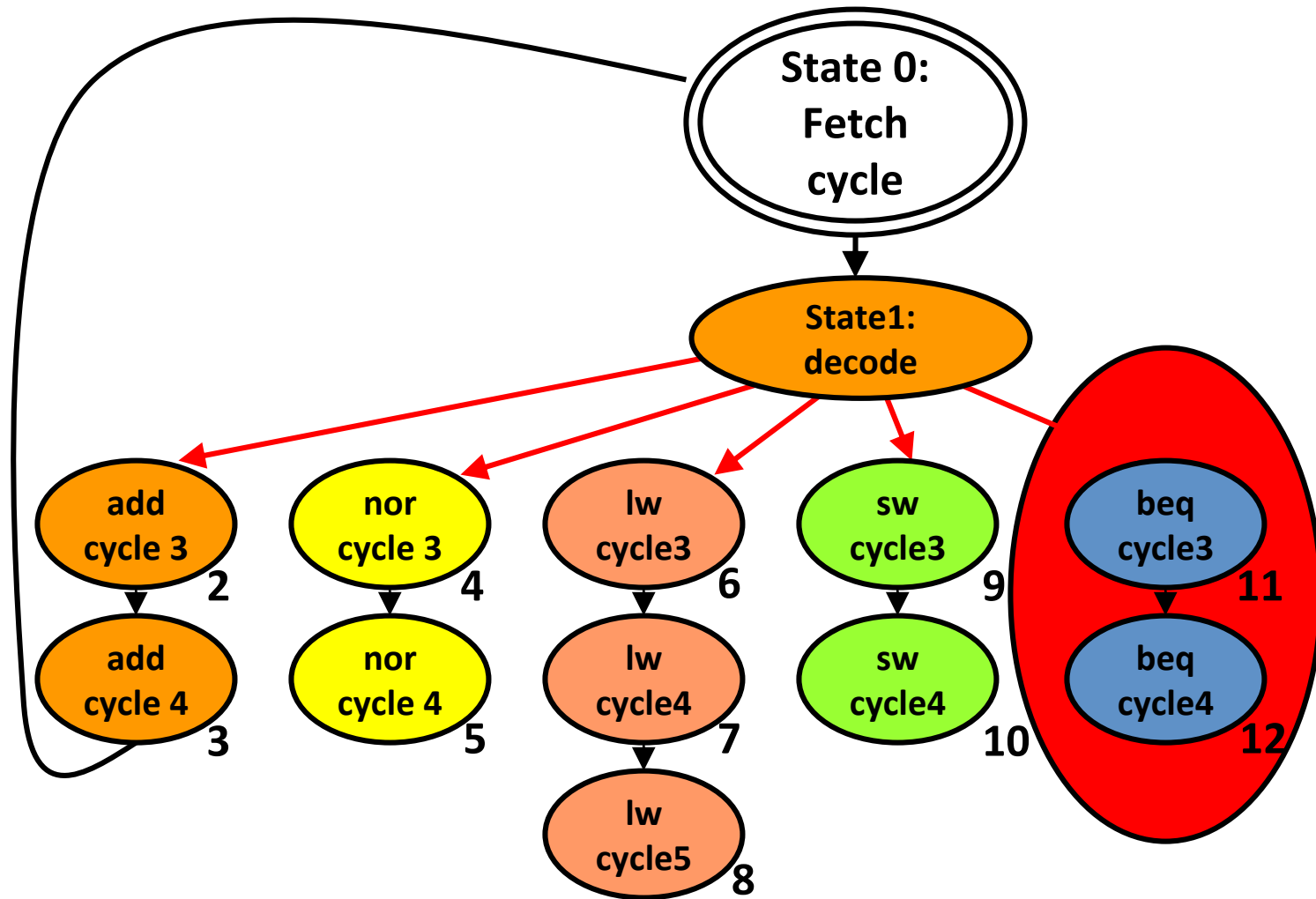


State 11: beq cycle 3

Calculate target address for branch

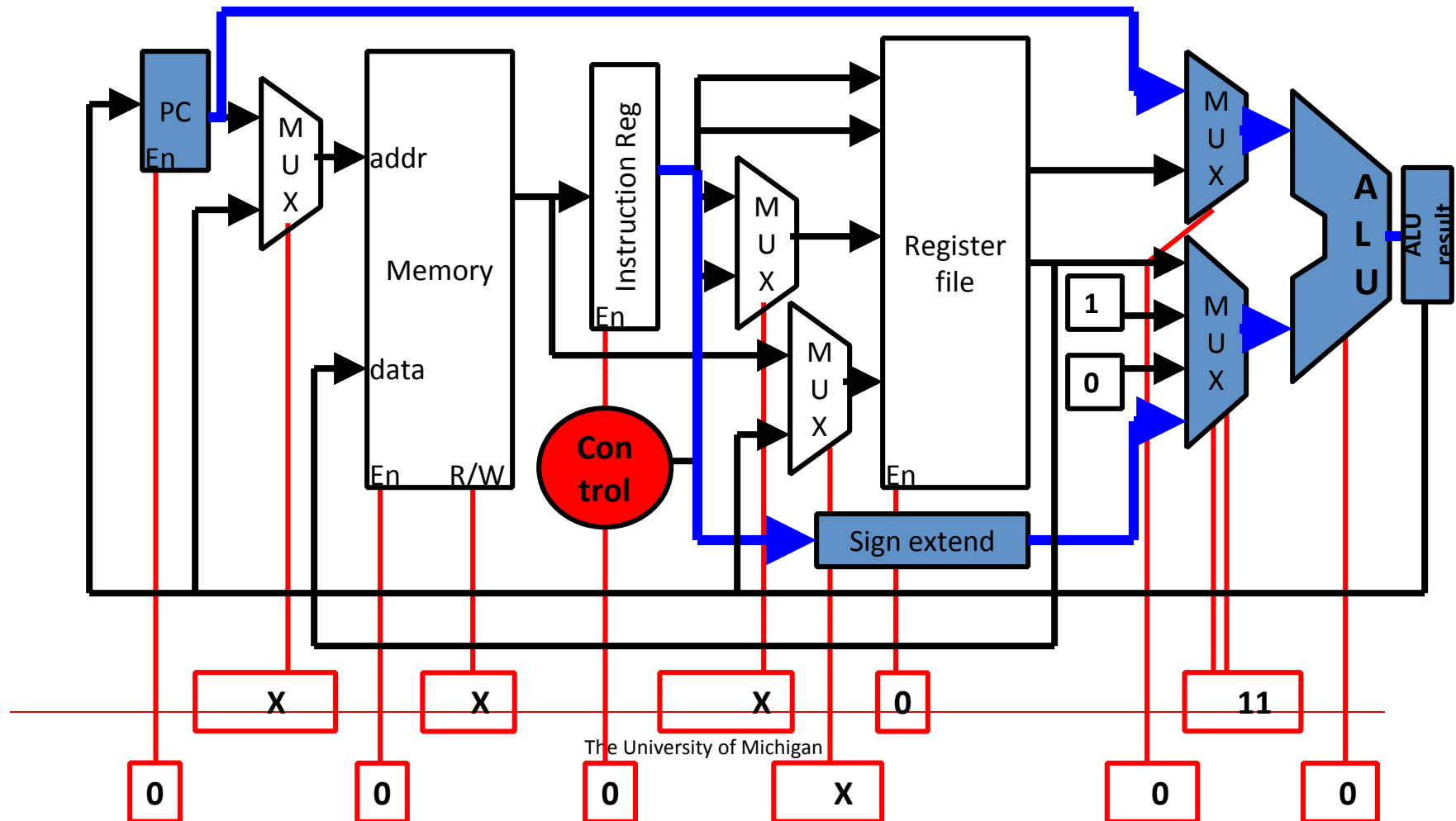


Control ROM (beq cycle 3)

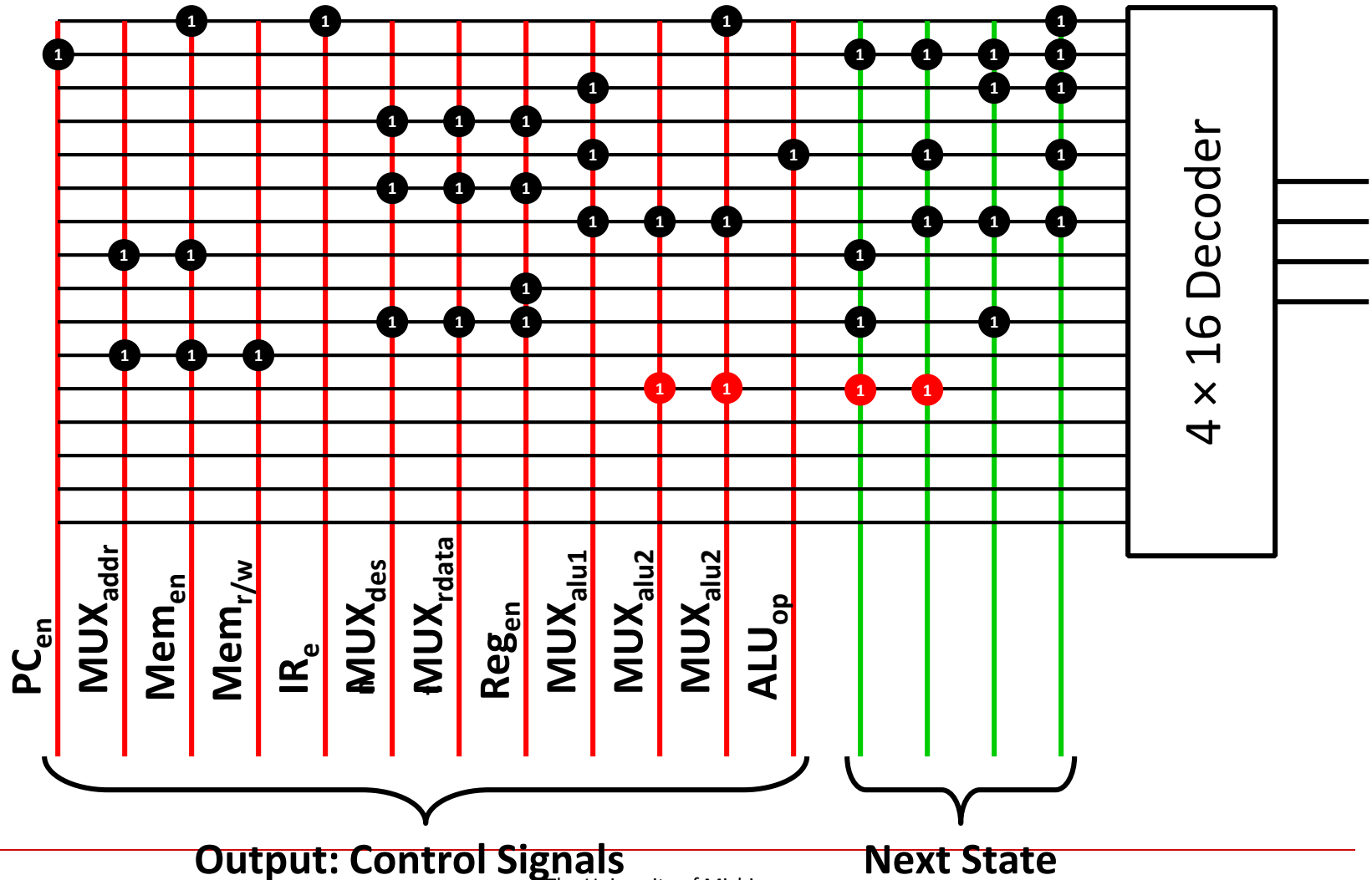


State 12: beq cycle 4

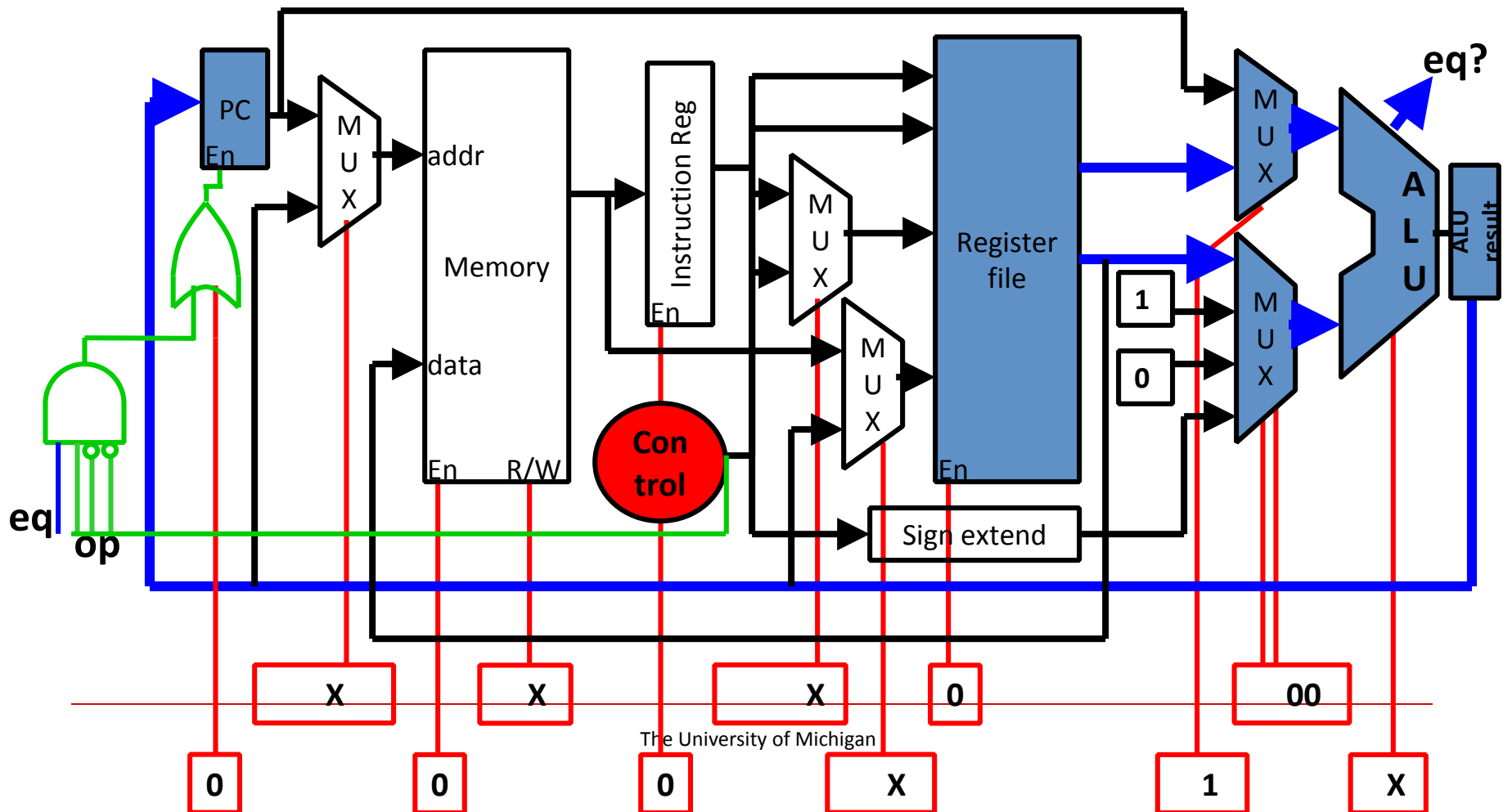
Write target address into PC
if ($\text{data}_{\text{rega}} == \text{data}_{\text{regb}}$)



Control ROM (beq cycle 4)

 

OK, what about the JALR instruction?

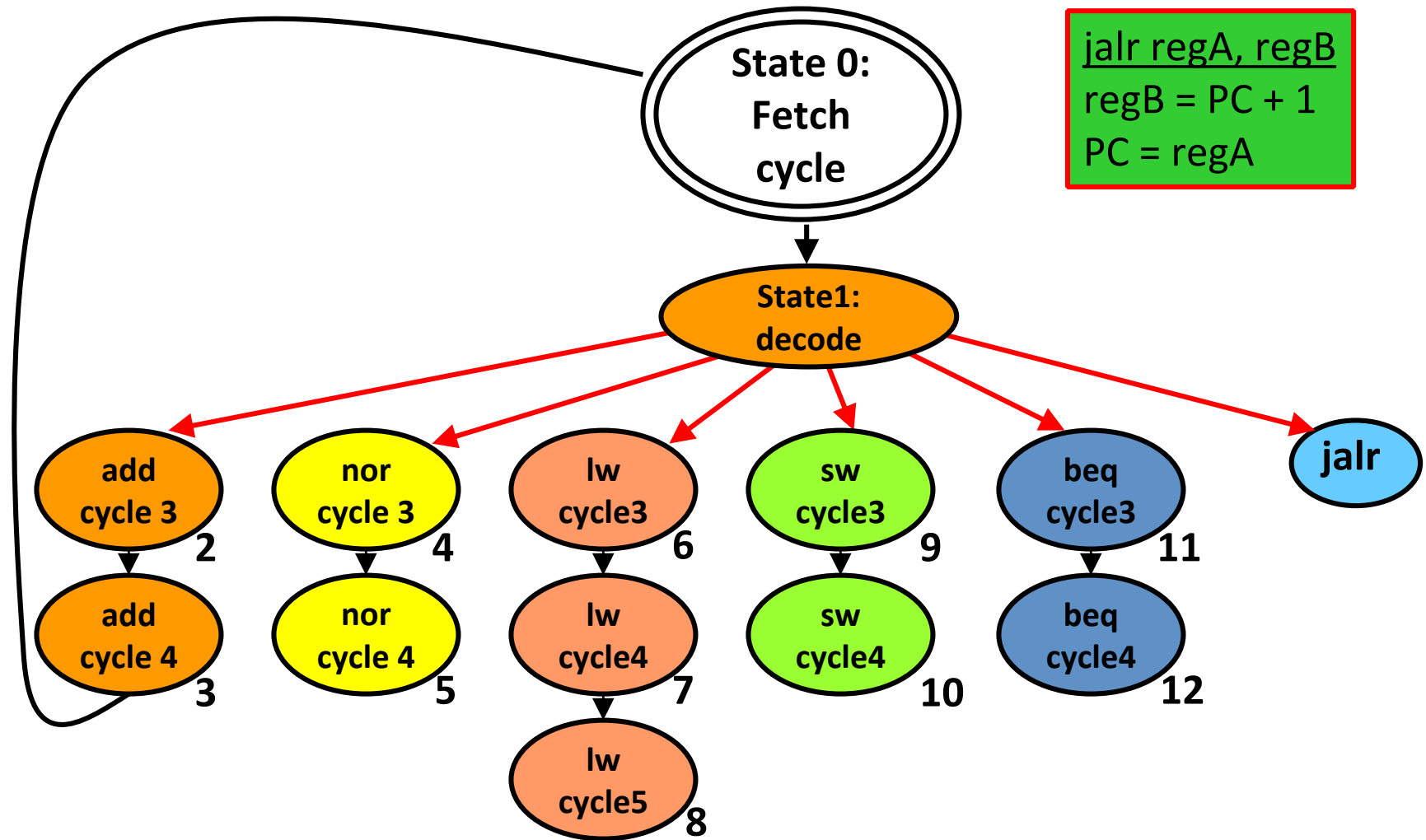

Single and Multicycle Performance

- 1 ns – Register File read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

1. Assuming the above delays, what is the best cycle time that the LC2k multicycle datapath could achieve?
2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

Single and Multicycle Performance

1 ns – Register read/write time

2 ns – ALU/adder

2 ns – memory access

0 ns – MUX, PC access, sign extend, ROM

1. Assuming the above delays, what is the best cycle time

that the LC2k multicycle datapath could achieve?

MC: $\text{MAX}(2, 1, 2, 2, 1) = 2\text{ns}$

SC: $2 + 1 + 2 + 2 + 1 = 8\text{ ns}$

2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

SC: $100\text{ cycles} * 8\text{ ns} = 800\text{ ns}$

MC: $(25*5 + 10*4 + 45*4 + 20*4)\text{cycles} * 2\text{ns} = 850\text{ ns}$