

# 9. Foundations of processor design: Memory Elements and Sequential Logic

---

**EECS 370 – Introduction to Computer Organization – Winter 2023**

**EECS Department  
University of Michigan in Ann  
Arbor, USA**

# Upcoming stuff


---

- ❑ Project 1s and 1m
  - Due today!
- ❑ HW2
  - Due Monday 2/6
  - Group part is non-trivial
- ❑ Project 2 is posted
  - 2a due Thursday 2/16
  - 2l due Thursday 2/23
  - 2c due Tuesday 3/10 (after break)
- ❑ HW3 out early next week, due Monday 2/20
- ❑ Midterm: Thursday 3/9 7-9pm


# Recap: Combinational Circuits – implement Boolean expressions

- ❑ **No memory**: Output a function only of input
  - ❑ Undefined input implies undefined output
- Adder is the basic gate of the ALU
  - Decoder is the basic gate of indexing
  - MUX is the basic gate controlling data movement


## Half Adder

 

## Decoder

 


## MUX

 


# LC2K ALU – From the Previous Lecture...

**Circuit**

 

**Symbol**

 

**Next topic:**

---


# Sequential logic: giving memory to circuits

# What is sequential logic?

---

- ❑ So far, we've covered combinational
  - Output is determined from input
  - But computers don't work that way -- they have state
- ❑ Examples of state
  - Registers
  - Memory
- ❑ Sequential logic's output depends not only on the current input, but also on its current state
- ❑ This lecture will show you how to build sequential logic from gates
  - The key is feedback


## Let's look at the following circuit

 

S	R	Q	$\bar{Q}$
0	1	0	1

What is the value of Q if R is 1 and S is 0?

# Building the Truth Table

 


$S$	$R$	$Q$	$\bar{Q}$
0	1	0	1
1	0	1	0

What is the value of  $Q$  if  $R$  is 0 and  $S$  is 1?



# For a Basic Memory Cell

 


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0

What is the value of  $Q$  if  $R$  is 0 and  $S$  is 0?

As long as  $R$  and  $S$  remain 0 then the value  $Q$  (and  $\bar{Q}$ ) will remain unchanged. This value is **stored** in this circuit. **This is a basic memory cell.**

## With “invalid” inputs 1,1

 


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

**Invalid ~ AVOID!**

What is the value of  $Q$  if  $R$  is 1 and  $S$  is 1?

$Q$  and  $\bar{Q}$  are supposed to be opposite of each other, so **this is a state we avoid**. This state can also lead to unstable future states. Try setting  $S = 0$  and  $R = 0$  now!


# SR Latch

 

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	BAD	

- What do S and R stand for?
- Set and Reset


# Transparent D Latch

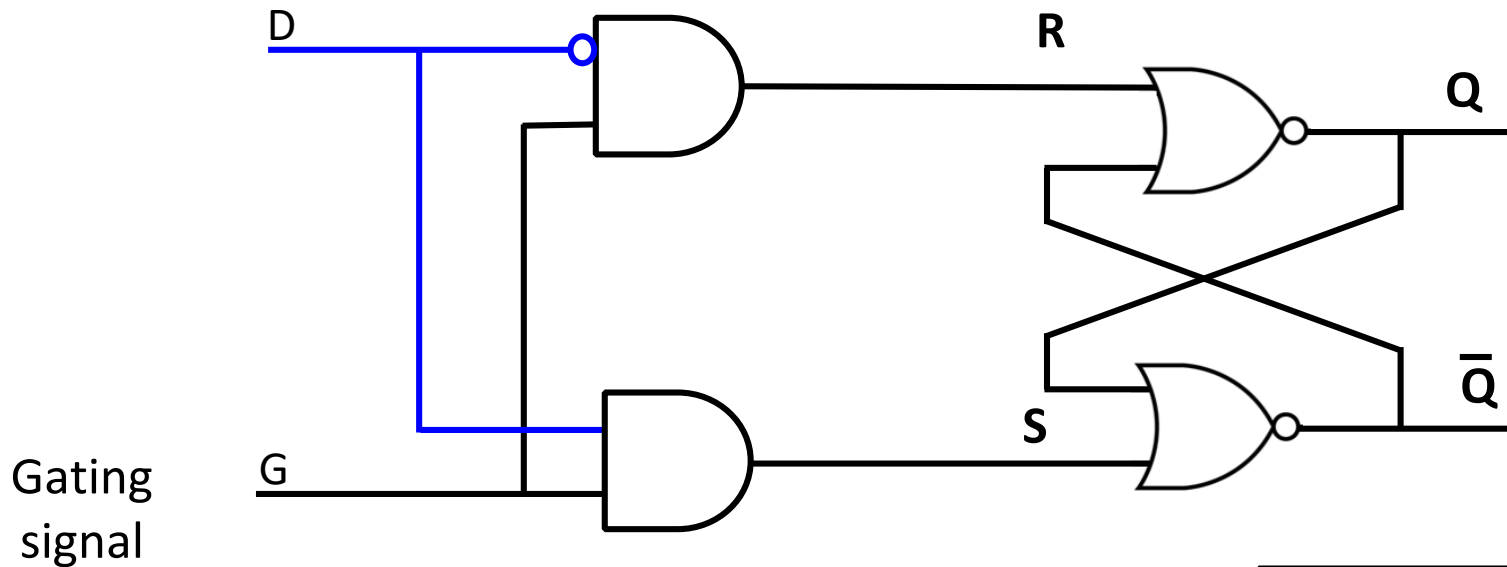


Next  
state  
is set

D	G	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	Q	$\bar{Q}$
1	1	1	0

 Set state  
is retained  
when gate  
is low



No invalid  
states ☺

 
[illegible]

Q changes when G is high.  
Q is preserved when G is low
 
# Is D-Latch Sufficient?


---

- Can we use D-latches to build our Program Counter logic?
- Idea:
  - Use 32 latches to hold current PC, send output Q to memory
  - Also pass output Q into 32-bit adder to increment by 1 (for word-addressable system)
  - Wrap sum around back into D as "next PC"
  - Once ready to execute next instruction, set G high to update



# Shortcoming of D-Latch

 - Problem: G must be set very precisely
  - Set high for too short: latch doesn't have enough time for feedback to stabilize
  - Set high for too long: Signal may propagate round twice and increment PC by 2 (or more)
- Challenging to design circuits with exactly the right durations



Not just a problem for PC, much of our processor will involve logic like this

# Adding a clock to the mix

---

- ❑ We can design more interesting circuits with a clock
  - ❑ Enables a sequential circuit to **predictably** change state (and store information)
  - ❑ A clock signal alternates between 0 and 1 states at a fixed frequency (e.g., 100MHz)
  
- ❑ What should the clock frequency be?
  - ❑ It depends on the longest propagation delay between state and next state combination logic
  - ❑ And a few other things beyond this class (*shout out 270*)




# Clocks


---
 
## ❑ Clock signal

- Periodic pulse
- Generated using oscillating crystal or ring oscillator
- Distributed throughout chip using clock distribution net



# Adding a Clock to the Mix

 


We won't discuss it further here, but this circuit sets  $Q=D$  **ONLY** when clock transitions from 0 -> 1

Intuitively, the design works by inverting the Gate signals, so only one passes at a time (like a double set of sliding doors)




# D Flip-Flop Timing Diagram

---

 


# What happens if Data changes on a clock edge?

---

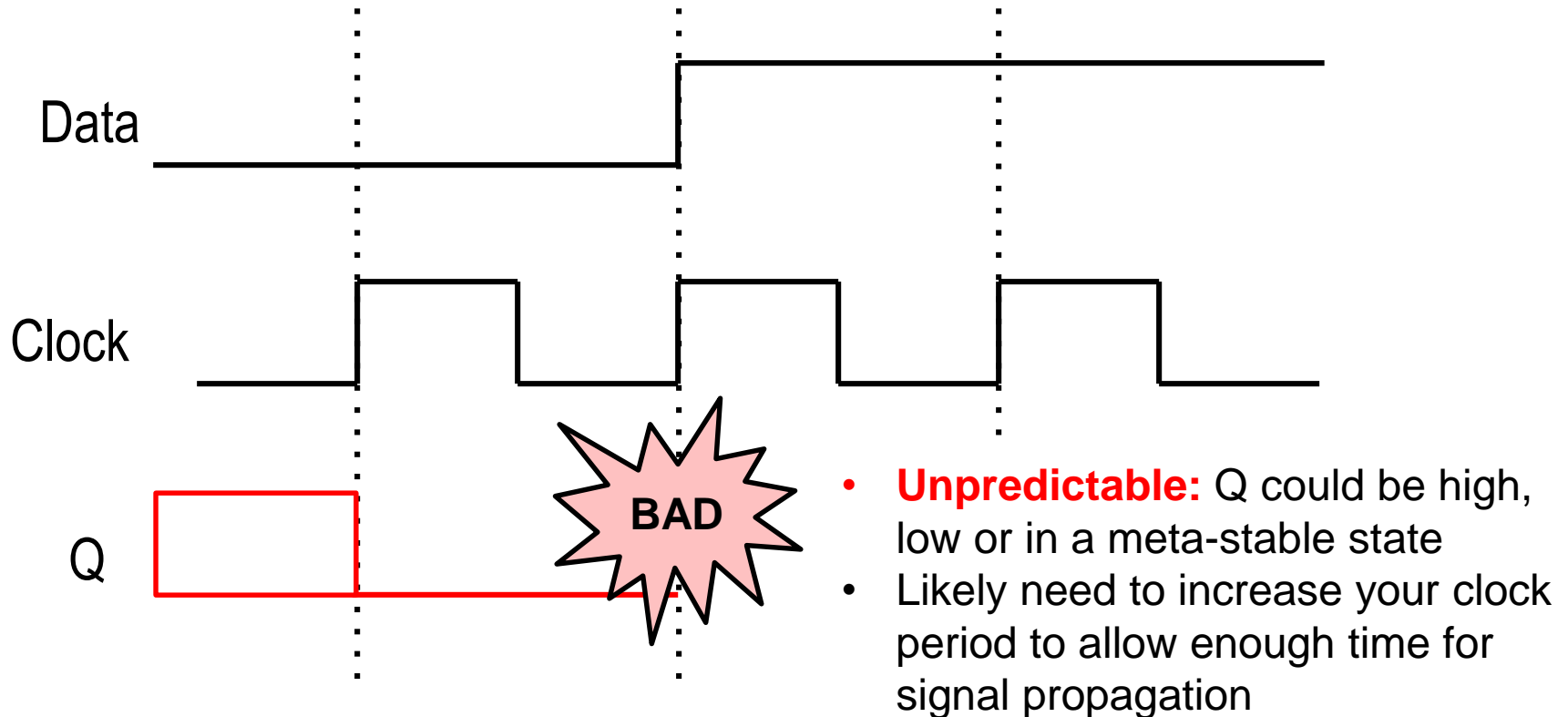


# Latches vs Flip-flops


---

 

D Latch

 

D Flip-flop

 

Enabled D Flip-flop  
(only updates on clock edge if 'en'  
is high)

# Finite State Machines

---

- ❑ So far we can do two things with gates:
  1. Combinational Logic: implement Boolean expressions
    - Adder, MUX, Decoder, logical operations etc
  2. Sequential Logic: store state
    - Latch, Flip-Flops, Memory
- ❑ How do we combine them to do something interesting?
  - Let's take a look at implementing the logic needed for a vending machine
  - Discrete states needed: remember how much money was input
    - Store sequentially
  - Transitions between states: money inserted, drink selected, etc
    - Calculate combinational or with a control ROM (*more on this later*)

# Vending Machine

---

- ❑ We could use a general purpose processor
- ❑ However, a custom controller will be:
  - Faster
  - Lower power
  - Cheaper to produce in high volume
- ❑ On the other hand, a custom controller:
  - Will be slower to design
  - More expensive in low volume
- ❑ Goals:
  - Take money, vend drinks.



# Input and Output


---

## ❑ Inputs:

- Coin trigger
- Refund button
- 10 drink selectors
- 10 pressure sensors
  - Detect if there are still drinks left
 
## ❑ Outputs:

- 10 drink release latches
- Coin refund latch





# Operation of Machine

---

- ☐ Accepts quarters only
- ☐ All drinks are \$0.75
- ☐ Once we get the money, a drink can be selected
- ☐ If they want a refund, release any coins inserted
- ☐ No free drinks!
- ☐ No stealing money.



# Building the controller

---

## ❑ Finite State

- Remember how many coins have been put in the machine and what inputs are acceptable

## ❑ Read-Only Memory (ROM)

- Define the outputs and state transitions

## ❑ Custom combinational circuits

- Reduce the size (and therefore cost) of the controller

# Finite State Machines

---

- ❑ A Finite State Machine (FSM) consists of:
  - K states:  $S = \{s_1, s_2, \dots, s_k\}$ ,  $s_1$  is initial state
  - N inputs:  $I = \{i_1, i_2, \dots, i_n\}$
  - M outputs:  $O = \{o_1, o_2, \dots, o_m\}$
  - Transition function  $T(S, I)$  mapping each current state and input to next state
  - Output Function  $P(S)$  or  $P(S, I)$  specifies output
    - $P(S)$  is a Moore Machine
    - $P(S, I)$  is a Mealy Machine

# Two Common State Machines

---


- ❑ Moore machine

output function based on **current state**  $P(S)$  only

- ❑ Mealy machine

output function based on **current state** and **current input**  $P(S,I)$


# FSM for Vending Machine

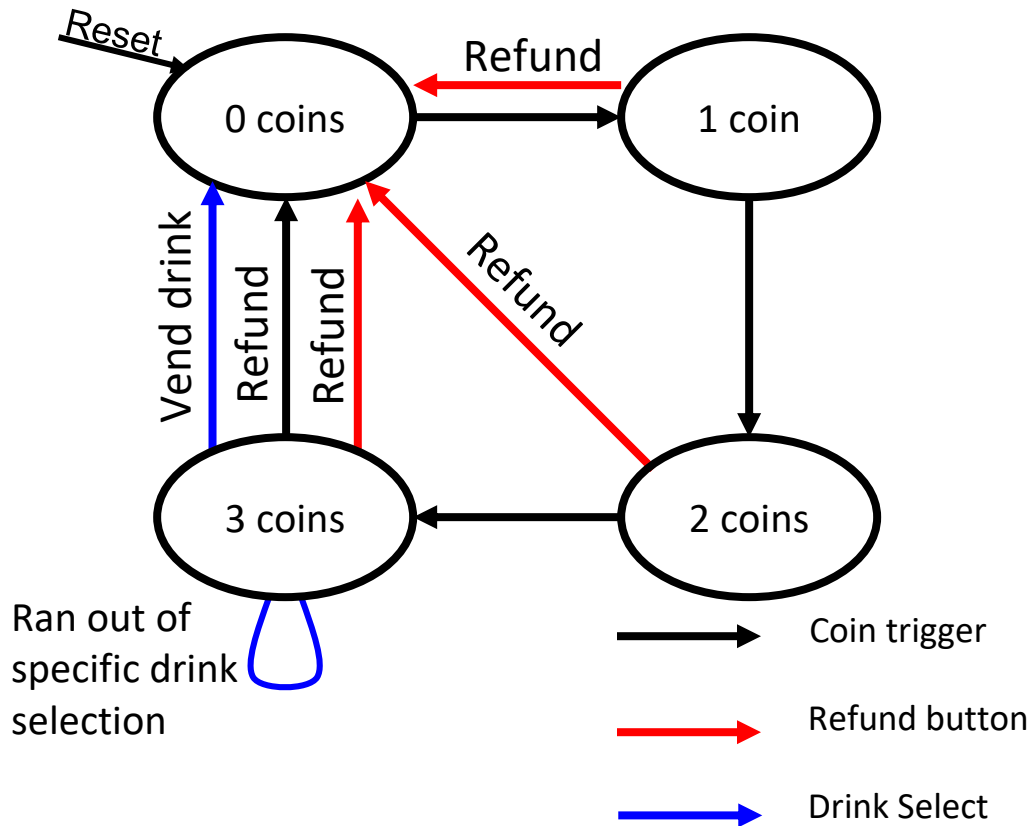

Is this a Mealy or Moore Machine?

Mealy ~ output is based on current state **AND** input

# Implementing a FSM

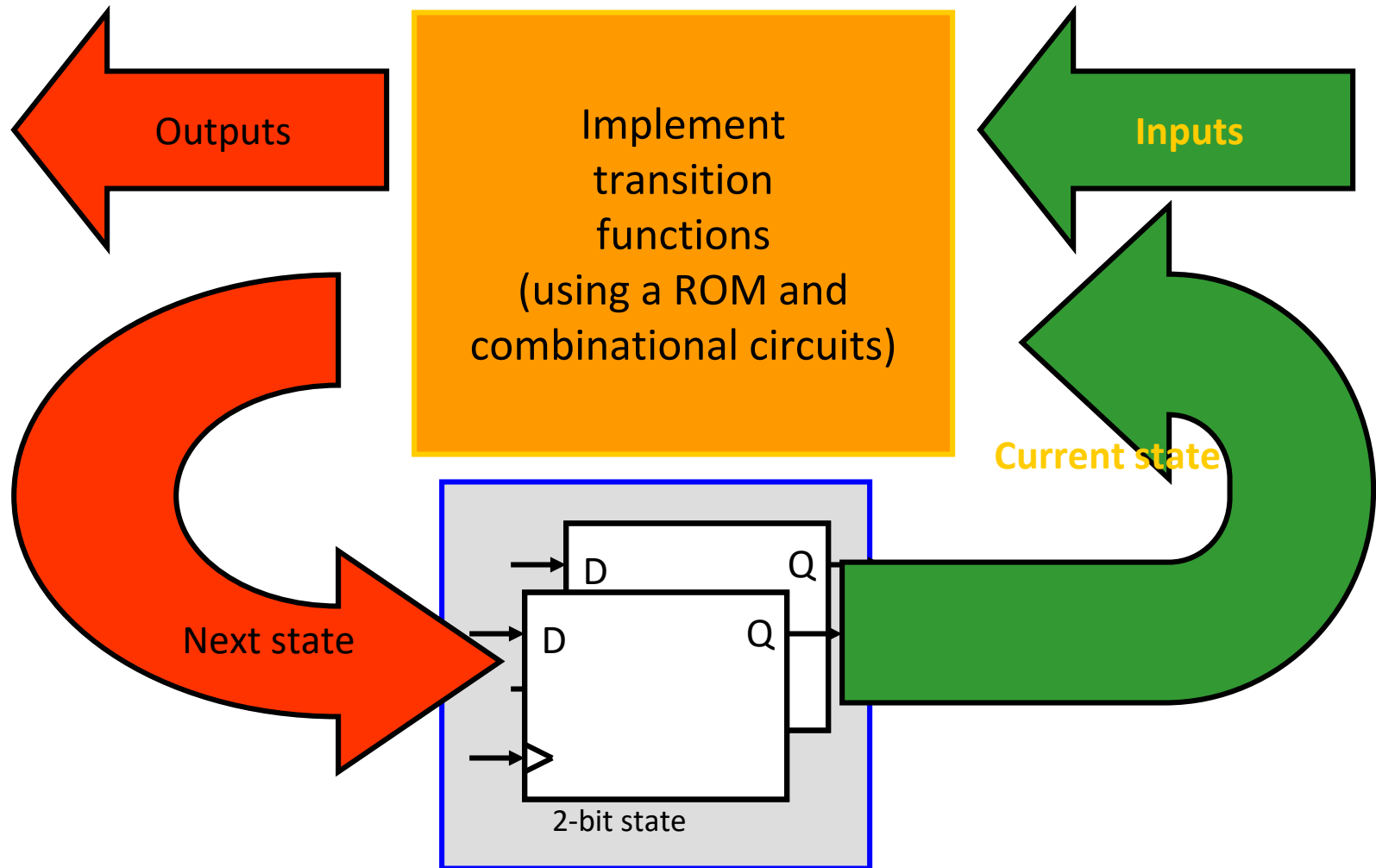

# ROMs and PROMs

---

## ❑ Read Only Memory

- Array of memory values that are constant
- Non-volatile


## ❑ Programmable Read Only Memory

- Array of memory values that can be written exactly once (destructive writes)

## ❑ You can use ROMs to implement FSM transition functions


- ROM inputs (i.e., ROM address): current state, primary inputs
- ROM outputs (i.e., ROM data): next state, primary outputs

# 8-entry 4-bit ROM

 




# 8-entry 4-bit ROM

 
 
# 8-entry 4-bit ROM

Poll: What's the formula for size of ROM needed?



# Aside: Other Memories

---

## ❑ Static RAM (random access memory)

- Built from sequential circuits
  - Takes 4-6 transistors to store 1 bit
  - Fast access (< 1 ns access possible)

## ❑ Dynamic RAM

- Built using a single transistor and a capacitor
  - 1's must be refreshed often to retain value
  - Slower access than static RAM
  - Much more dense layout than static RAM



## ❑ Both require constant power, or they will lose their data (i.e. are **volatile**)

## ❑ These will be used to build computer memory hierarchies (later in class)

# Implementing Combinational Logic

---


## ❑ Custom logic

- Pros:
  - Can optimize the number of gates used
- Cons:
  - Can be expensive / time consuming to make custom logic circuits

## ❑ Lookup table:

- Pros:
  - Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly
- Cons:
  - Size requirement grows exponentially with number of inputs (adding one just more bit **doubles** the storage requirements!)

# Controller Design So far

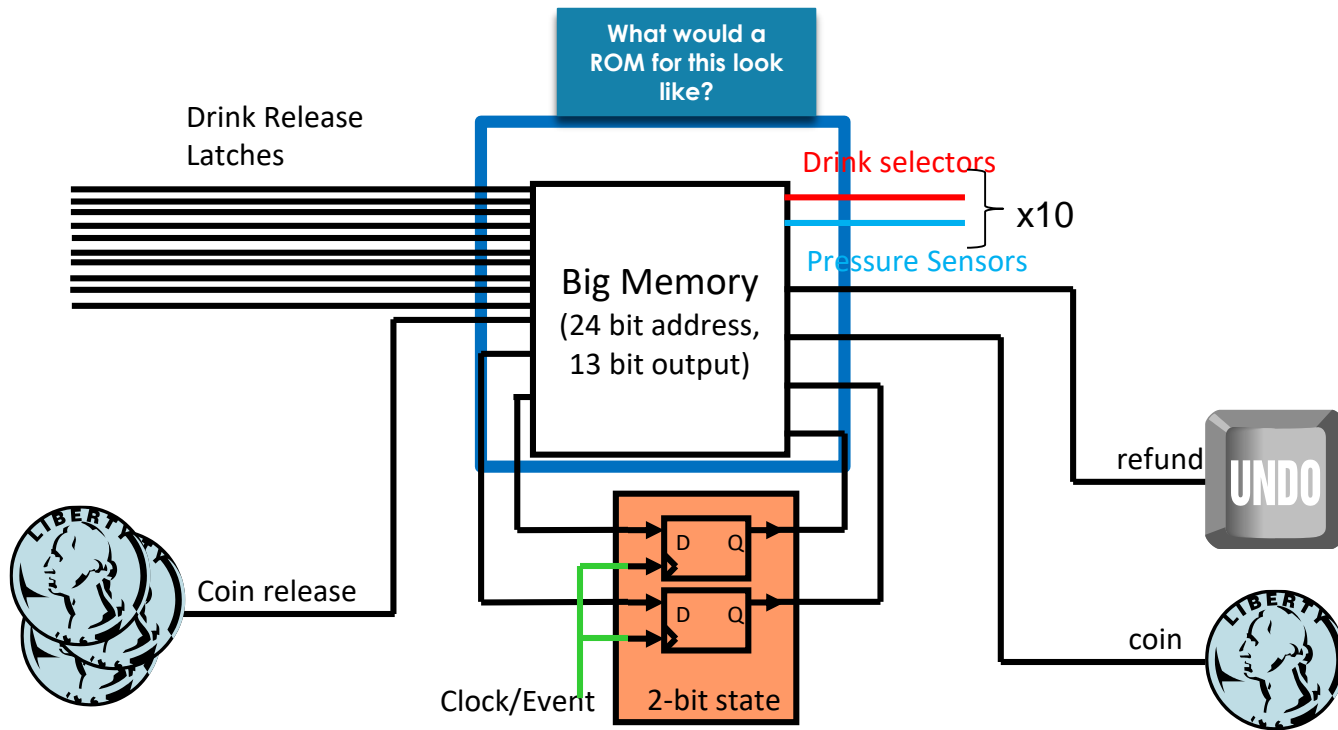

# ROM for Vending Machine Controller

---


- ❑ Use current state and inputs as address
  - 2 state bits + 22 inputs = 24 bits (address)
  - Coin, refund, 10 drink selectors, 10 sensors
  
- ❑ Read next state and outputs from ROM
  - 2 state bits + 11 outputs = 13 bit (memory)
  - Refund release, 10 drink latches
  
- ❑ We need  $2^{24}$  entry, 13 bit ROM memories
  - 218,103,808 bits of ROM seems excessive for our cheap controller

# Reducing the ROM needed

---


- ❑ Replace 10 selector inputs and 10 pressure inputs with a single bit input (drink selected)
  - Use drink selection input to specify which drink release latch to activate
  - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)
  
- ❑ Now:
  - 2 current state bits + 3 input bits (5 bit ROM address)
  - 2 next state bits + 2 control trigger bits (4 bit memory)
  - $2^5 \times 4 = 128$  bit ROM (good!)

# Putting it all together

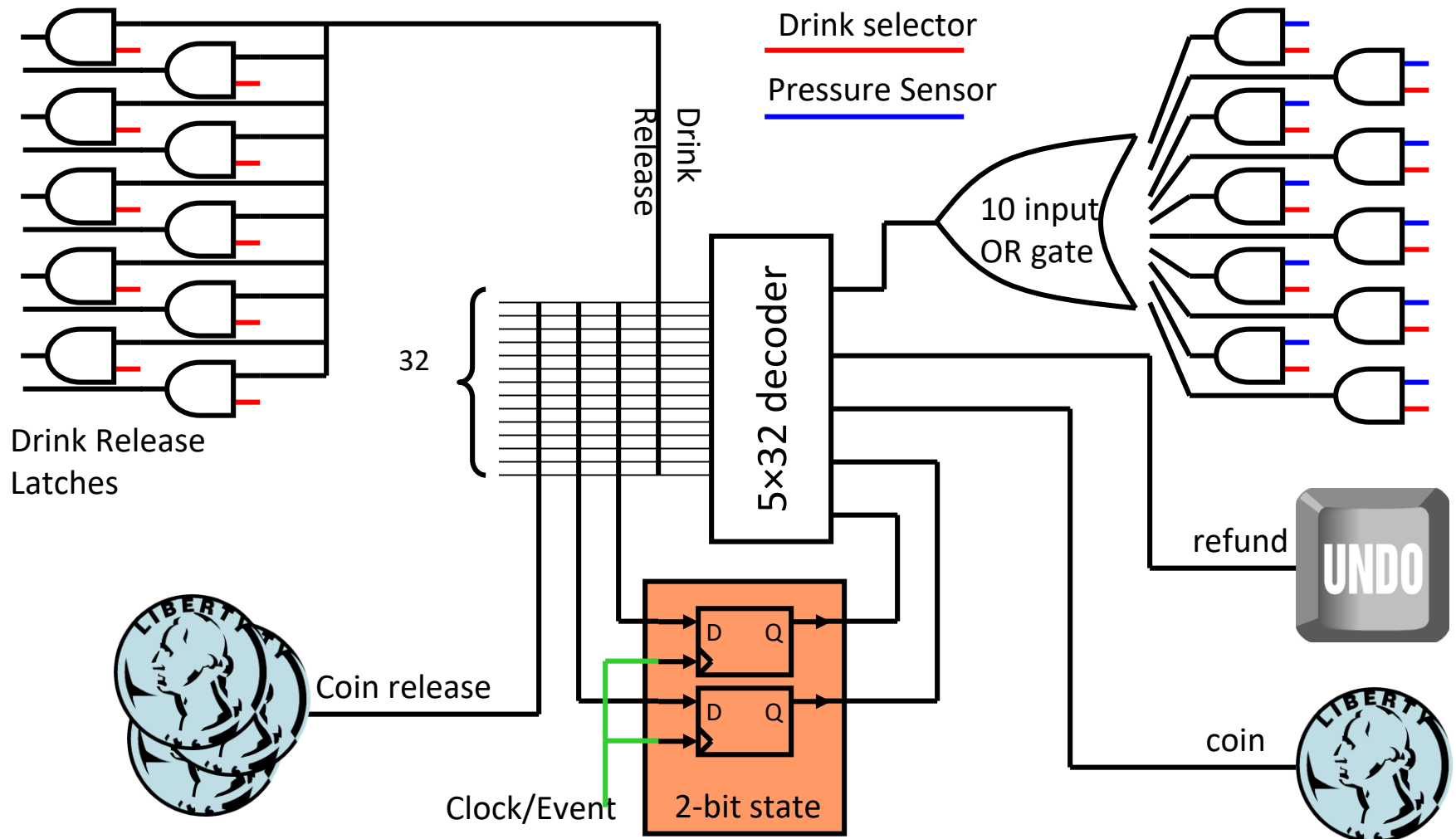



# Some of the ROM contents

 

Current state	Coin trigger	Drink select	Refund button	Next state	Coin release	Drink release
0 0	0	0	0	0 0	0	0
0 0	0	0	1	0 0	0	0
0 0	0	1	0	0 0	0	0
0 0	1	0	0	0 1	0	0
0 1	1	0	0	1 0	0	0
1 0	1	0	0	1 1	0	0
1 1	0	1	0	0 0	0	1
1 1	1	0	0	0 0	1	0
... 24 more entries				... 24 more entries		

ROM address (current state, inputs)

ROM contents (next state, outputs)

# Limitations of the controller

---

- ❑ What happens if we make the price \$1.00?, or what if we want to accept nickels, dimes and quarters?
  - Must redesign the controller (more state, different transitions)
  - A programmable processor only needs a software upgrade.
    - If you had written really good software anticipating a variable price, perhaps no change is even needed
  
- ❑ **Next Topic - Our first processor!**

# Single-Cycle Processor Design—LC2K

---


- ❑ General-Purpose Processor Design
  - Fetch Instructions
  - Decode Instructions
    - Instructions are input to control ROM
  - ROM data controls movement of data
    - Incrementing PC, reading registers, ALU control
  - Clock drives it all
  - Single-cycle datapath: Each instruction completes in one clock cycle

# Extra slides


---

- ❑ The following slides go into more detail about how an edge-triggered flip-flop works
  - And how it is built out of two D-latches and an inverter.
- ❑ This is more “for your information” though you may find it helpful in understanding some of this material.
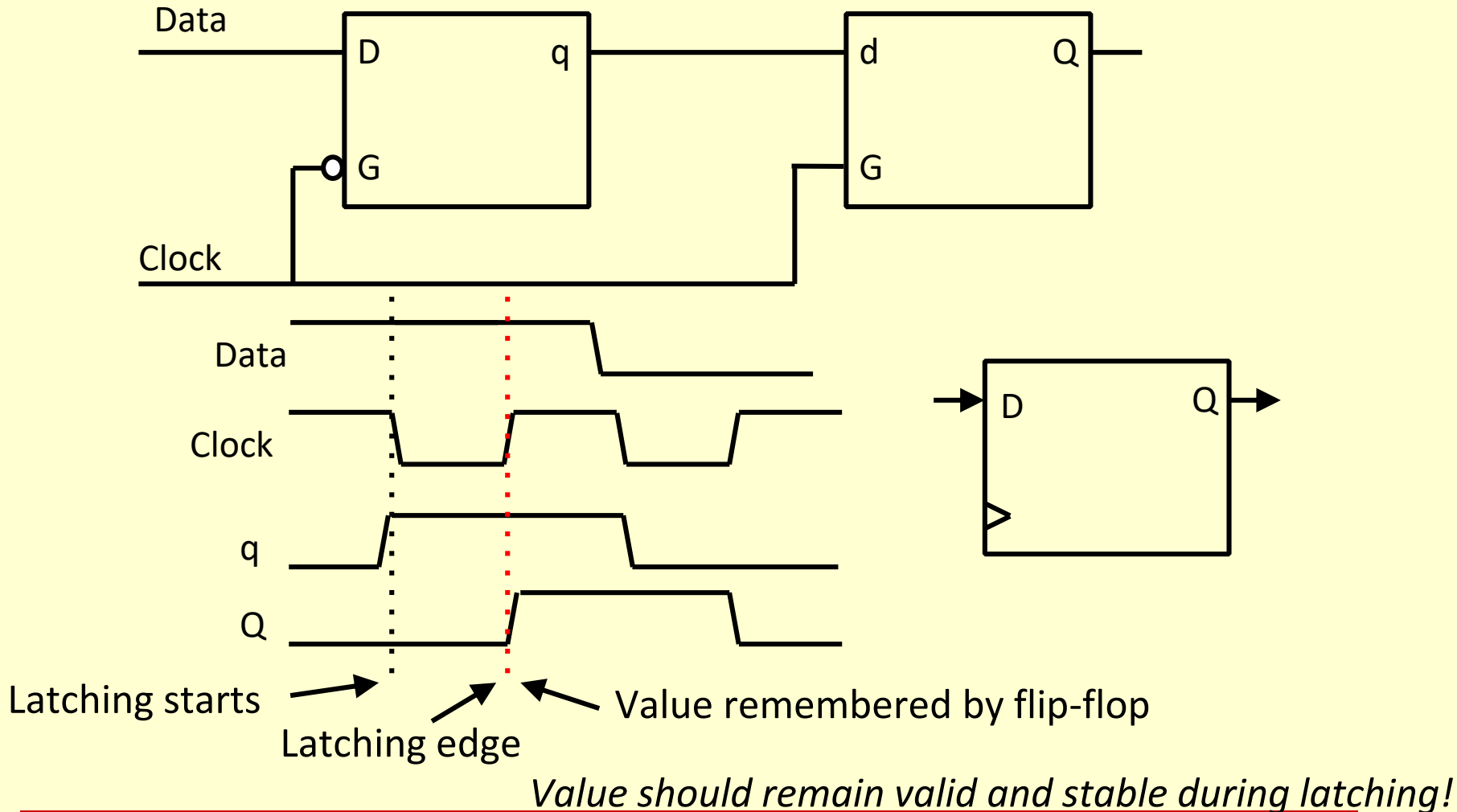
# Rising-Edge Triggered D Flip-flop (Extra slide)




# Extra Slides

 

- ❑ When "Clock" is low, first latch is transparent
- ❑ But Q is latched to previous value of q

# Extra Slides

---

 

- ❑ When "Clock" is high, q latches to D's value
- ❑ Second latch is transparent
- ❑ Q now holds value of D from the instant Clock went high
- ❑ Won't change again until the next instant clock goes from low to high

# Extra Slides

